

# Phase Measurements. Grounding.

M.V. Iordache, *EEGR2051 Circuits and Measurements Lab*, Fall 2020, LeTourneau University  
See <https://mviordache.name/EEGR2051> for more information.

# Review—Amplitude Measurements

- Based on the volts/div setting (vertical sensitivity) of the oscilloscope, amplitude measurements can be easily performed.

**Example 1:** If channel 2 (CH2) has 2V/div, then the peak-to-peak amplitude of the CH2 signal is


$$V_{pp2} = 3.6 \text{ div} \times 2 \frac{\text{V}}{\text{div}} = 7.2 \text{ V}.$$

**Example 2:** If channel 1 (CH1) has 1V/div, then the peak-amplitude of the CH1 signal is

$$V_{p1} = 3.2 \text{ div} \times 1 \frac{\text{V}}{\text{div}} = 3.2 \text{ V}.$$

The RMS value of the AC component on CH1 is
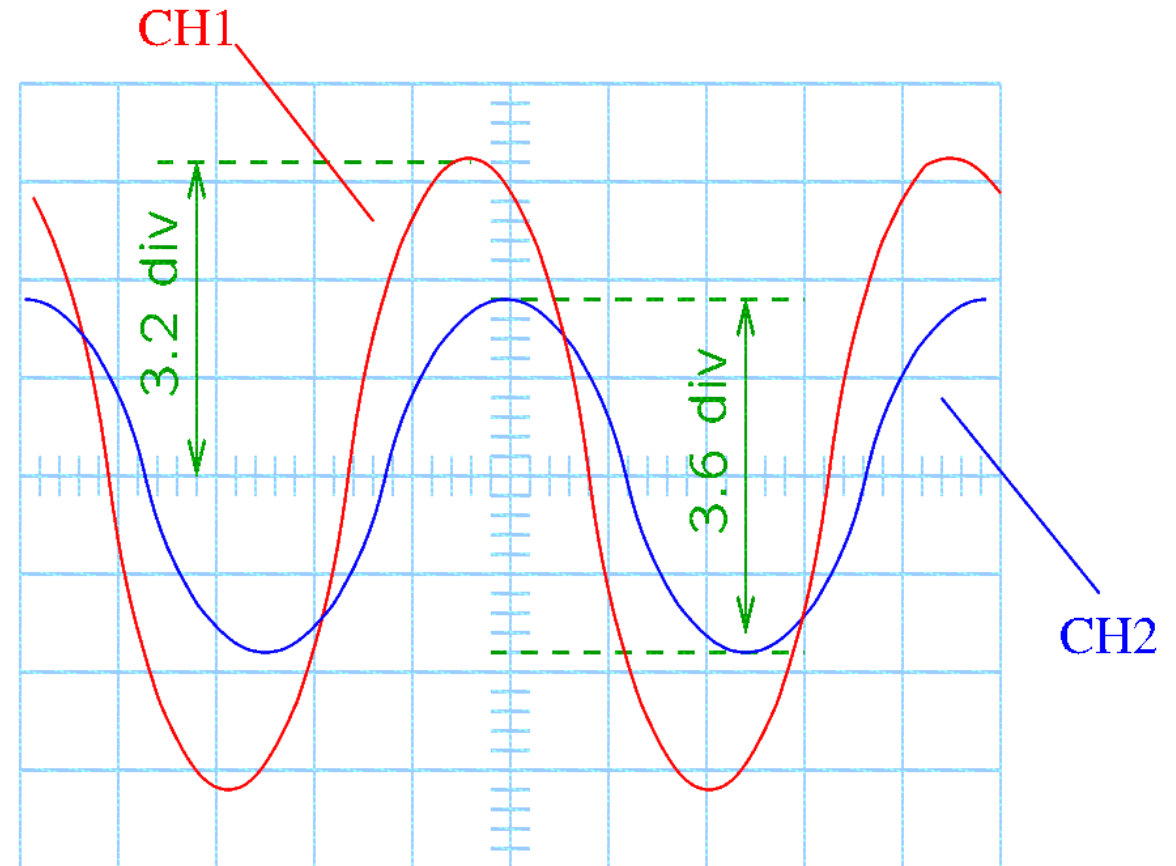
$$V_{rms1} = \frac{3.2}{\sqrt{2}} = 2.26 \text{ V}.$$



# Review—Frequency Measurements


- Based on the time/div setting (horizontal sensitivity) of the oscilloscope, time measurements can be easily performed.

**Example:** Assuming a horizontal sensitivity of  $5 \mu\text{s}/\text{div}$ , the period of the two signals is


$$T = 5 \text{ div} \times 5 \frac{\mu\text{s}}{\text{div}} = 25 \mu\text{s}.$$

The frequency is

$$f = \frac{1}{T} = 40 \text{ kHz}.$$

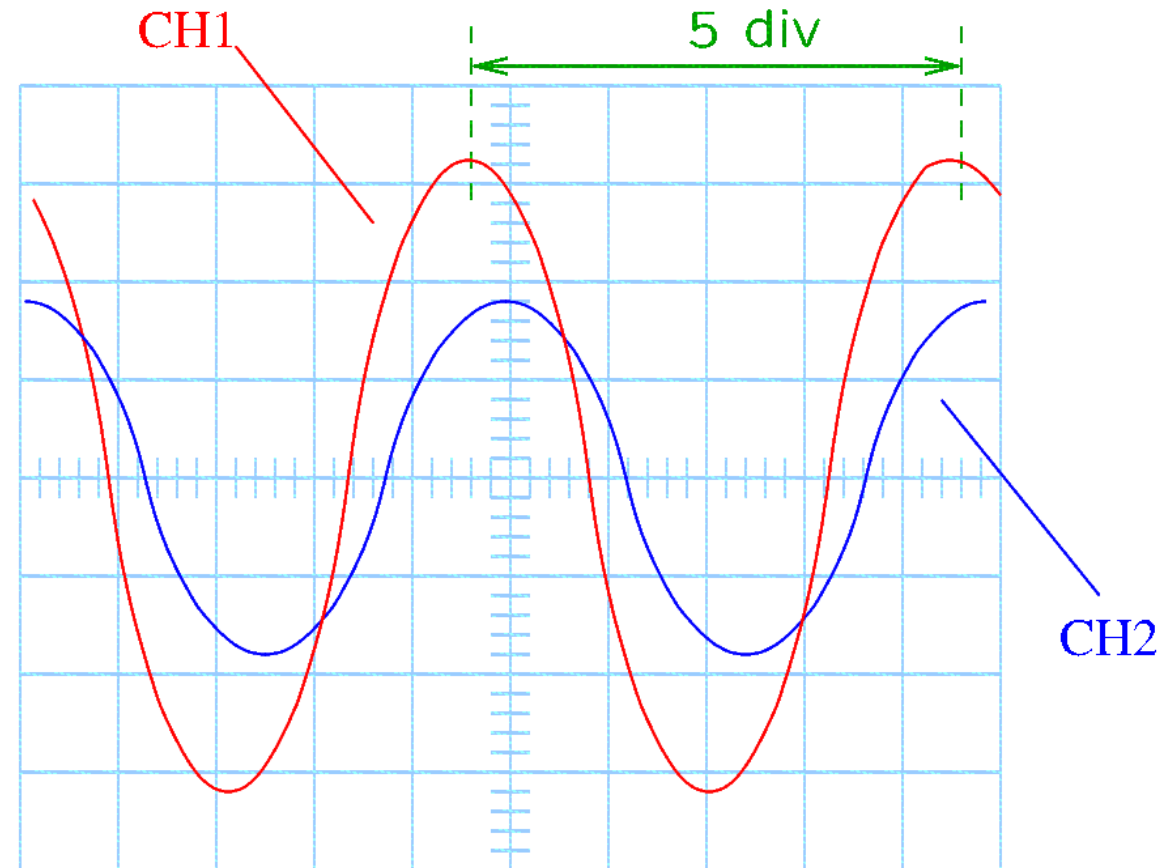

# The Sinusoidal Function

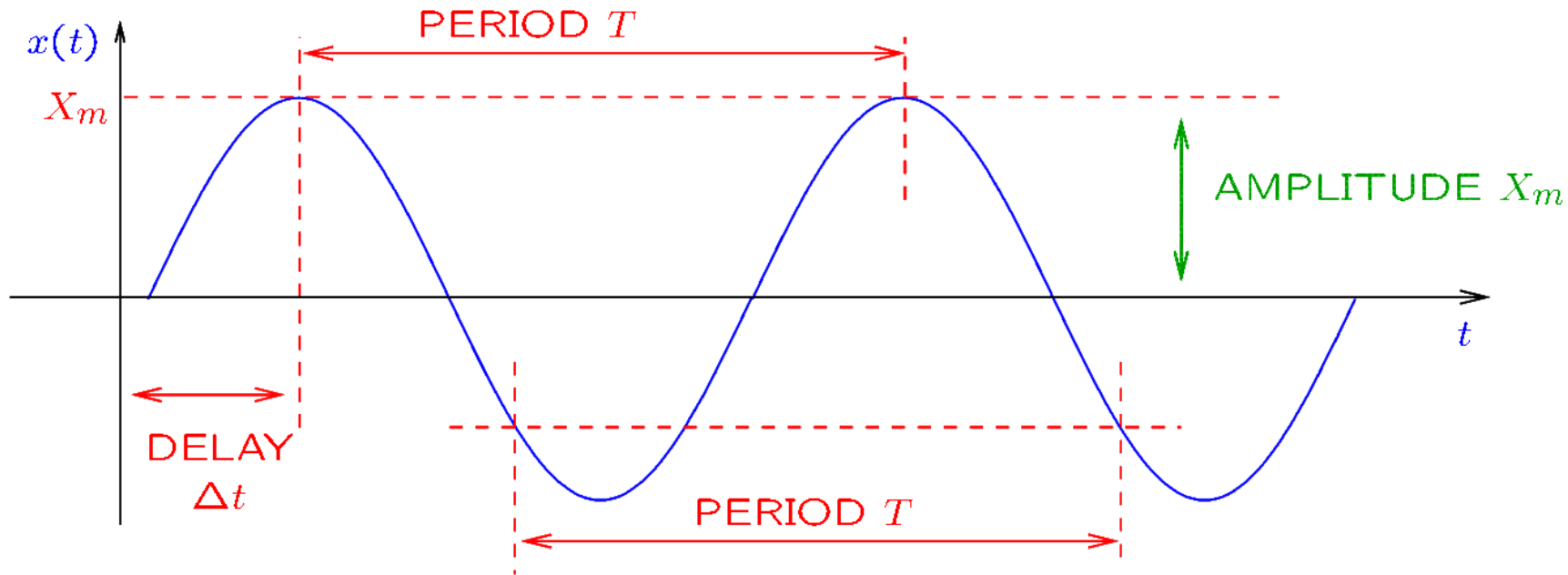


- The figure shows a delayed cosine,  $x(t) = X_m \cos(\omega(t - \Delta t))$ .
- Let  $\alpha = -\omega\Delta t$ .
- Then  $x(t) = X_m \cos(\omega t + \alpha)$

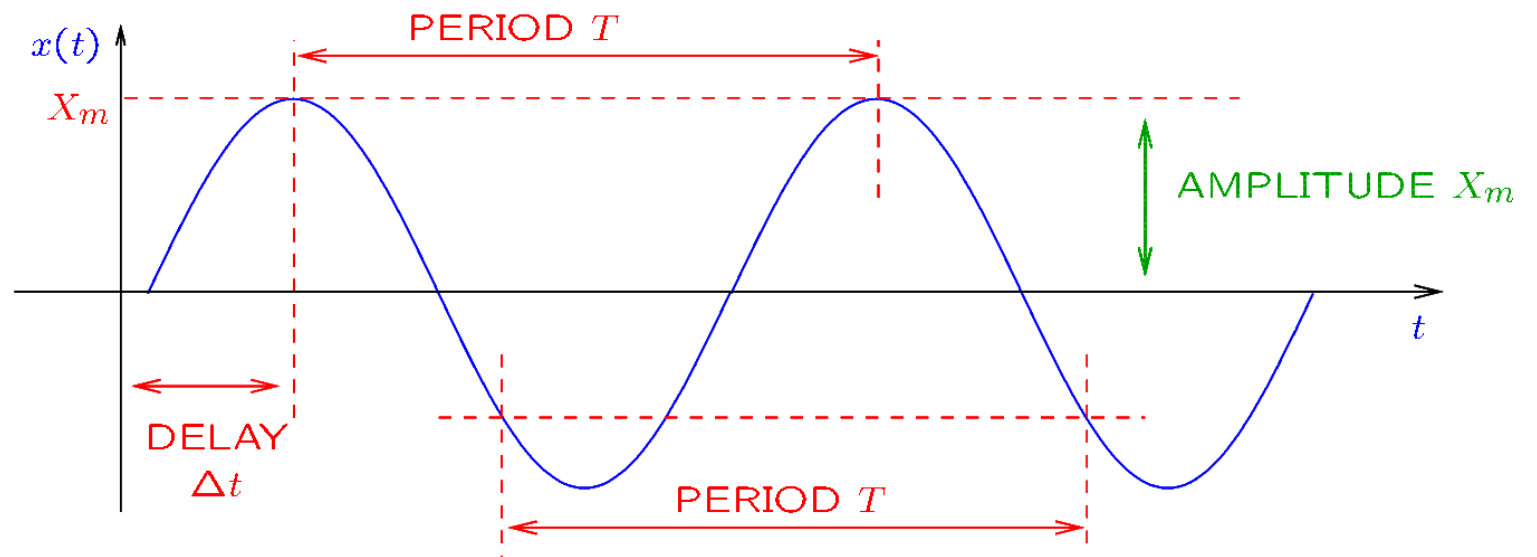
# The Sinusoidal Function

Given  $x(t) = X_m \cos(\omega t + \alpha)$  of period  $T$ :

- $\omega = \frac{2\pi}{T}$  is the **angular frequency**; it is measured in **rad/s**.
- $f = \frac{1}{T}$  is the **frequency**; it is measured in **Hz**.
- $\alpha$  is the **phase angle**; it is measured in **degrees** or **radians**.
- $X_m$  is the **peak amplitude**.




# Lead/Lag Relationships

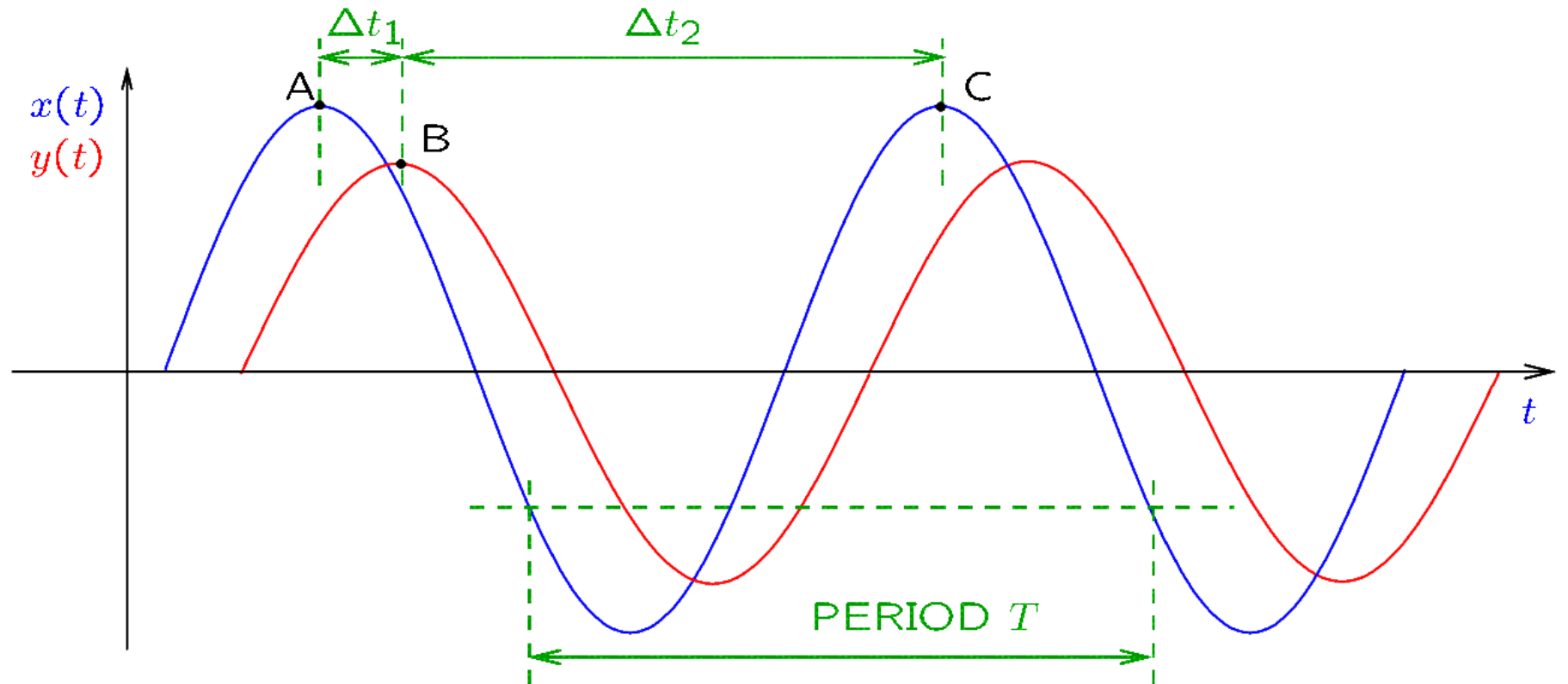


- When two signals have the same frequency, their phase can be compared.
- Note that  $x(t)$  reaches the peak A before  $y(t)$  reaches its peak B.
- Thus,  $x(t)$  leads  $y(t)$  by  $\Delta t_1$  and  $y(t)$  lags  $x(t)$  by  $\Delta t_1$ .

# Lead/Lag Relationships

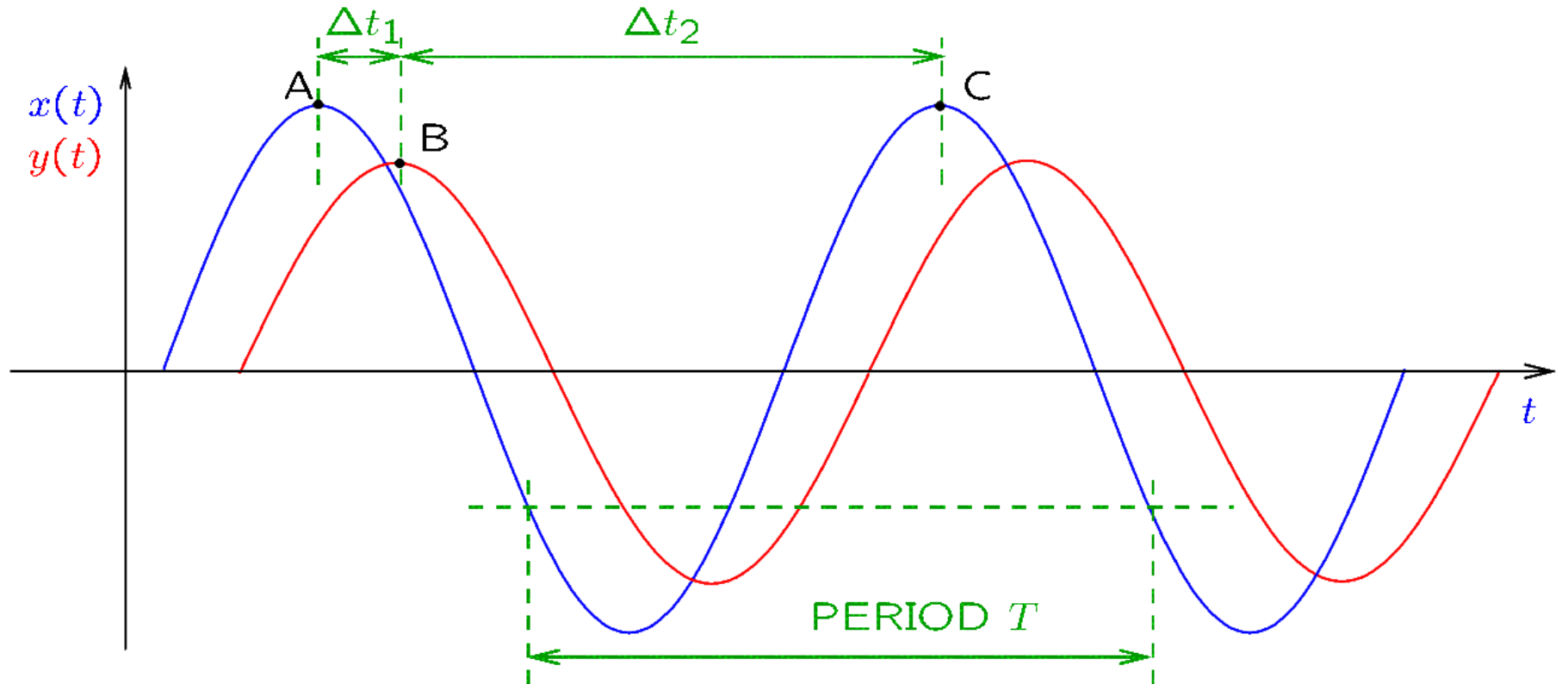

- A signal  $a(t)$  **leads** (**lags**)  $b(t)$  if it leads (lags) by less than half of a period.
- In the figure, though  $y(t)$  leads  $x(t)$  by  $\Delta t_2$ , we cannot say that  $y(t)$  leads  $x(t)$  because  $\Delta t_2 > T/2$ .

# Phase Difference

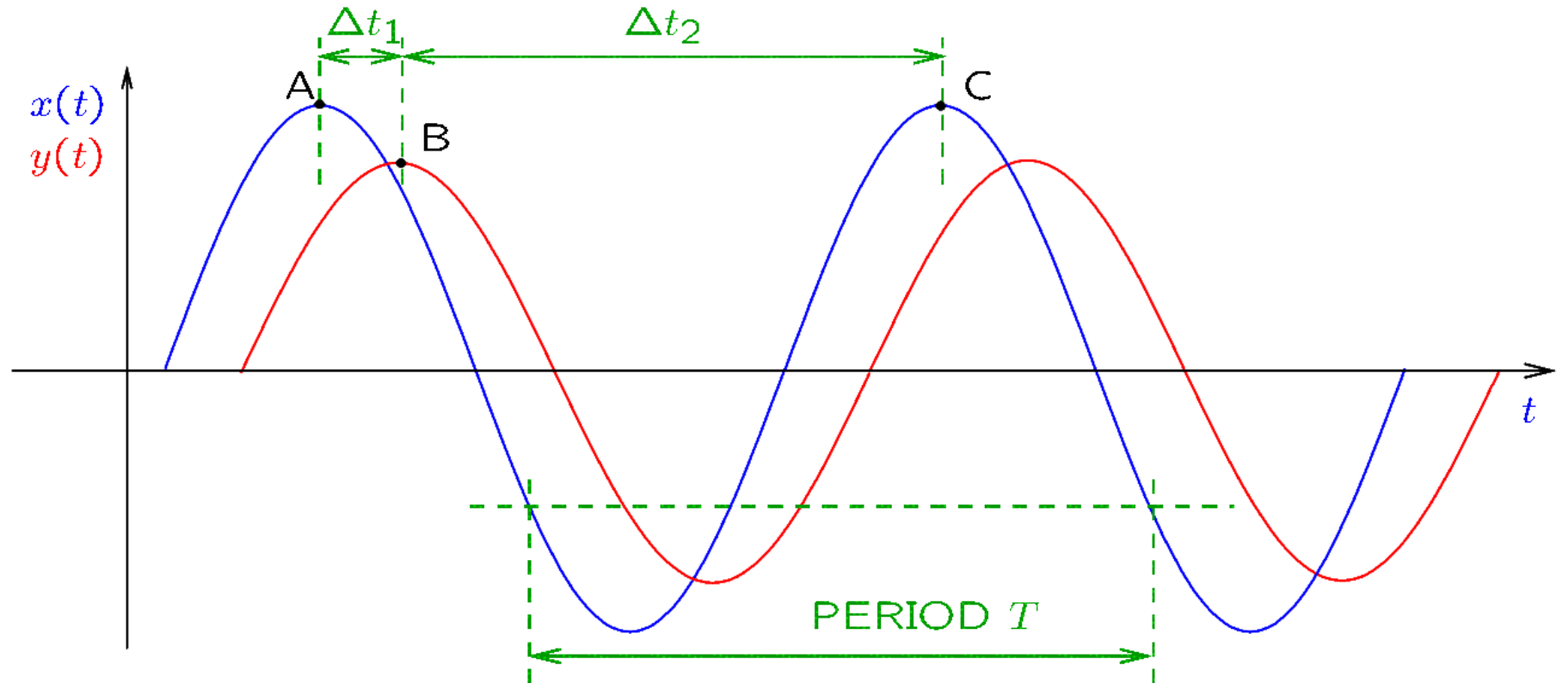


- We will express the lead/lag relationship in terms of the phase difference

$$\theta = \omega \Delta t_1 = 360^\circ \cdot \Delta t_1 / T$$


- $x(t)$  **leads**  $y(t)$  by  $\Delta\phi$  and  $y(t)$  **lags**  $x(t)$  by  $\theta$ .
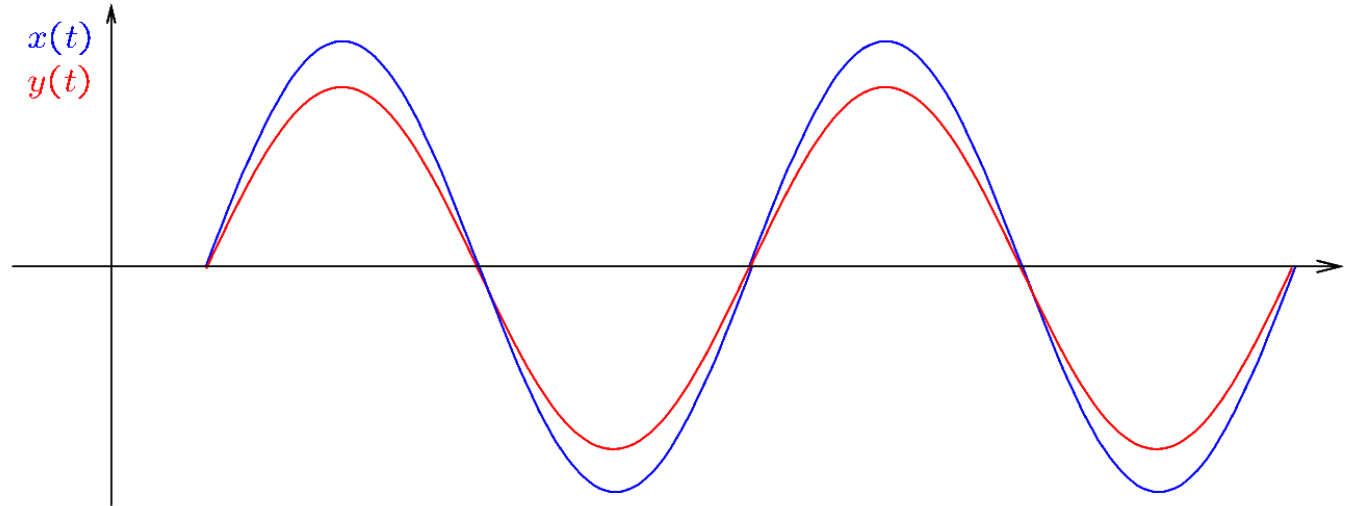
# Phase Difference

- When  $\theta = 0$  the signals are **in phase**.




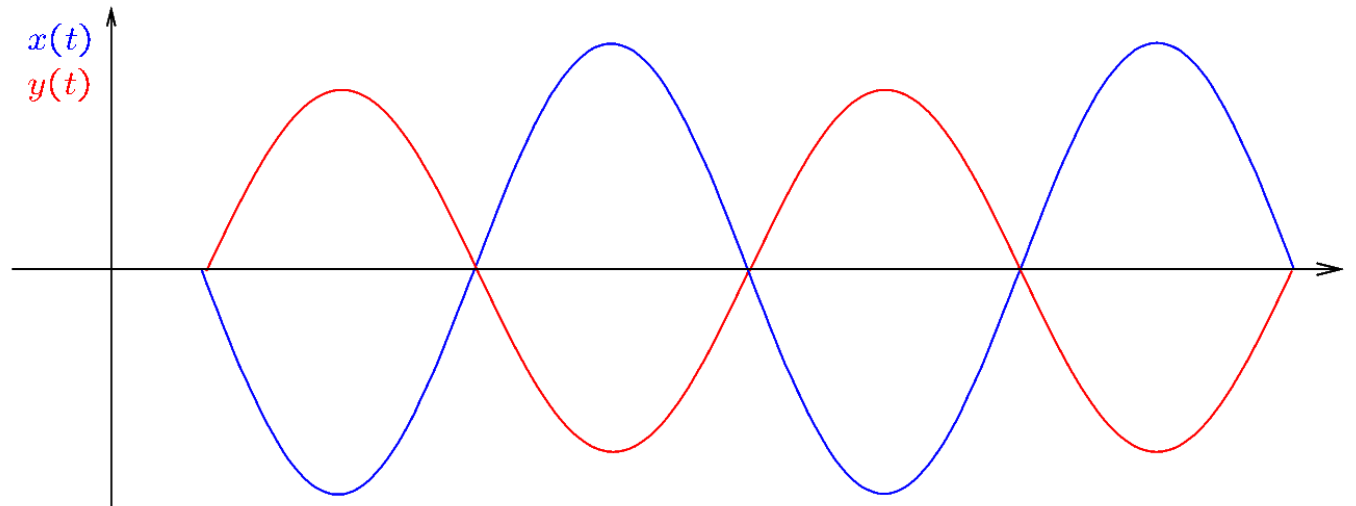- When  $\theta = 180^\circ$  the signals are  **$180^\circ$  out of phase**.


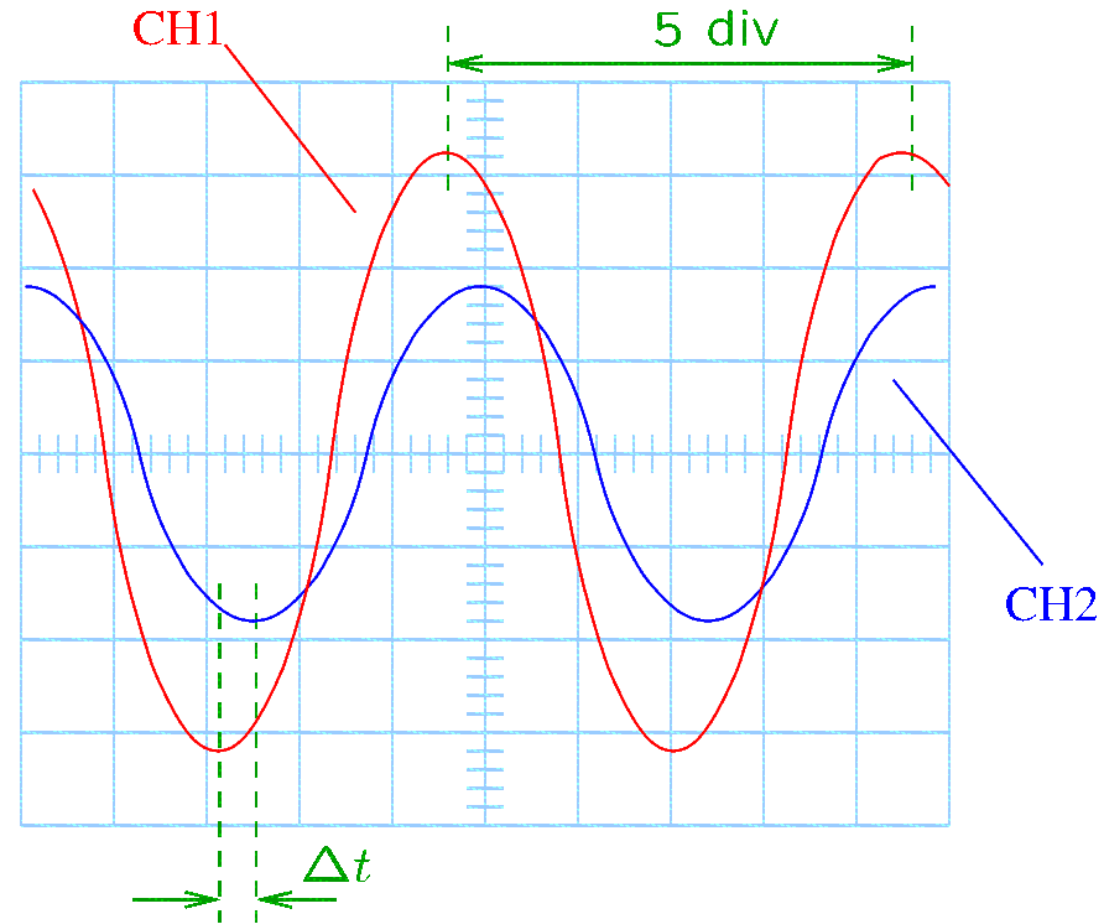
# Phase Measurements—Example

- Note that CH1 **leads** CH2.
- The phase difference is
$$\theta = 360^\circ \cdot \Delta t / T$$
$$= 360^\circ \cdot \frac{0.4 \text{ div}}{5 \text{ div}}$$
$$\Rightarrow \theta = 28.8^\circ$$
- If CH1 has  $x(t) = X_m \cos(\omega t)$ , then CH2 has  $y(t) = Y_m \cos(\omega t - \theta)$ , where *the minus sign preceding  $\theta$  indicates that  $y(t)$  lags  $x(t)$  by  $\theta$ .*
- In other words, if  $y(t) = Y_m \cos(\omega t)$ , then  $x(t) = X_m \cos(\omega t + \theta)$ , where the plus sign indicates that  $x(t)$  leads.



# Phase Measurements—The Lissajous Pattern Method


- Let  $x(t) = X_m \cos(\omega t + \theta)$  be applied to CH1 and  $y(t) = Y_m \cos(\omega t)$  to CH2.
- When the oscilloscope is in *XY mode*, it will display the position of the points  $(x, y)$  in the  $XY$  plane for all  $t$ .
- Curves such as the one to the right will be displayed.
- In the figure,

$$A = 2Y_m |\sin \theta|$$

$$B = 2Y_m$$

- By measuring  $A$  and  $B$ , we find
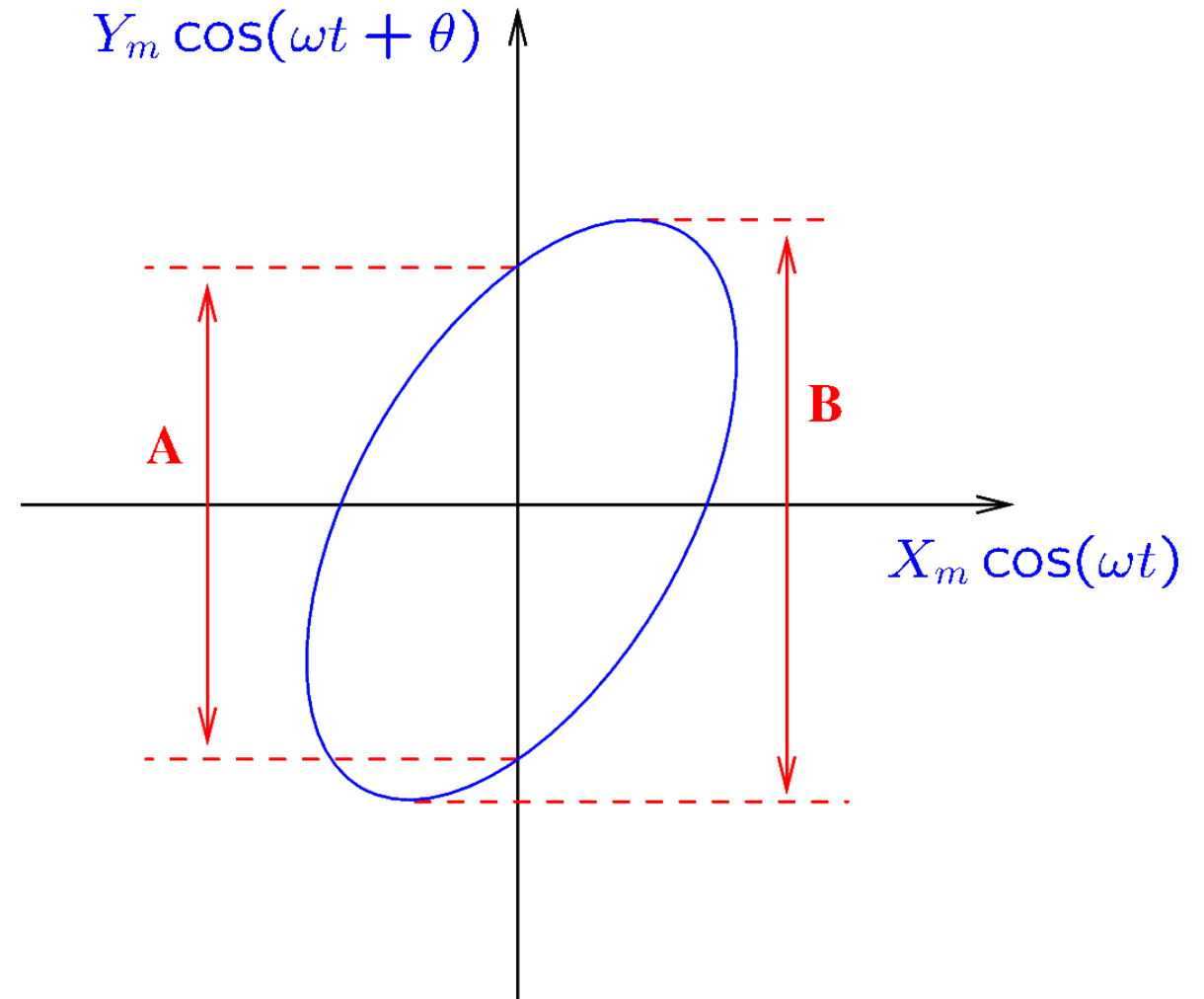
$$\theta = \pm \sin^{-1} \left( \frac{A}{B} \right)$$




# Phase Measurements—The Lissajous Pattern Method

- By measuring  $A$  and  $B$ , we find

$$\theta = \pm \sin^{-1} \left( \frac{A}{B} \right)$$


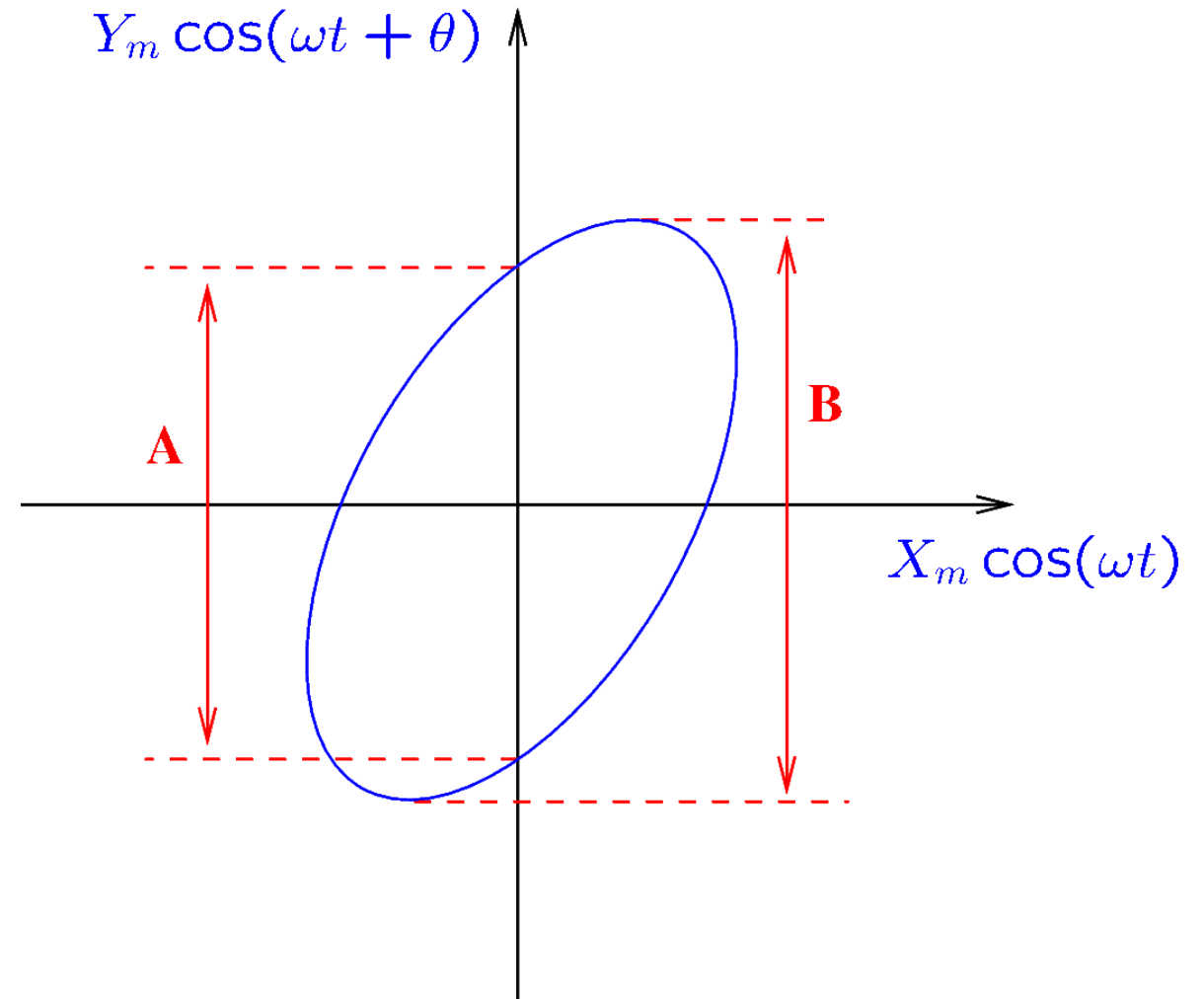
- The curve by itself does not indicate whether  $x(t)$  leads or lags  $y(t)$ .
- It can be verified that if  $\theta > 0$  the points  $(x, y)$  move clockwise along the curve, but counterclockwise if  $\theta < 0$ .
- If  $\theta = 0$  the signals are in phase and the curve becomes a straight line.




Grounding
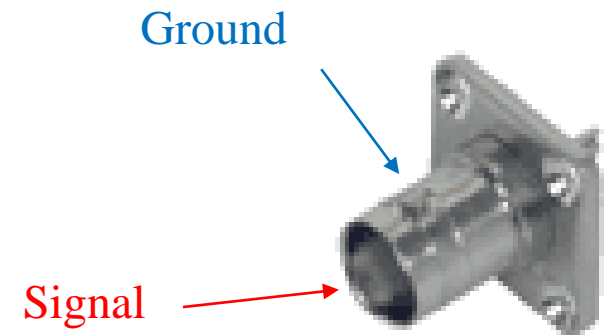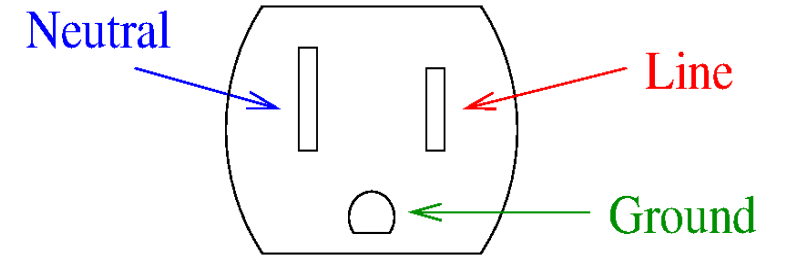
# Grounding

- Various instruments generate or measure voltage with respect to earth ground.
- They are connected to earth ground by means of the ground terminal of the wall outlet.
- Circuits connected to earth ground are said to be *grounded*.
- Circuits that are not connected to earth ground are said to be *floating*.
- For example, the oscilloscope and some waveform generators are grounded.
- The BNC connectors of a grounded instrument will have the shield connected to ground.




# Grounding

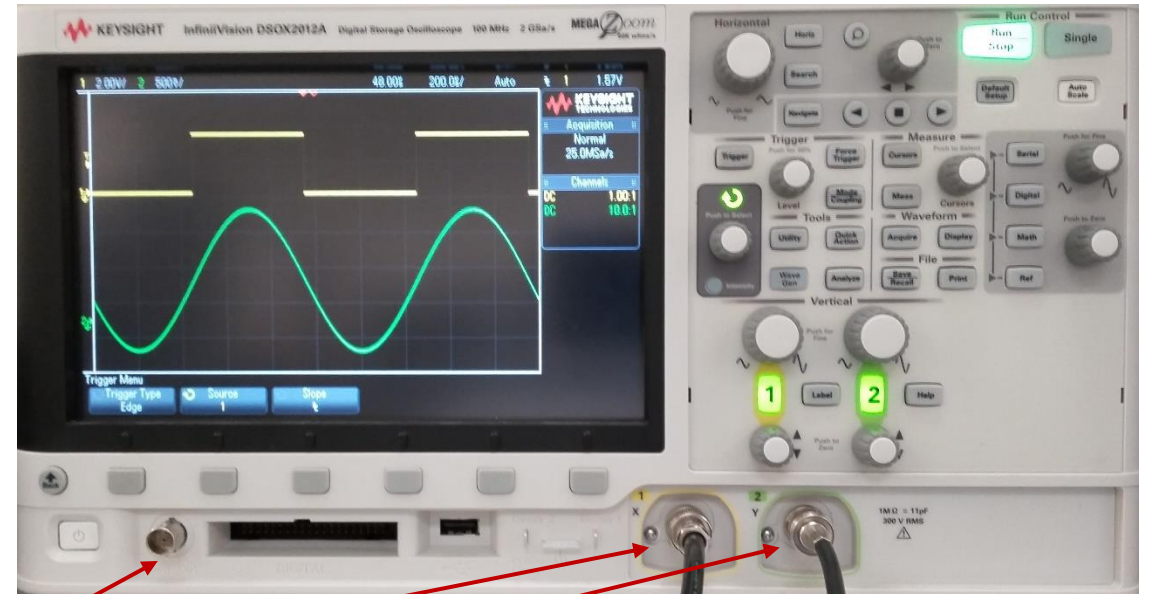


earth ground

- As soon as a grounded instrument is plugged into the wall outlet, the shield of its BNC connectors becomes earth ground.
- Floating instruments do not connect input or output terminals to earth ground.
- For example, any battery powered instrument is floating; some waveform generators are floating; DMMs and DC power supplies are floating.

# Grounding

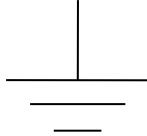
- Floating instruments also have a common point of reference, called ground, though this ground is not connected to earth ground.
- The shield of the BNC connectors is normally connected to the ground reference.
- When a floating instrument is connected to a grounded instrument, the ground references will also be connected, and thus the ground of the floating instrument will become earth ground.
- *Since multiple instrument terminals are connected to the same ground reference, an inadequate connection of the instruments to a circuit may result in short-circuits!*
- The ground is abbreviated GND and has the symbol 

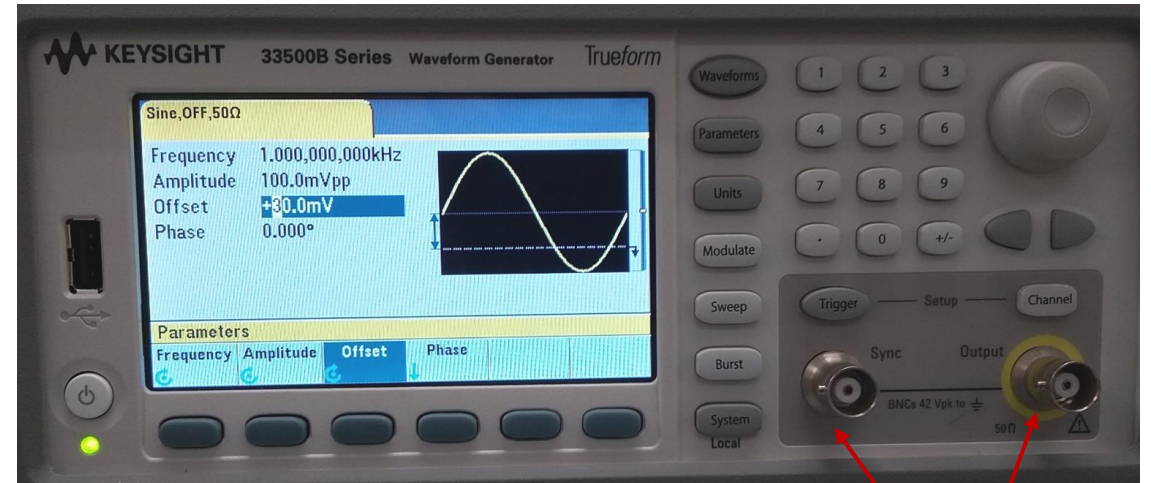

ground reference

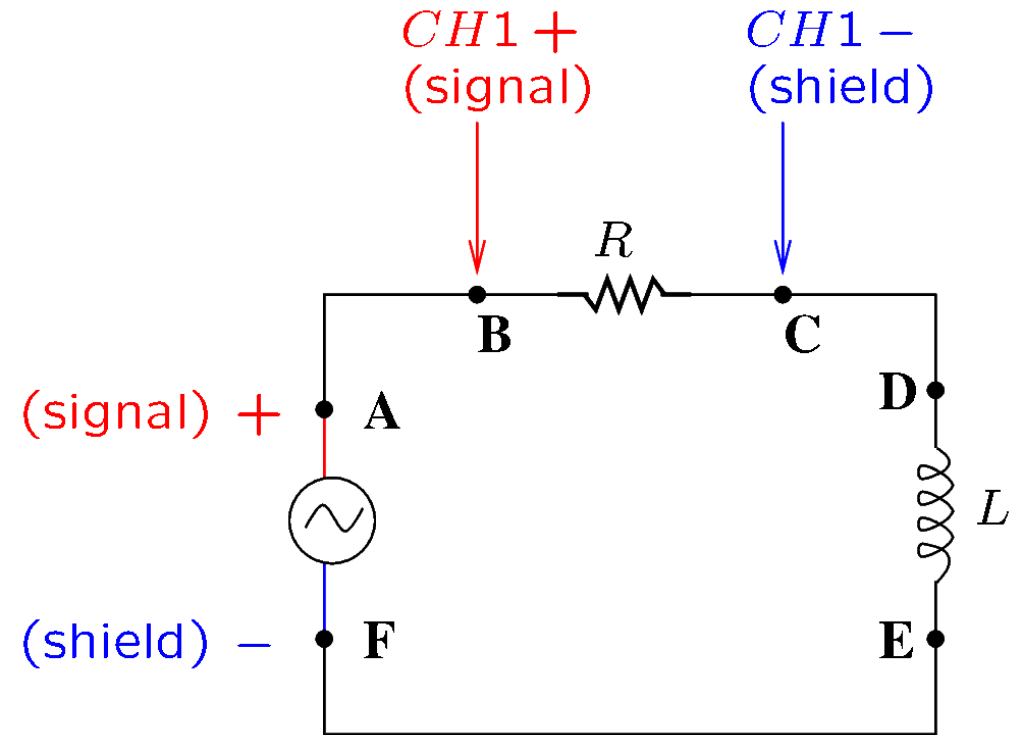
# Example 1

- The circuit consists of a resistor  $R$ , an inductor  $L$ , and a waveform generator connected between the points **A** and **F**.
- Channel 1 of the oscilloscope is connected to the circuit as shown in the figure.
- Both the oscilloscope and the waveform generator are grounded.
- The waveform generator outputs 5 V peak-to-peak.
- What voltage will the oscilloscope measure?
- Are the instruments connected correctly?



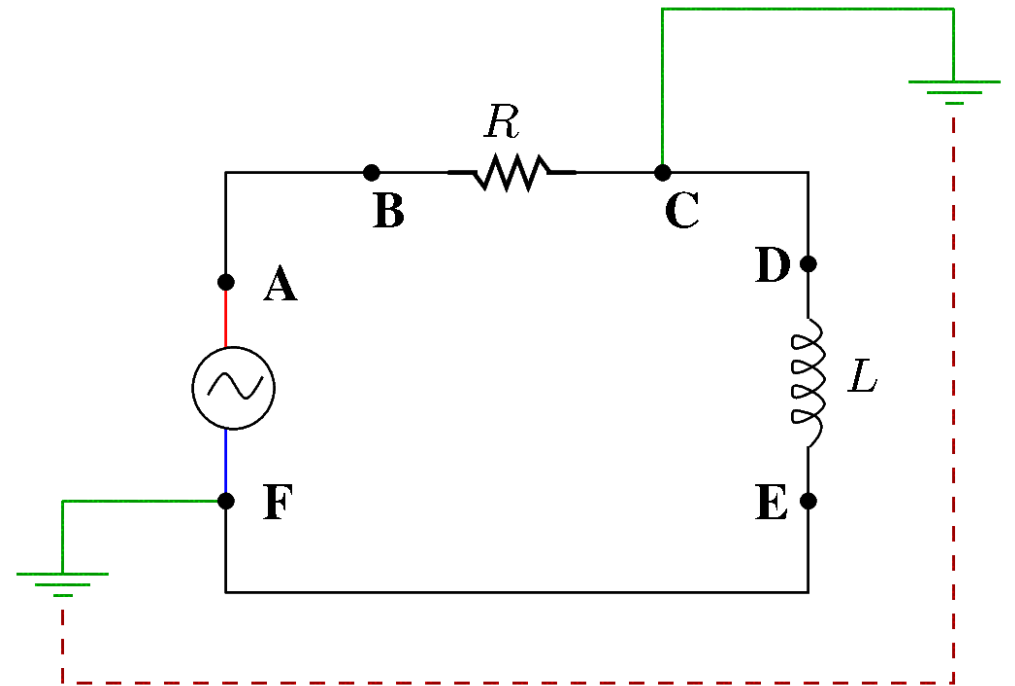
# Example 1—Solution

- *Since both instruments are grounded, the shield is connected to earth ground for both instruments:*
  - *Point F is connected to the GND terminal of the wall outlet of the waveform generator.*
  - *Point C is connected to the GND terminal of the wall outlet of the oscilloscope.*
  - *The GND terminals of the wall outlets are connected together to the same GND.*
  - *Therefore, points C and F are connected!*
- *Therefore, the inductor is short-circuited.*
- *Therefore, the entire voltage of the source will be on the resistor.*
- *The oscilloscope will measure  $5 V_{pp}$ .*
- *The oscilloscope is connected incorrectly to the circuit because it short-circuits the inductor!*



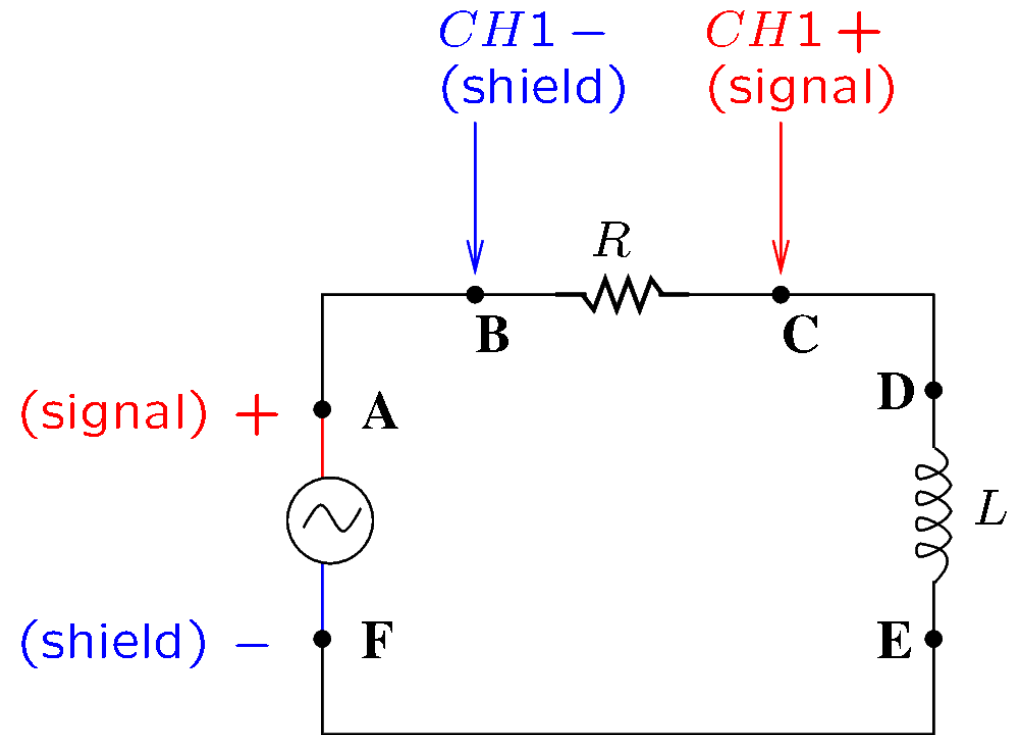
## Example 2

- Consider the previous circuit with the oscilloscope connections interchanged.
- What voltage will the oscilloscope measure?
- Are the instruments connected correctly?



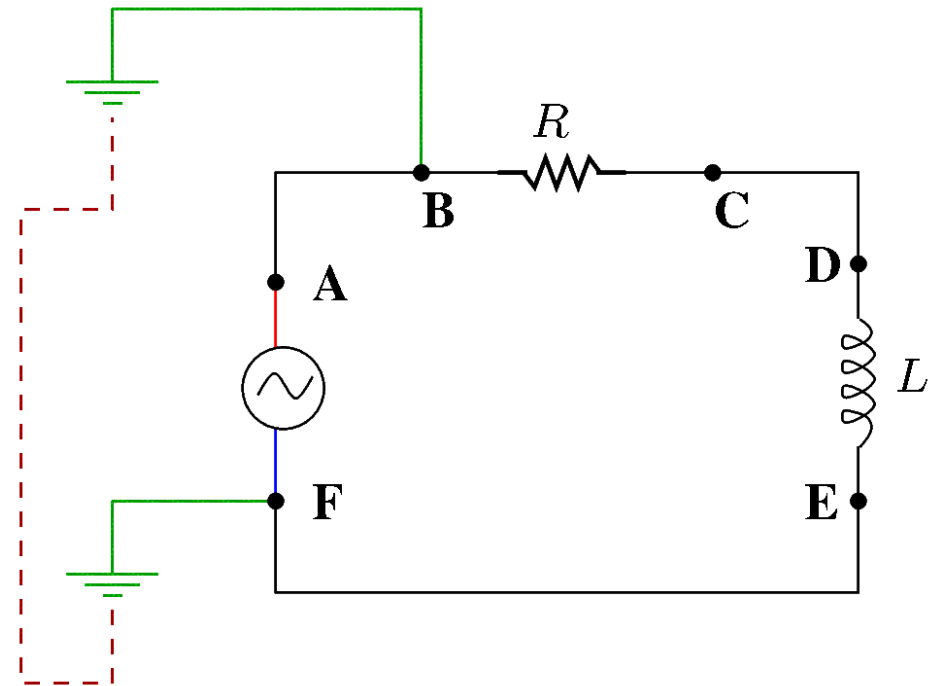
# Example 2—Solution

- *Since both instruments are grounded, the shield is connected to earth ground for both instruments:*
  - *Point F is connected to the GND terminal of the wall outlet of the waveform generator.*
  - *Point B is connected to the GND terminal of the wall outlet of the oscilloscope.*
  - *The GND terminals of the wall outlets are connected together to the same GND.*
  - *Therefore, points C and F are connected!*
- *Therefore, the waveform generator is short-circuited.*
- *Therefore, the circuit will not be powered.*
- *The oscilloscope will measure  $0 V_{pp}$ .*
- *The oscilloscope is connected incorrectly to the circuit because it short-circuits the waveform generator!*





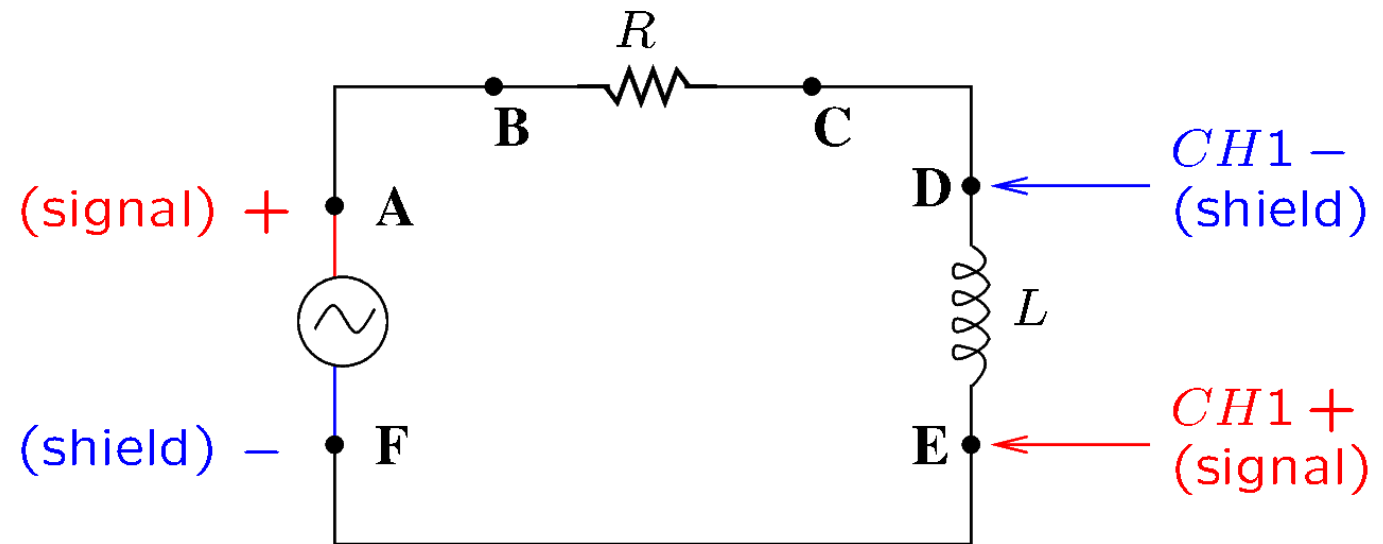
# Example 3

- Consider the previous circuit.
- Suppose that the voltage of  $L$  should be measured.
- Indicate whether the oscilloscope is connected correctly.
- If the oscilloscope is connected incorrectly, show how to connect it correctly.


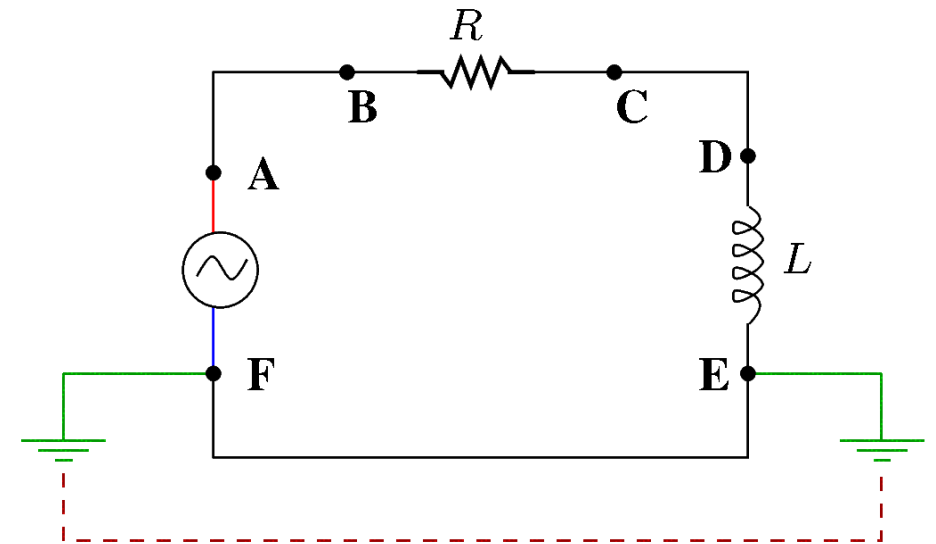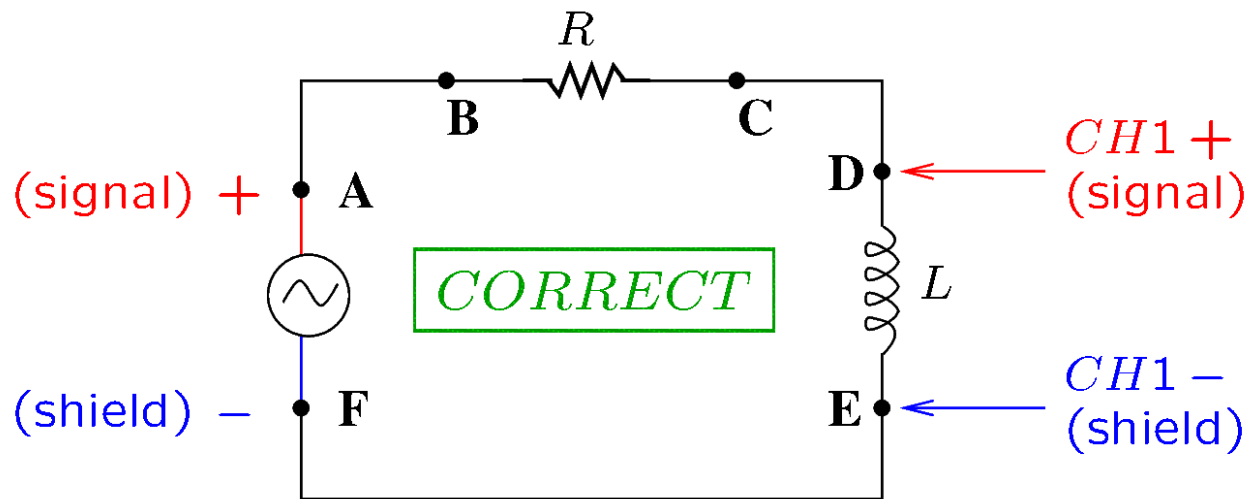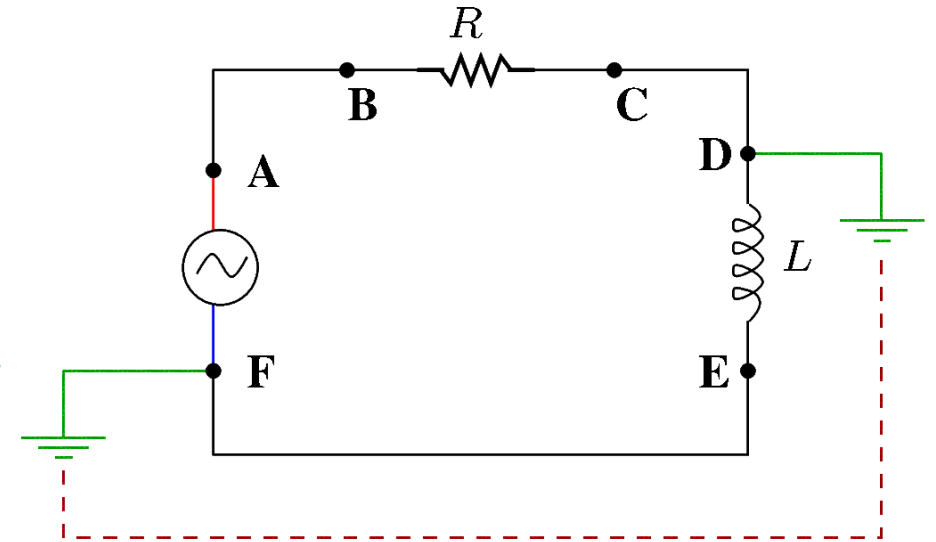
# Example 3—Solution

- *The oscilloscope is connected incorrectly, because it short-circuits  $L$ .*
- *By interchanging the connections of the oscilloscope, the voltage is measured correctly.*
- *The ground connection connects now two points of the circuit belonging to the same node, so there is no problem.*




# Example 4

Indicate how to measure correctly the voltage on  $R$  with the oscilloscope.



Several solutions are possible:

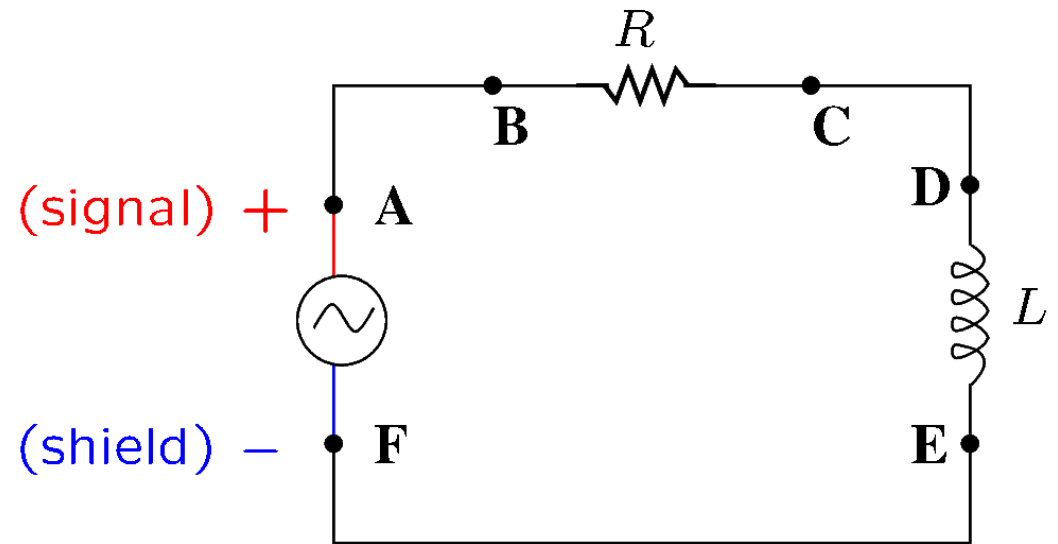- Method 1: Interchange connections of waveform generator.
- Method 2: Reorder series components so that  $R$  has a terminal connected to the GND of the source.
- Method 3: Perform a differential measurement.
- Method 4: Use a ground adapter.
- Method 5: Isolate the source from the circuit with a transformer.



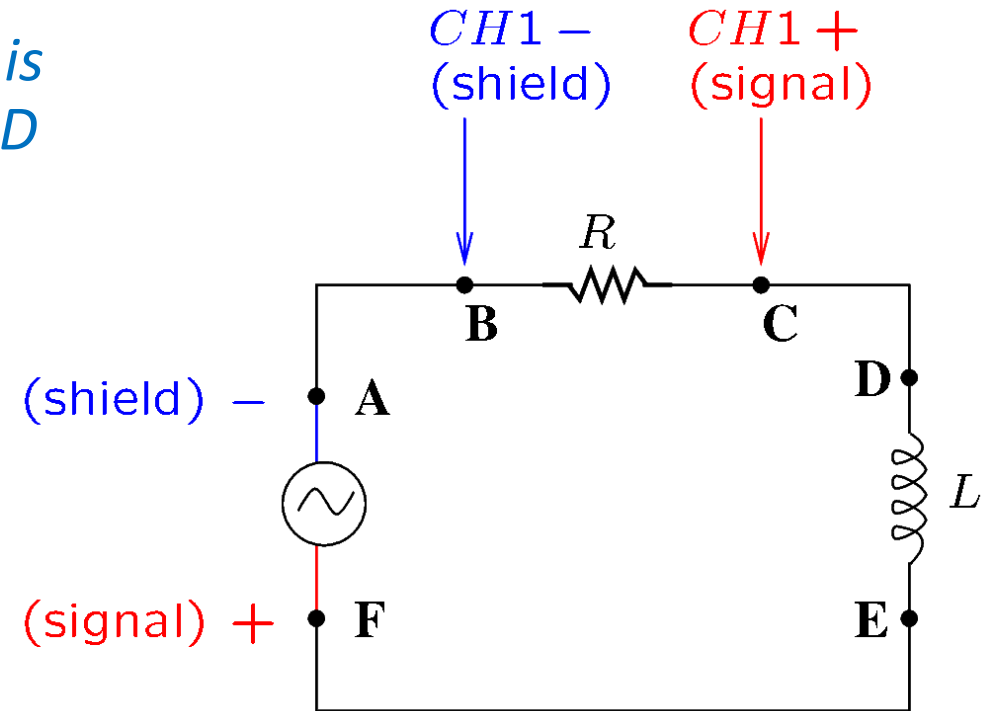
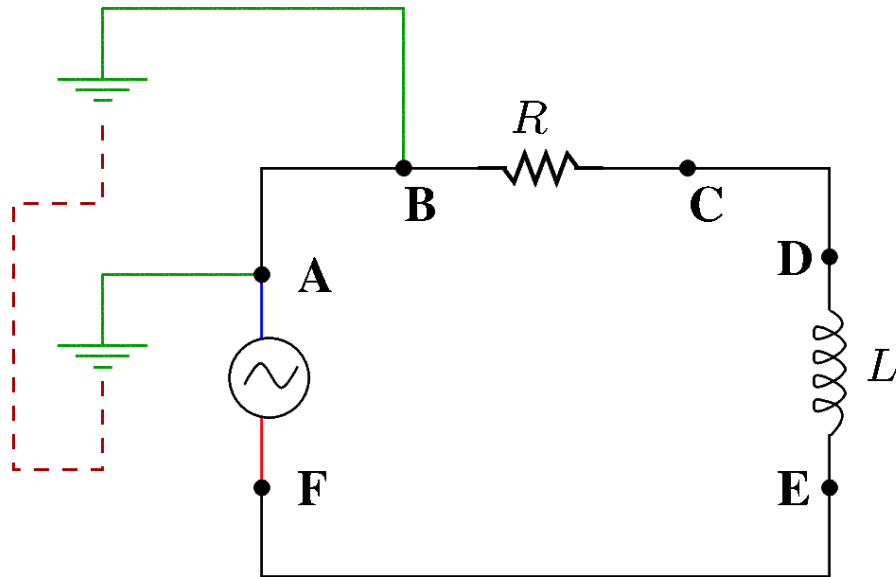
# Solution 1—Interchange Source Connections

- After interchanging the source connection, it is possible to connect the shield of CH1 (the GND terminal) at the point **B**.
- The ground connection connects now two points of the circuit belonging to the same node, so there is no problem.


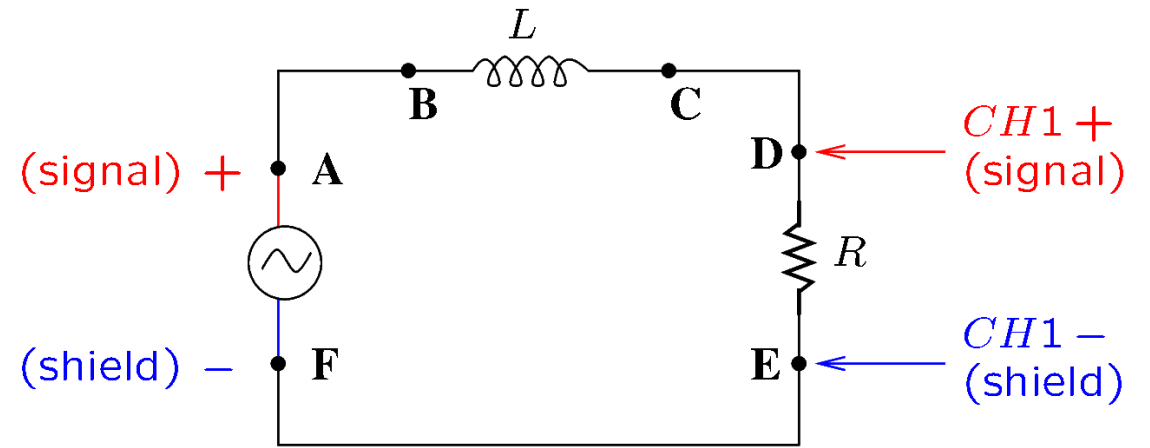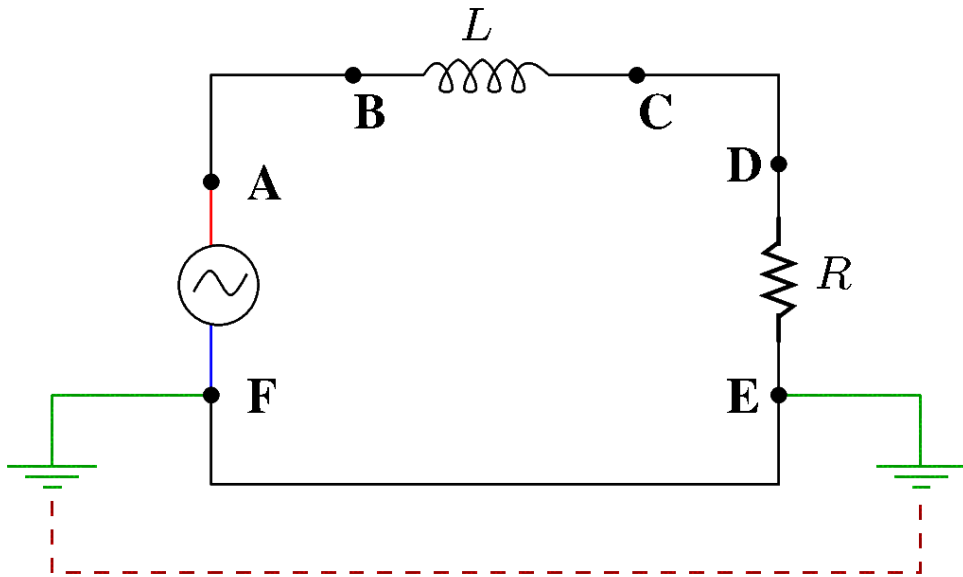
# Solution 2—Interchange $R$ and $L$

- After interchanging  $R$  and  $L$ , the voltage between the points  $D$  and  $E$  is the voltage of  $R$ .
- The ground connection connects now two points of the circuit belonging to the same node, so there is no problem.



# Other Solutions

- *Perform a differential measurement.*
  - *Measure on CH1 the source voltage.*
  - *Measure on CH2 the voltage on the inductor  $L$ .*
  - *Display on the oscilloscope the difference  $CH1 - CH2$ .*
  - *Drawback: The resolution of  $CH1 - CH2$  might be an issue if the difference is small.*
- *Use a three-prong/two-prong adapter.*
  - *This adapter could be used to disconnect the source or the oscilloscope from the GND of the wall outlet.*
  - *This method is unsafe and is not recommended.*
- *Use a transformer to isolate the source from the circuit.*
  - *Transformers will be discussed later in our class.*

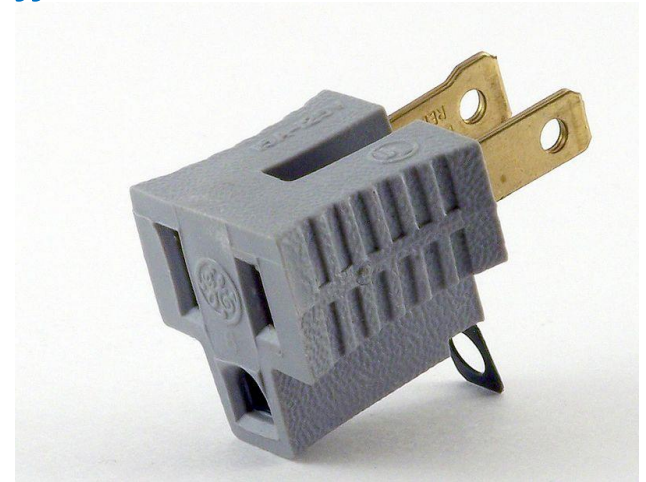


Image from [https://en.wikipedia.org/wiki/File:Cheater\\_plug\\_edited.jpg](https://en.wikipedia.org/wiki/File:Cheater_plug_edited.jpg)