

Data Acquisition Systems

Analog to Digital Converters, Digital to Analog Converters, Operational Amplifiers

M.V. Iordache, *EEGR2051 Circuits and Measurements Lab*, Fall 2020, LeTourneau University
See <https://mviordache.name/EEGR2051> for more information.

Interfacing Analog and Digital Systems

- A *multifunction I/O device*, such as PCIe-6321 inside the lab computers, can
 - Digitize analog signals from the physical world and transmit them to computer software (such as LabVIEW).
 - Convert software-generated digital signals to physical analog signals.
- Some of the most important components needed to interface computers to the physical world are:
 - Analog to digital converters.
 - Digital to analog converters.
 - Electronic amplifiers.



PCIe-6321 from National Instruments

<https://www.ni.com/en-us/support/model.pcie-6321.html>


Number Representation

- The internal representation of numbers in digital systems is in base 2.
- Each digit of a base-two number is called *bit*.
- An n -bit base-2 number $b_{n-1}b_{n-2} \dots b_2b_1b_0$ corresponds in base 10 to a number

$$N = b_{n-1}2^{n-1} + b_{n-2}2^{n-2} + \dots + b_22^2 + b_12^1 + b_02^0$$

For example, to convert the base-2 number 1011 0011 to base 10:

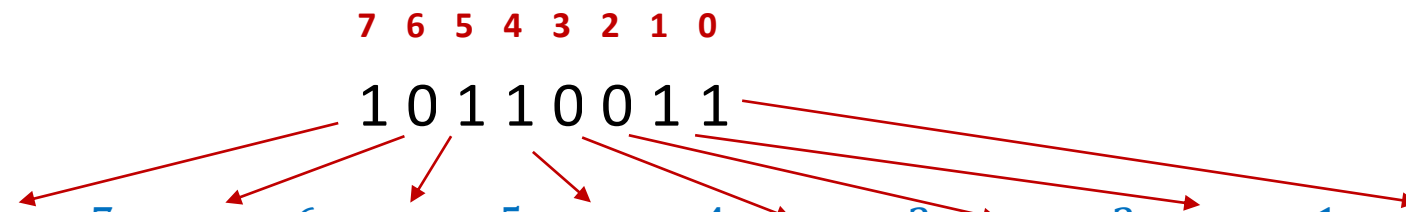- *Count the digits of the number from right to left, beginning with 0.*




- *Note that $N = 1 \cdot 2^7 + 0 \cdot 2^6 + 1 \cdot 2^5 + 1 \cdot 2^4 + 0 \cdot 2^3 + 0 \cdot 2^2 + 1 \cdot 2^1 + 1 \cdot 2^0$.*
- *The answer is $N = 179$.*

Number Representation

For example, let's write the number 138 in base 2:

- Note that $138 = 1 \cdot 2^7 + 0 \cdot 2^6 + 0 \cdot 2^5 + 0 \cdot 2^4 + 1 \cdot 2^3 + 0 \cdot 2^2 + 1 \cdot 2^1 + 0 \cdot 2^0$.
- Therefore, the base-2 number is **1000 1010**.
- The decomposition into a sum of powers of 2 could be obtained by successive divisions by 2 and by reading the remainders in reverse order:


$138 \div 2 = 69$ with remainder of 0	$\Rightarrow b_0 = 0.$	
$69 \div 2 = 34$ with remainder of 1	$\Rightarrow b_1 = 1.$	
$34 \div 2 = 17$ with remainder of 0	$\Rightarrow b_2 = 0.$	
$17 \div 2 = 8$ with remainder of 1	$\Rightarrow b_3 = 1.$	
$8 \div 2 = 4$ with remainder of 0	$\Rightarrow b_4 = 0.$	
$4 \div 2 = 2$ with remainder of 0	$\Rightarrow b_5 = 0.$	
$2 \div 2 = 1$ with remainder of 0	$\Rightarrow b_6 = 0.$	
$1 \div 2 = 0$ with remainder of 1	$\Rightarrow b_7 = 1.$	

Number Representation

Consider a base-2 number.

- The *most significant bit (msb)* is the first bit.

1001 0010

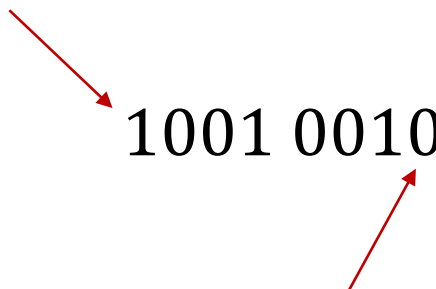The diagram shows the binary number '1001 0010' centered on the page. A red arrow originates from the text 'most significant bit (msb)' in the bullet point above and points to the first '1' of the number. Another red arrow originates from the text 'least significant bit (lsb)' in the bullet point below and points to the final '0' of the number.

- The last bit is the *least significant bit (lsb)*.

Digital to Analog Converters

- Digital instruments represent voltages with numbers.
- *Digital to Analog Converters (DACs)* convert numbers N to voltages.
- Given a number N , a DAC will output a voltage $V_o = V_{LO} + step \cdot N$ where
 - V_{LO} is the *low reference voltage*; typically, $V_{LO} = 0$.
 - $step$ is the *voltage resolution* of the converter, also known as *LSB*.
 - The voltage resolution is the amount by which the output voltage V changes when the least significant bit of N changes.
- If V_{HI} is the *high reference voltage* and the DAC works with m bit numbers, that is, m is the *bit resolution* of the DAC, then:

$$step = \frac{V_{HI} - V_{LO}}{2^m}$$

Examples

1) A DAC has a 20 mV voltage resolution. Assuming $V_{LO} = 0$, find the output voltage when the input is $N = 0110\ 0011$.


- In base 10, $N = 2^6 + 2^5 + 2^1 + 2^0 \Rightarrow N = 99$.
- Since $step = 20\text{ mV}$ and $V_o = V_{LO} + step \cdot N$, it follows that $V_o = 1.98\text{ V}$.

2) A 10-bit DAC has $V_{LO} = 0$ and $V_{HI} = 15\text{ V}$. Find N for which $V_o = 3.456\text{ V}$.

- Since $step = \frac{V_{HI} - V_{LO}}{2^m}$ and $m = 10$, it follows that $step = \frac{15}{2^{10}}\text{ V}$.
- Note that $3.456 = step \cdot N \Rightarrow N = 235.93$.
- Rounding to the nearest integer, $N = 236$.


Digital to Analog Converters

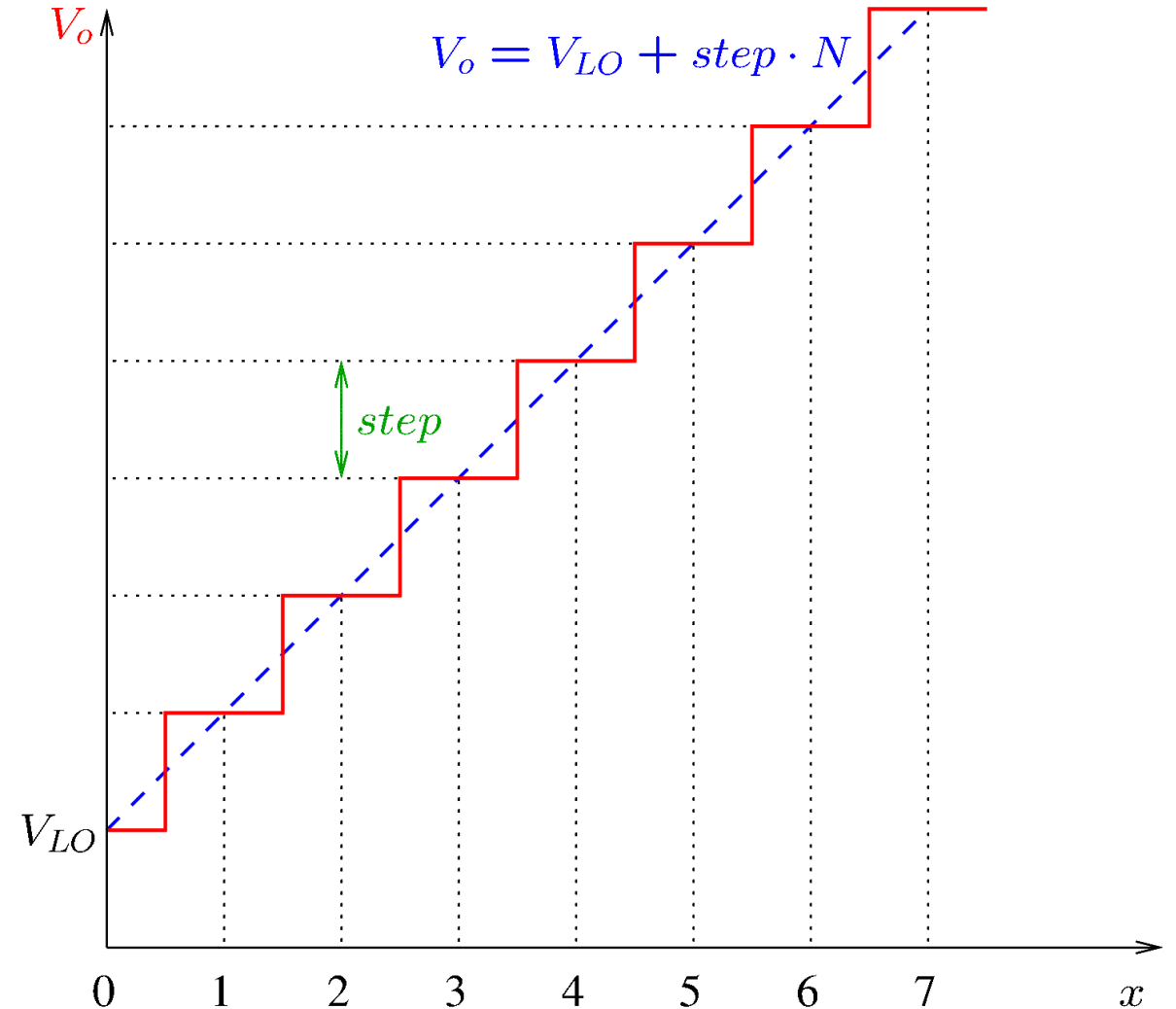- A signal $x(t)$, when applied to a DAC, will have its values rounded to the nearest integer N .
- Note that the output of the DAC will change in steps.



Digital to Analog Converters

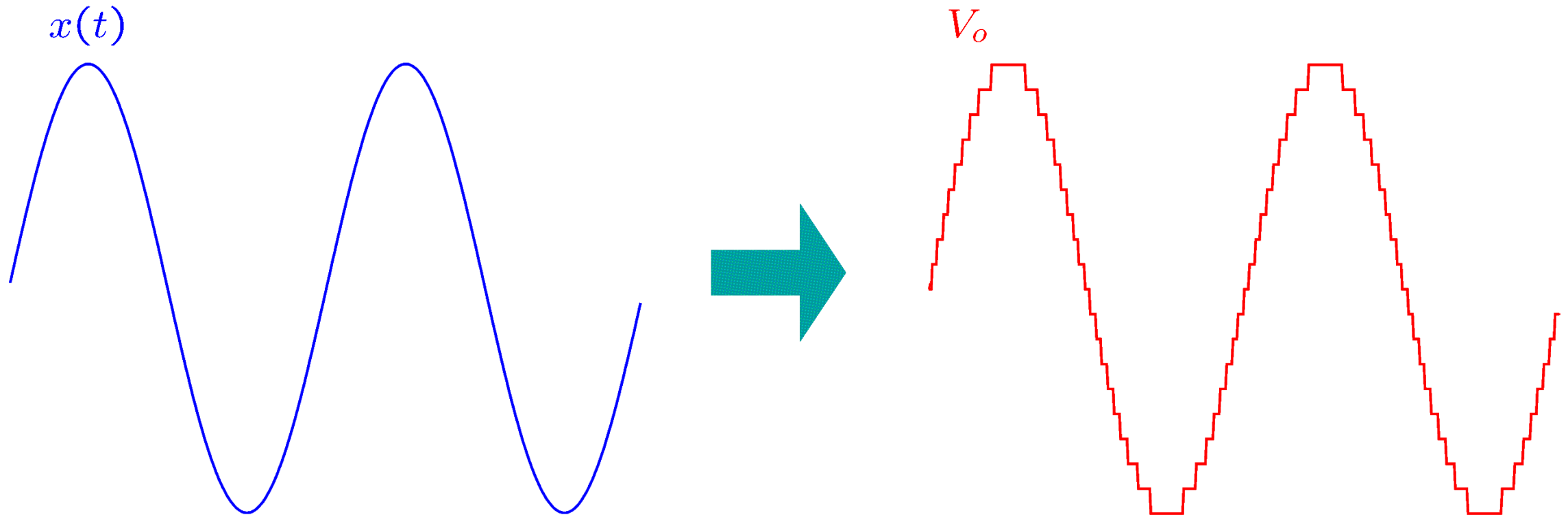- A signal $x(t)$, when applied to a DAC, will have its values rounded to the nearest integer N .
- Note that the output of the DAC will change in steps.



Analog to Digital Converters

- Digital to Analog Converters convert integer numbers to voltages.
- Analog to Digital Converters (ADCs) perform the converse operation, as they convert voltages to integer numbers.
- If an ADC outputs the number N , the input voltage V_{in} satisfies


$$V_{in} = V_{LO} + step \cdot N \pm \frac{step}{2}$$

- V_{LO} is the *low reference voltage*; typically, $V_{LO} = 0$.
- $step$ is the *voltage resolution* of the converter, also known as *LSB*.
- If V_{HI} is the *high reference voltage* and the DAC works with m bit numbers, that is, m is the *bit resolution* of the DAC, then:

$$step = \frac{V_{HI} - V_{LO}}{2^m}$$

Analog to Digital Converters

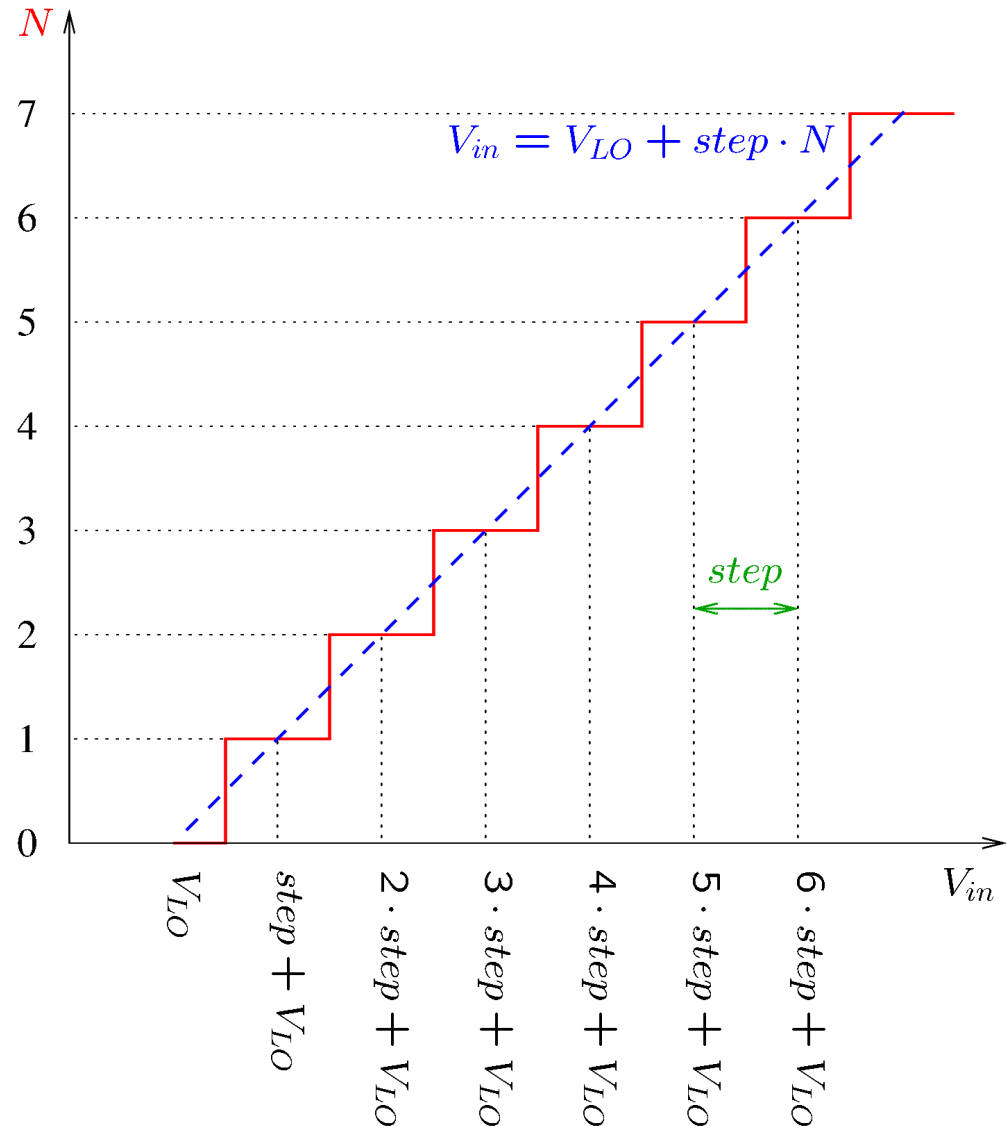
- The range of N is $0 \dots 2^m - 1$.
- As the graph shows, the equation $V_{in} = V_{LO} + step \cdot N$ predicts the input voltage V_{in} with an uncertainty of $\pm step/2$.
- $\pm step/2$ is the ideal uncertainty.
- A practical ADC has sources of error that make the uncertainty larger.



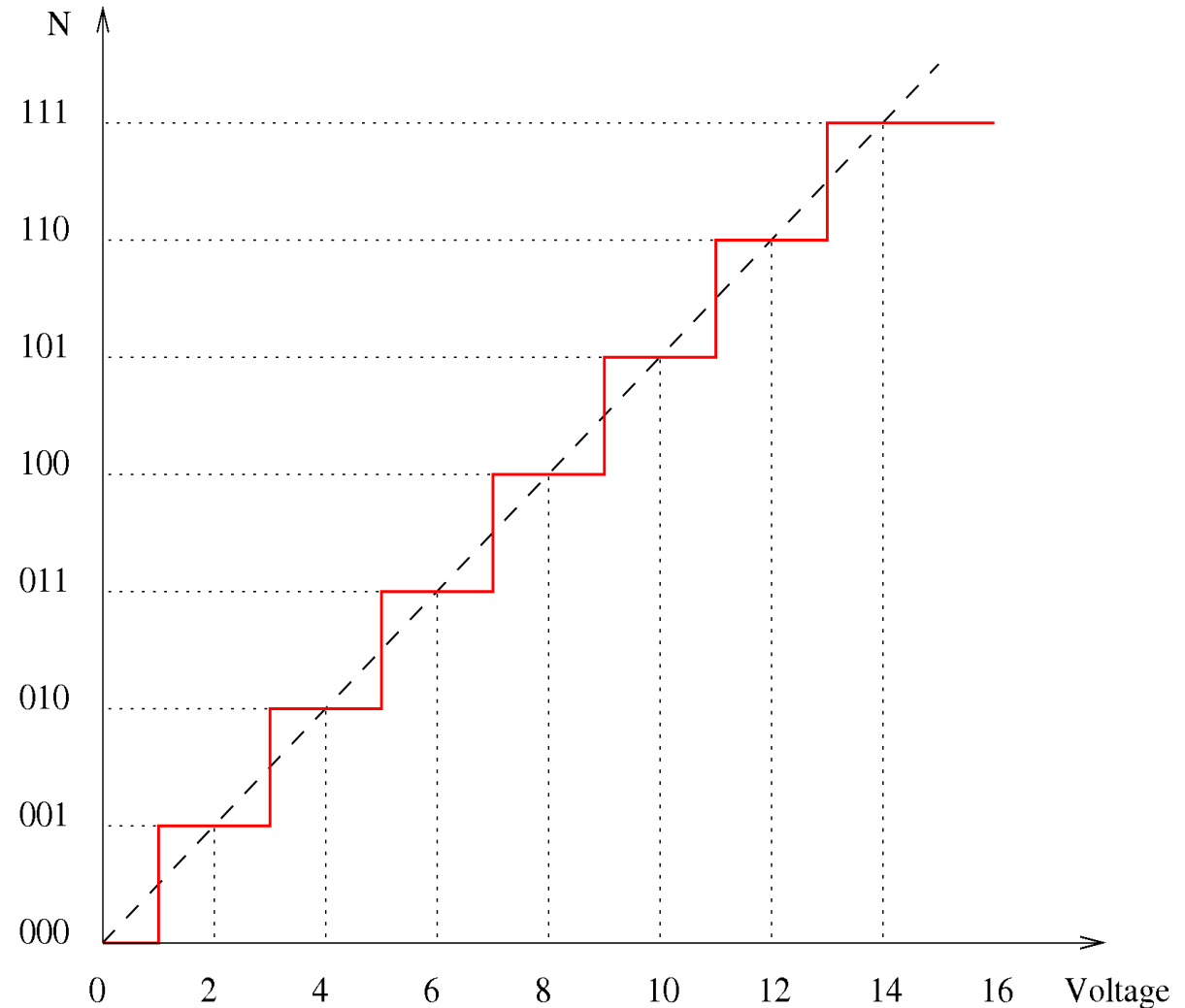Example

The ADC shown in the figure outputs the following base-2 numbers: 000, 001, 010, 011, 100, 101, 110, and 111. Find V_{LO} and V_{HI} .

- N has 3 digits in base 2, so $m = 3$.
- The line representing the equation $V_{in} = V_{LO} + step \cdot N$ goes through the origin, so $V_{LO} = 0$.
- The graph indicates that $step = 2 V$.
- From $step = \frac{V_{HI} - V_{LO}}{2^m}$ we derive $V_{HI} = 16 V$.



Examples

1) An 8-bit ADC has $V_{LO} = 0$ and $V_{HI} = 10$ V. What is V_{in} when $N = 20$?

- $step = \frac{V_{HI} - V_{LO}}{2^m} = 39.06$ mV.

- $V_{in} = V_{LO} + step \cdot N \pm \frac{step}{2} \Rightarrow V_{in} = 781.25 \pm 19.53$ mV.

2) Repeat the previous example assuming a 12-bit ADC.

- $step = \frac{V_{HI} - V_{LO}}{2^m} = 39.06$ mV.

- $V_{in} = V_{LO} + step \cdot N \pm \frac{step}{2} \Rightarrow V_{in} = 48.83 \pm 1.22$ mV.

Ideally, uncertainty decreases exponentially with the number of bits.

Differential Channels

- The voltage of a *single-ended channel* is measured with respect to GND.
- In a *differential channel*, voltage is measured with respect to an arbitrary reference.
- So far, we have considered ADCs with single-ended channels.
- ADCs are often used with differential channels, such as in the lab.
- With a differential channel, N may be positive or negative and is in the range $-2^{m-1} \dots 2^{m-1} - 1$.
- V_{in} also may be positive or negative; it can be calculated with

$$V_{in} = step \cdot N \pm \frac{step}{2}, \text{ where } step = \frac{V_{HI} - V_{LO}}{2^{m-1}}$$

- Note 2^{m-1} instead of 2^m in the previous formula.

The Nyquist Frequency

- Note that any signal can be decomposed into a sum of sinusoidal components, each with a different frequency.
- Consider an ADC that samples an input signal at the rate of f_s samples per second.
- If f_{max} is the maximum frequency of the signal components, then the input signal can be reconstructed correctly from its samples if

$$f_s \geq 2f_{max}$$

- $f_N = 2f_{max}$ is known as the *Nyquist frequency*.

Example

A 12-bit successive approximation ADC operates at a clock frequency $f = 5 \text{ MHz}$. What is the maximum frequency of the signal components for which the signal can be reconstructed correctly from its samples?

- Note that the conversion time of a successive approximation ADC is $T_c \simeq \frac{m}{f}$, where m is the number of bits.
- The maximum rate at which the ADC can sample the input is $f_{s,max} = \frac{1}{T_c}$.
- Sampled signals can be reconstructed correctly from their samples if $f_s \geq 2f_{max}$.
- We derive that $f_{max} \leq \frac{f_s}{2} \leq \frac{f_{s,max}}{2} \simeq \frac{f}{2m}$.
- Numerically, $f_{max} \leq 208.33 \text{ kHz}$.

Electronic Amplifiers

- Amplifiers are used to increase the voltage or power of an input signal.
- If V_{out} is the amplitude of the output signal and V_{in} the amplitude of the input signal, then the voltage gain of the amplifier is

$$A = \frac{V_{out}}{V_{in}}$$

- The decibel gain of the amplifier is


$$A_{dB} = 20 \cdot \log_{10} \frac{V_{out}}{V_{in}}$$

Example: A 3 mV peak-to-peak signal is applied to a 40 dB amplifier. What is the peak-to-peak amplitude of the amplifier output?

$$40 \text{ dB} = 20 \cdot \log_{10} \frac{V_{out}}{3 \text{ mV}} \Rightarrow V_{out} = 300 \text{ mV peak-to-peak.}$$



Operational Amplifiers

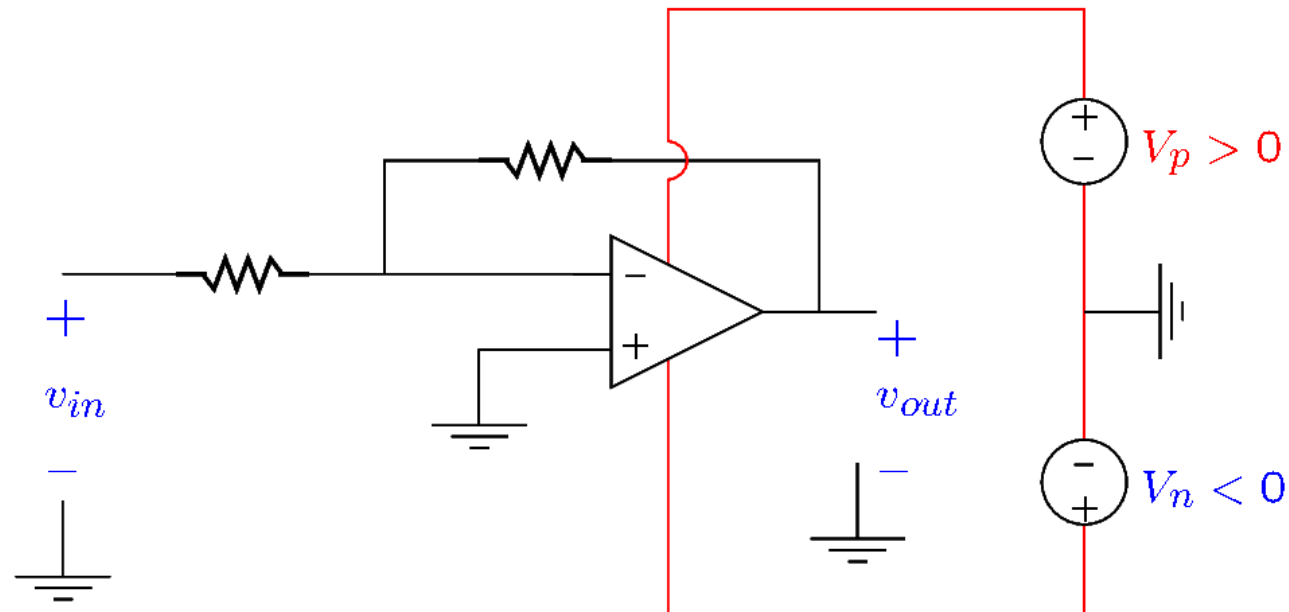- The figure shows an amplifier circuit that uses an operational amplifier.
- Operational amplifiers are commonly used to amplify signals.
- They have pins for the input and output signals (shown in black) and supply pins (shown in red) used to power the operational amplifier.



Operational Amplifiers

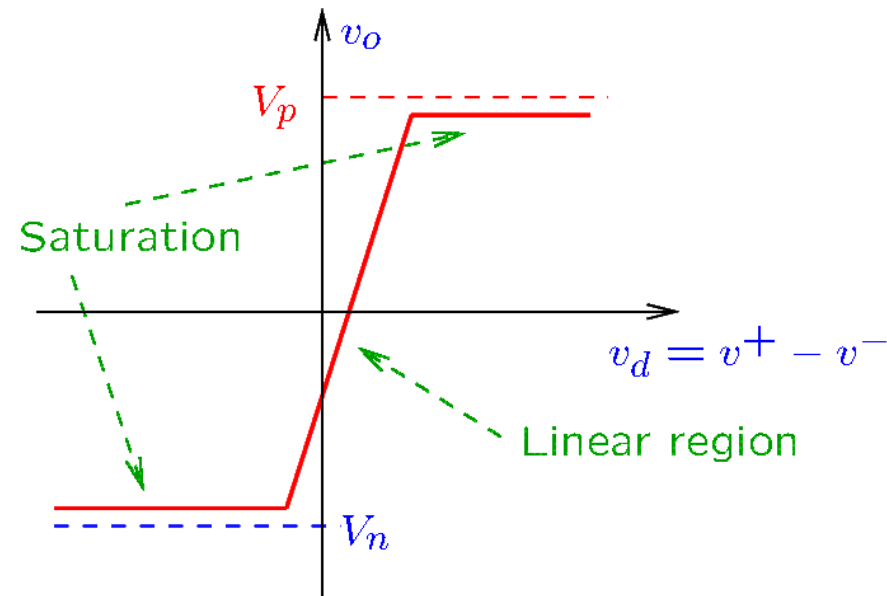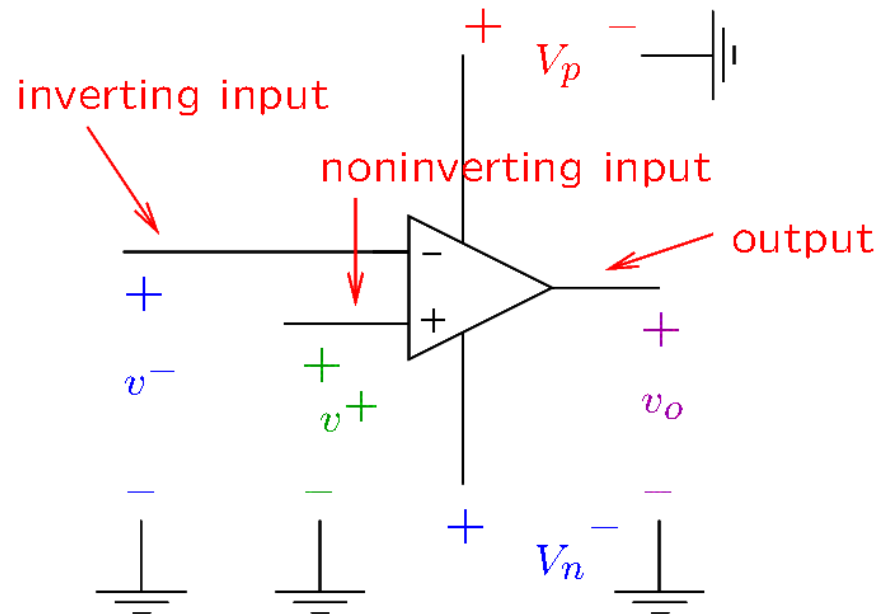- Let v^+ be the *noninverting input* voltage and v^- the *inverting input* voltage.
- Let V_p be the voltage on the positive supply pin and V_n the voltage on the negative supply pin.
- In *saturation*, the output voltage is $v_o \simeq V_p$ or $v_o \simeq V_n$.
- In the *linear region*, $v_o \simeq A(v^+ - v^-)$, where A is the operational amplifier **gain**.



Operational Amplifiers


- Because the gain A is typically very large:

$$v^+ \simeq v^- \text{ in the linear region.}$$


- The input currents are normally negligible:

$$i^+ \simeq i^- \simeq 0.$$

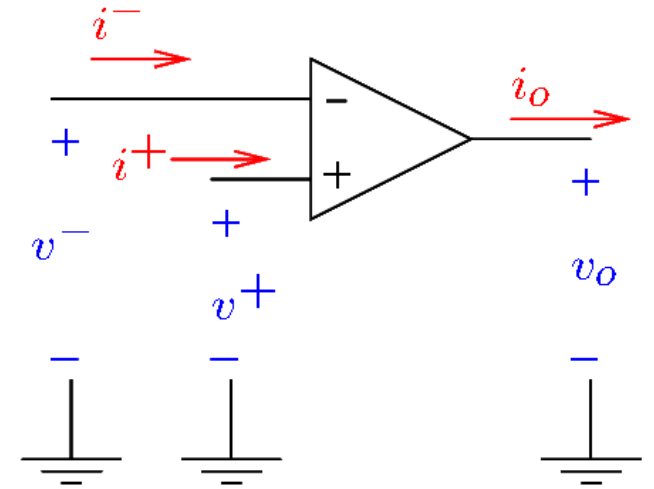- The equations $v^+ = v^-$ and $i^+ = i^- = 0$ can be used to solve operational amplifier circuits.





The Noninverting Amplifier

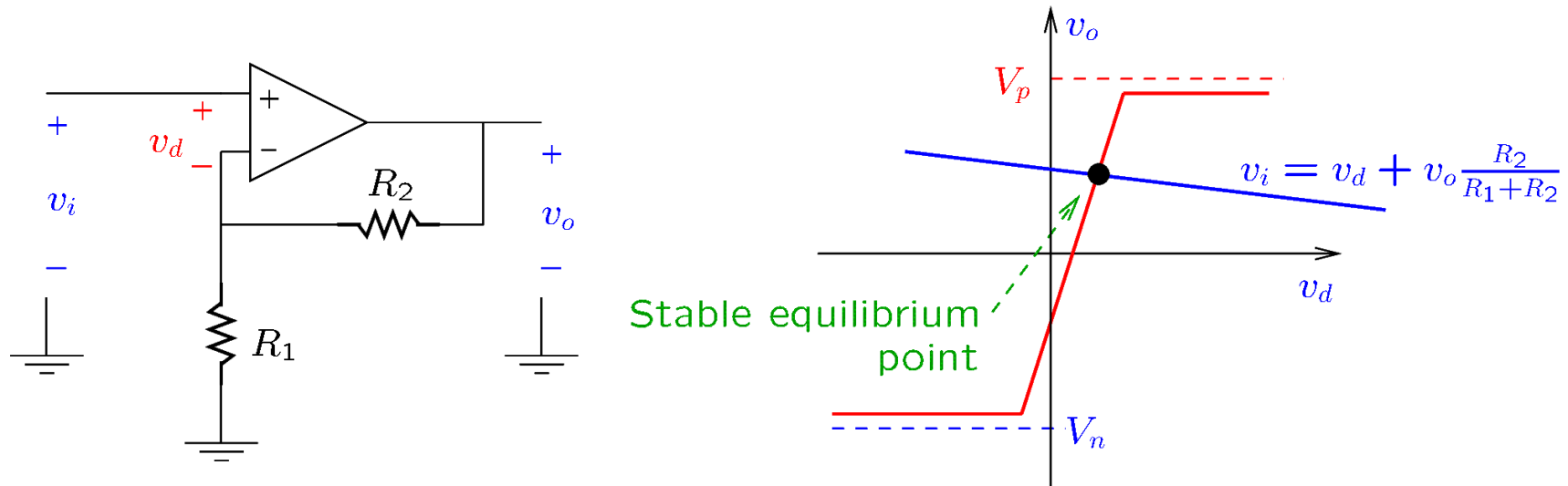

- Operational amplifiers are normally used with *feedback*.
- A feedback network connects the output of the amplifier to the input so as to ensure that the operational amplifier works in the linear region.
- In the figure, the resistor R_2 connects the output of the amplifier to the inverting input, creating in this way feedback.
- The circuit shown in the figure is known as the *noninverting amplifier*.

The Noninverting Amplifier

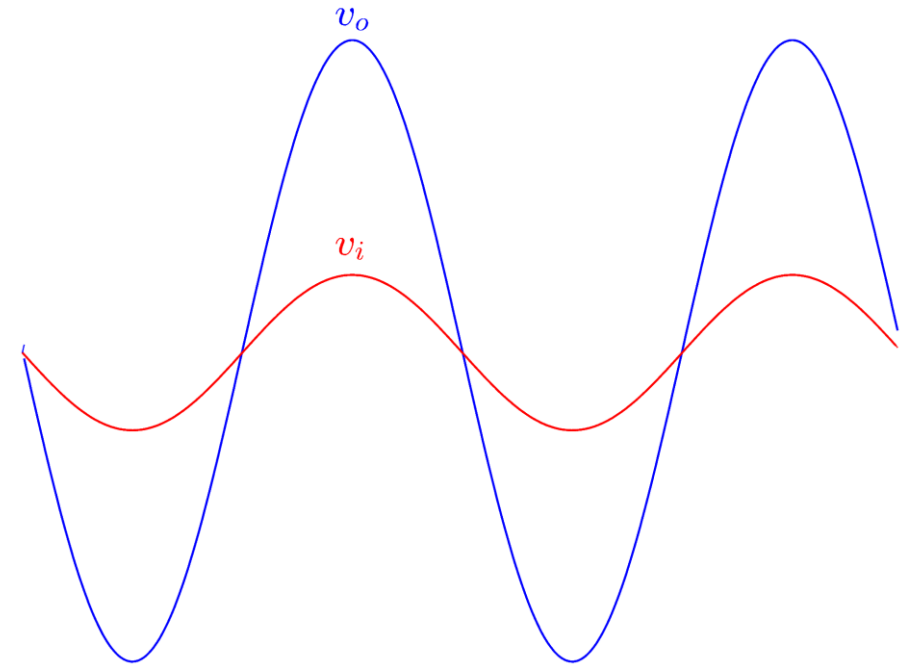
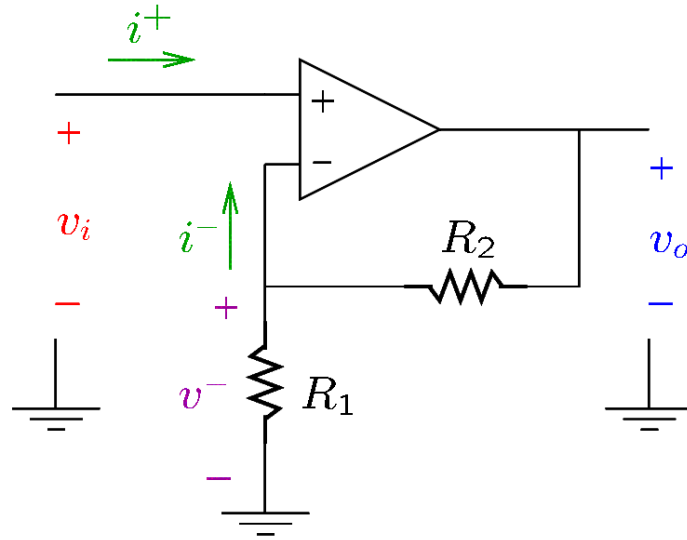


- The gain of the noninverting amplifier is

$$\frac{v_o}{v_i} = 1 + \frac{R_2}{R_1}$$



- The formula can be easily proven:
 - Note that $v^+ = v_i$.
 - $i^- = 0 \Rightarrow v^- = v_o \frac{R_1}{R_1 + R_2}$
 - $v^+ = v^- \Rightarrow v_i = v_o \frac{R_1}{R_1 + R_2}$, from which the gain formula follows.

The Inverting Amplifier

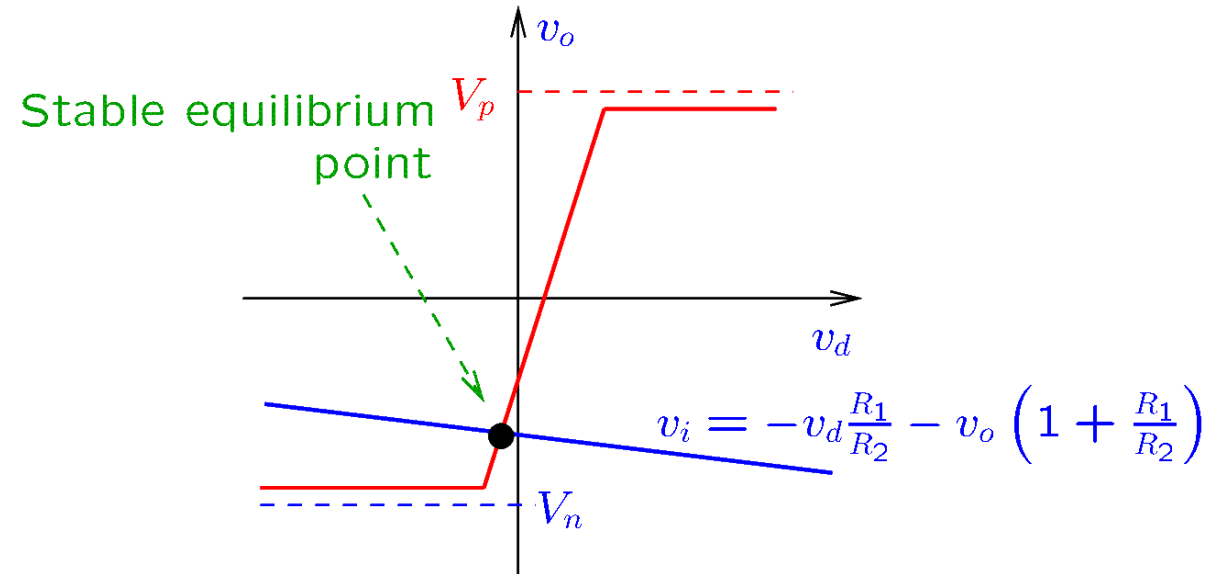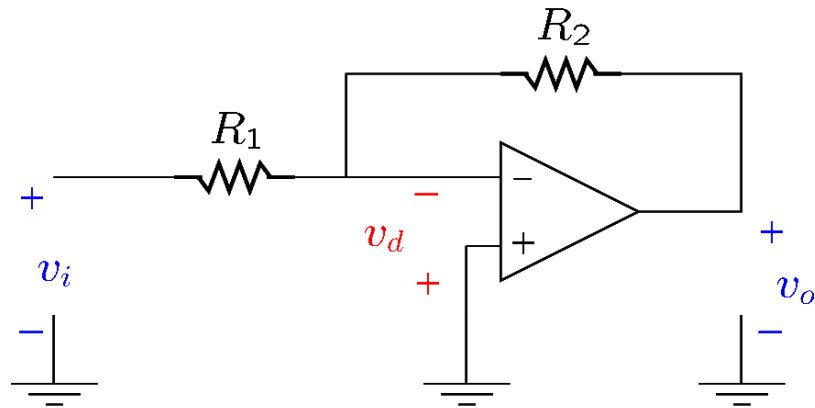

- In the figure, the resistor R_2 connects the output of the amplifier to the inverting input, creating in this way feedback.
- This feedback ensures that the operational amplifier works in the linear region.
- The circuit shown in the figure is known as the *inverting amplifier*.

The Inverting Amplifier

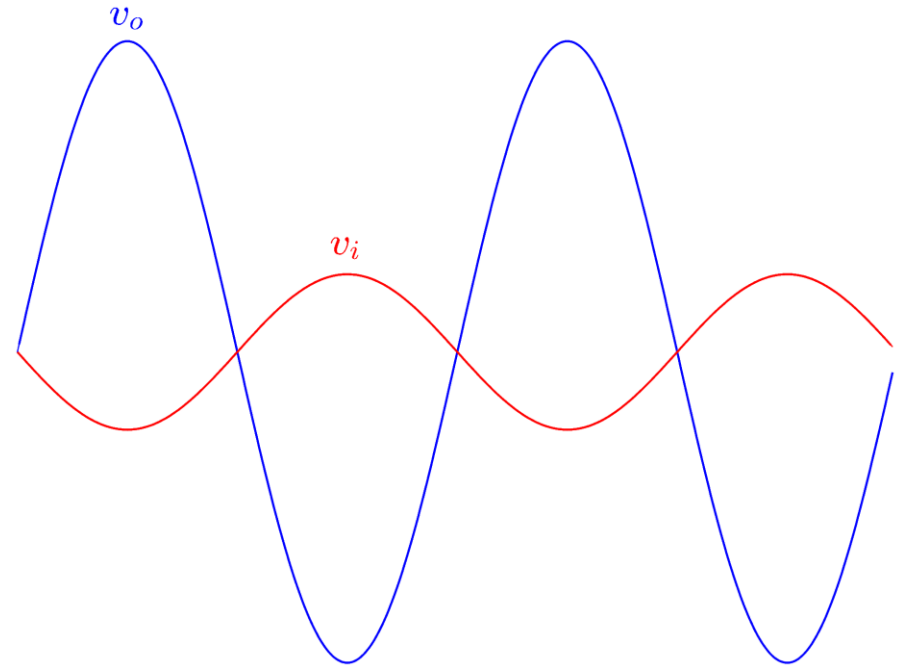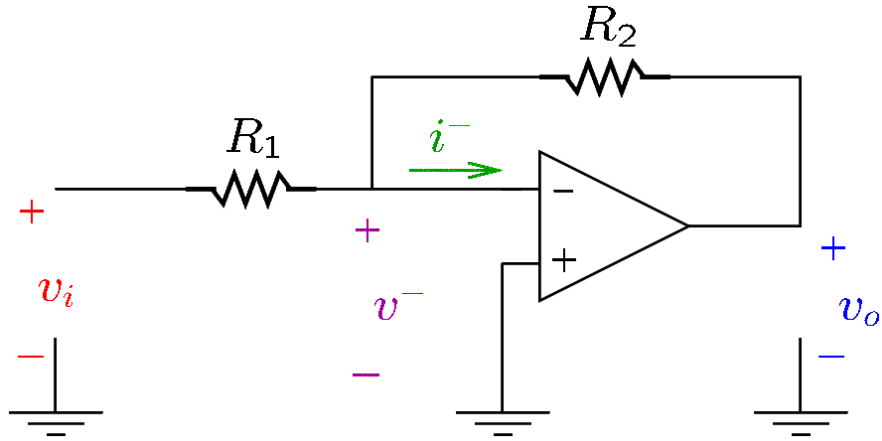

- The gain of the inverting amplifier is



$$\frac{v_o}{v_i} = -\frac{R_2}{R_1}$$

- The formula can be easily proven:

- The nodal equation is $\frac{v_i - v^-}{R_1} + \frac{v_o - v^-}{R_2} = i^-$.

- The gain formula follows immediately by substituting $i^- = 0$ and $v^- = v^+ = 0$.

The Voltage Follower

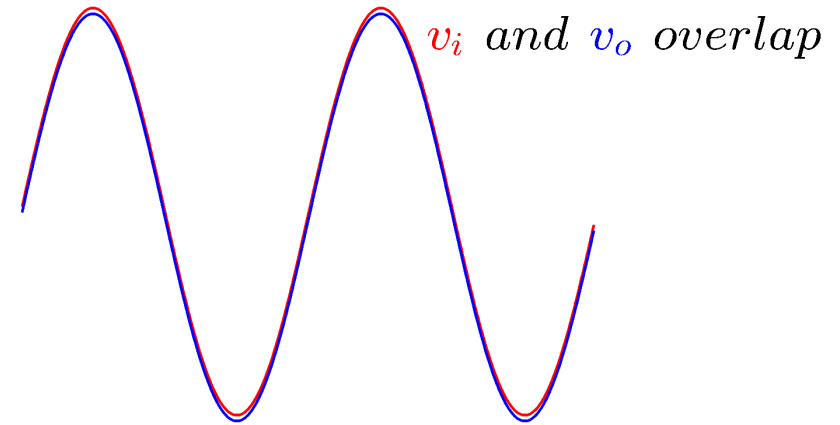
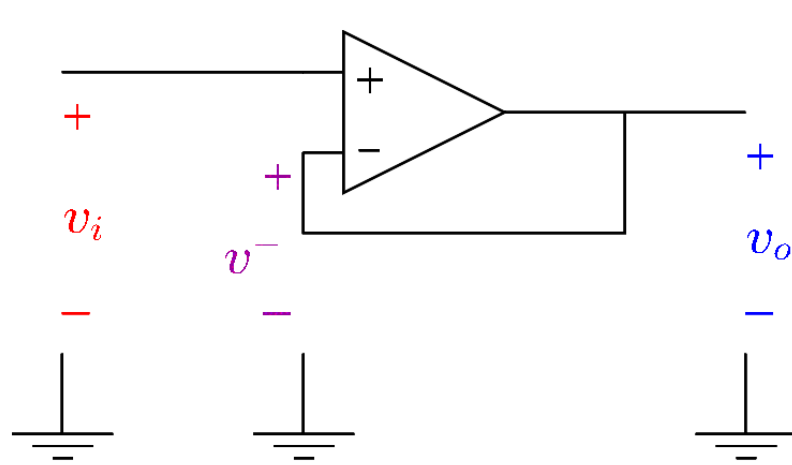


- Feedback ensures that the operational amplifier is in the linear region.
- The circuit shown in the figure is known as a *voltage follower*.
- The voltage follower has the gain

$$\frac{v_o}{v_i} = 1$$

- It has a negligible input current, while delivering the required output current.
- The voltage gain formula can be easily proven:
 - $v_i = v^+$, $v^+ = v^-$, and $v^- = v_o$ imply $v_o = v_i$.

Voltage Comparator

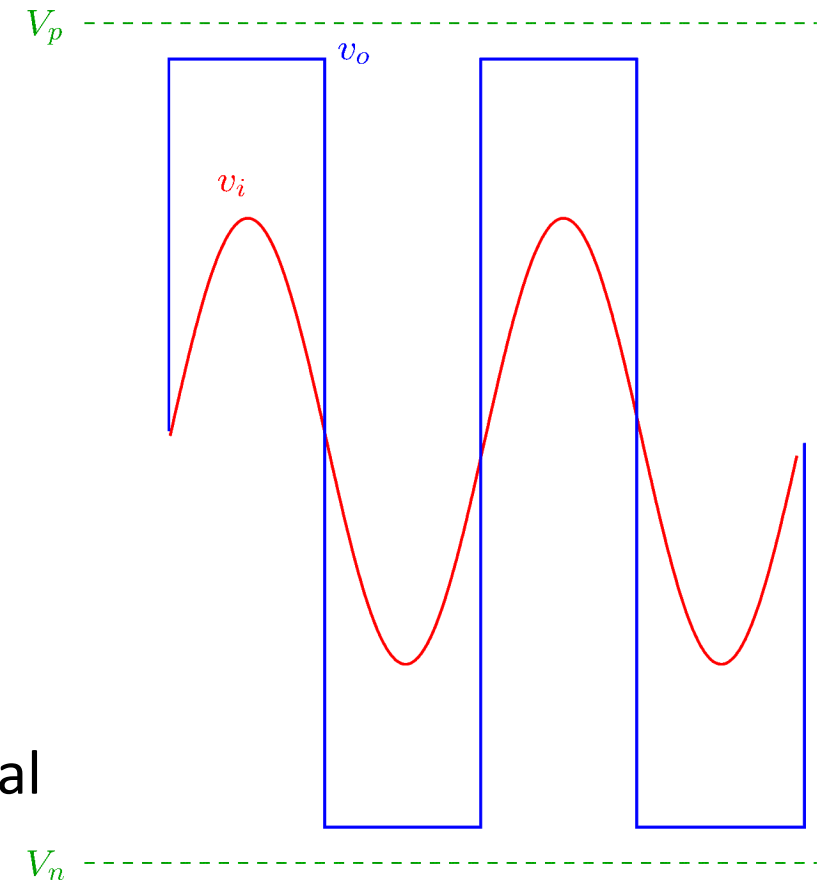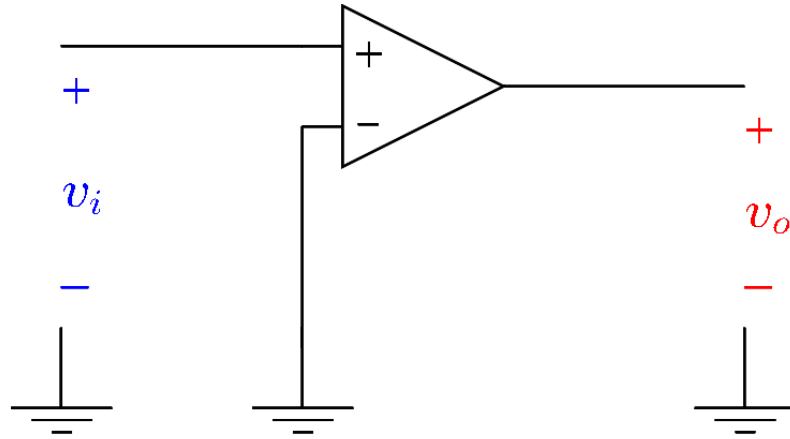

- Since there is no feedback, the operational amplifier will be saturated.
- Let V_p be the positive supply voltage of the operational amplifier and V_n the negative supply voltage.
- If $v_i > 0$, the operational amplifier will output maximum voltage; $v_o \simeq V_p$.
- If $v_i < 0$, the operational amplifier will output the most negative voltage; $v_o \simeq V_n$.
- The circuit compares the voltage of the noninverting input to the voltage of the inverting input and outputs V_p if the former is larger and V_n if smaller.