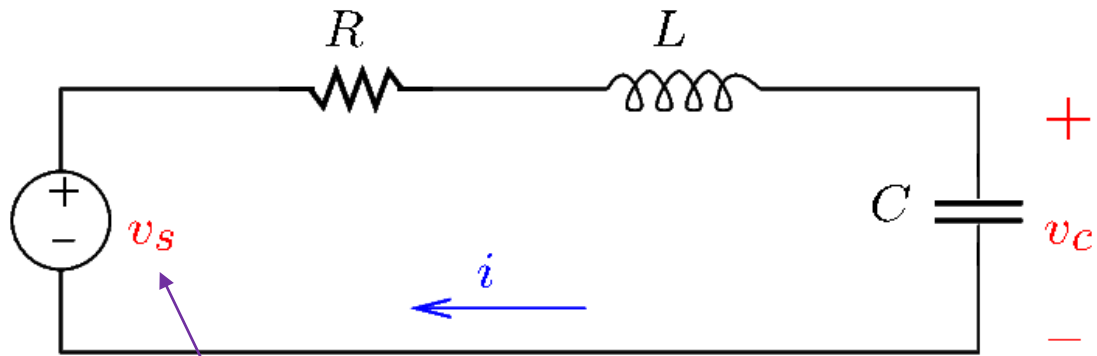



Phasors

Representing Sinusoidal Voltages and Currents in the Frequency Domain

Introduction



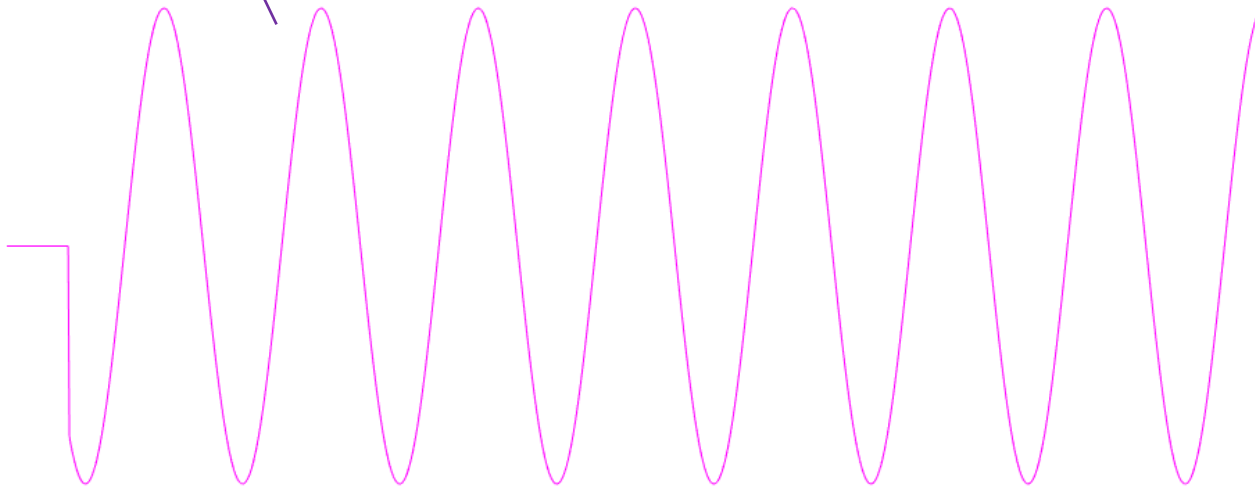
- Suppose that a sinusoidal voltage $v_s(t)$ is applied at time t_0 .
- Any voltage or current could be found by solving a system of *differential equations*.
- For example, $v_c(t)$ is found by solving the system of equations:



$$i = C \frac{dv_c}{dt}$$
$$iR + L \frac{di}{dt} + v_c = v_s$$


Introduction

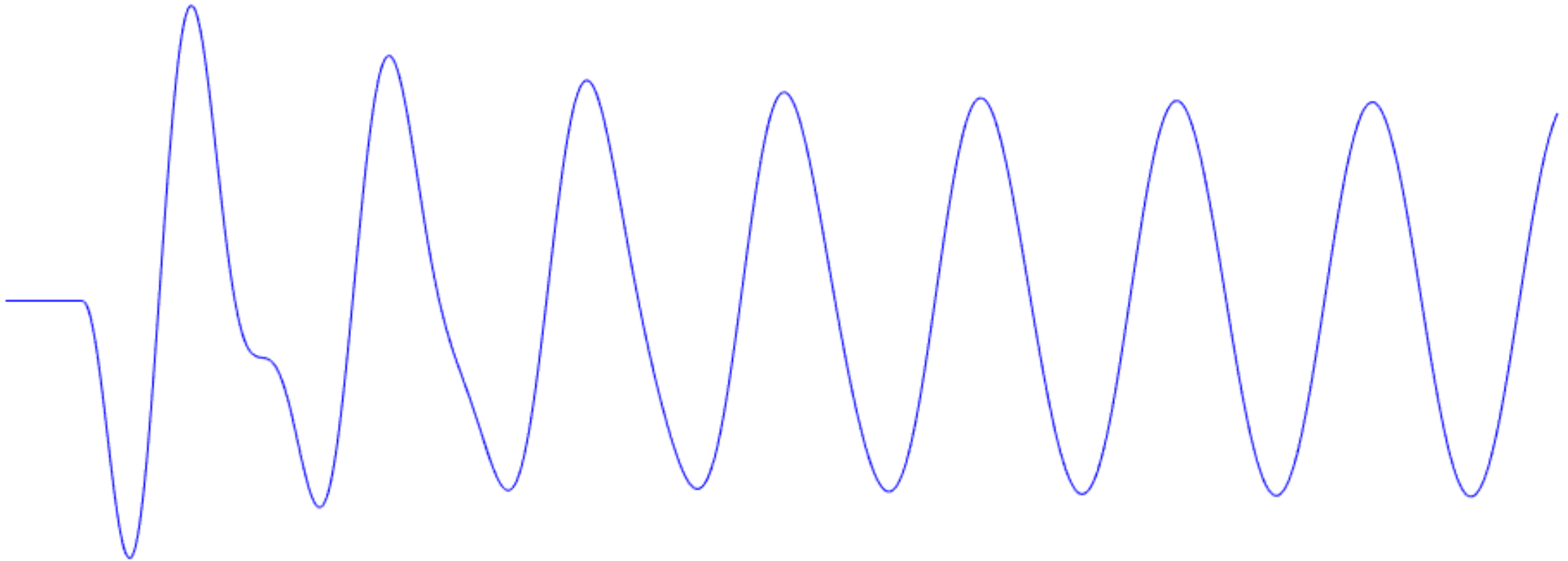By solving the differential equations, we obtain $v_c(t)$ having the following graph.



Introduction

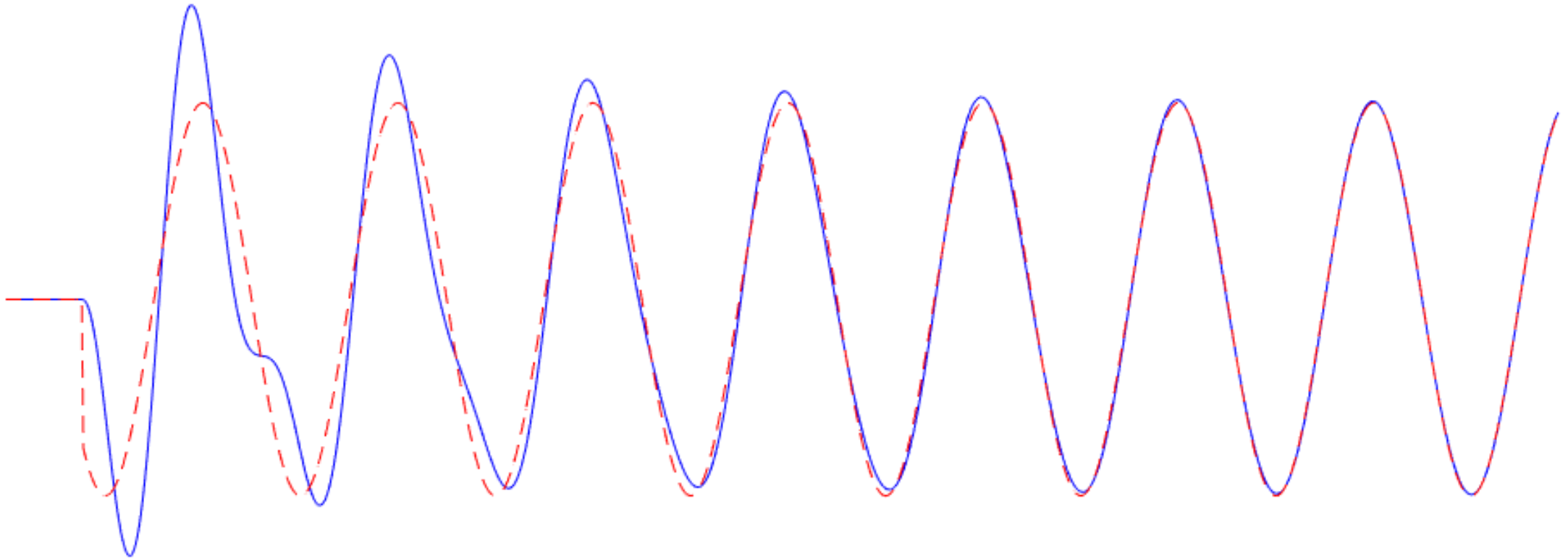- Note that $v_c(t)$ converges to the red curve.
- The red curve is called *steady-state response*.



Introduction

- Often, we do not care about transients, but we only need the steady-state.
- The steady-state response can be obtained without solving differential equations.
- To find the steady-state response, we will use this simpler method:
 - Convert the circuit to the **frequency domain**.
 - Solve for the unknowns in the frequency domain.
 - Convert the unknowns back to the **time domain**.

The Frequency Domain

- Up to this point we have worked in the *time domain*.
- Let $m(t) = M \cos(\omega t + \alpha)$ be a current or a voltage.
- We say that $m(t)$ is in the *time-domain*.
- The **frequency domain** representation of $m(t)$ is the complex-valued function

$$M(t) = M e^{i(\omega t + \alpha)}$$

- Note that $M e^{i(\omega t + \alpha)}$ is the complex number of magnitude M and angle $\omega t + \alpha$.
- We also write $M e^{i(\omega t + \alpha)}$ as $M \angle \omega t + \alpha$.

Example:

$$10 \angle 30^\circ = 10 e^{i30^\circ} = 10 \cos 30^\circ + i 10 \sin 30^\circ = 5\sqrt{3} + i5.$$

The Frequency Domain—Notation

- Note that $i = 1\angle 90^\circ = \sqrt{-1}$ is the unit vector in the direction of the imaginary axis.
- From now on, to avoid confusion with currents, j will be used in the place of i .
- So $j = 1\angle 90^\circ = \sqrt{-1}$.

Example: $h = 3 + 4j$ is the complex number of real part 3 and imaginary part 4.


That is, $Real(h) = 3$ and $Imag(h) = 4$.

In the complex plane, h is represented by

a vector of length $|h| = \sqrt{3^2 + 4^2} = 5$,

at an angle $arg(h) = \tan^{-1} \frac{4}{3} = 53.13^\circ$.

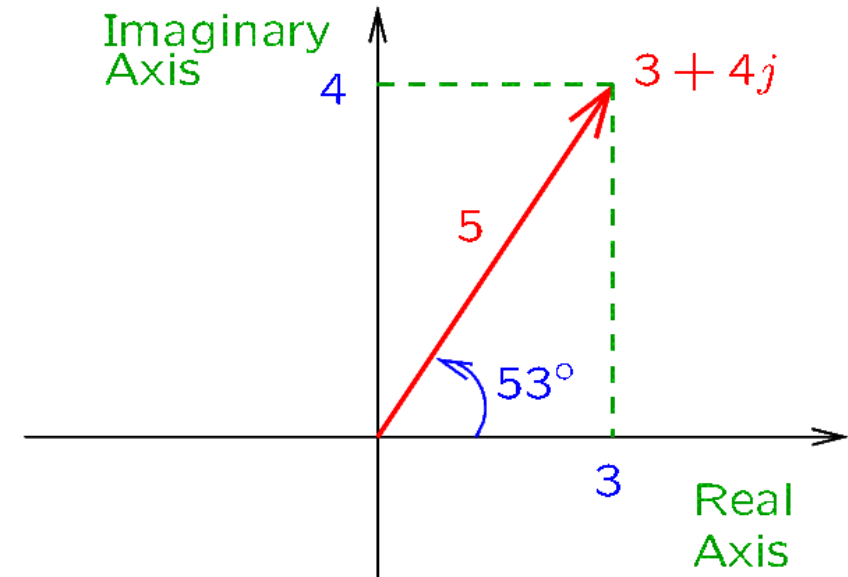
We write that $h = 3 + 4j = 5\angle 53.15^\circ$.




The Frequency Domain

- In the **time domain**, the signal $m(t) = M \cos(\omega t + \alpha)$ is a sinusoidal function.
- In the **frequency domain**, the signal is a vector $\mathbf{M}(t) = M \angle \omega t + \alpha$ that rotates counterclockwise in the complex plane at an angular velocity ω .
- Such rotating vectors are called **PHASORS**.

TIME DOMAIN

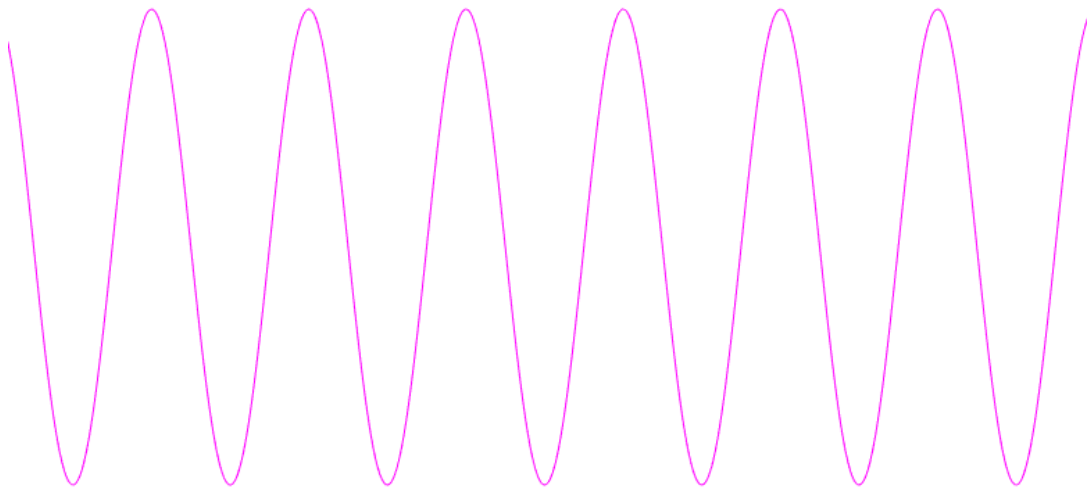

FREQUENCY DOMAIN

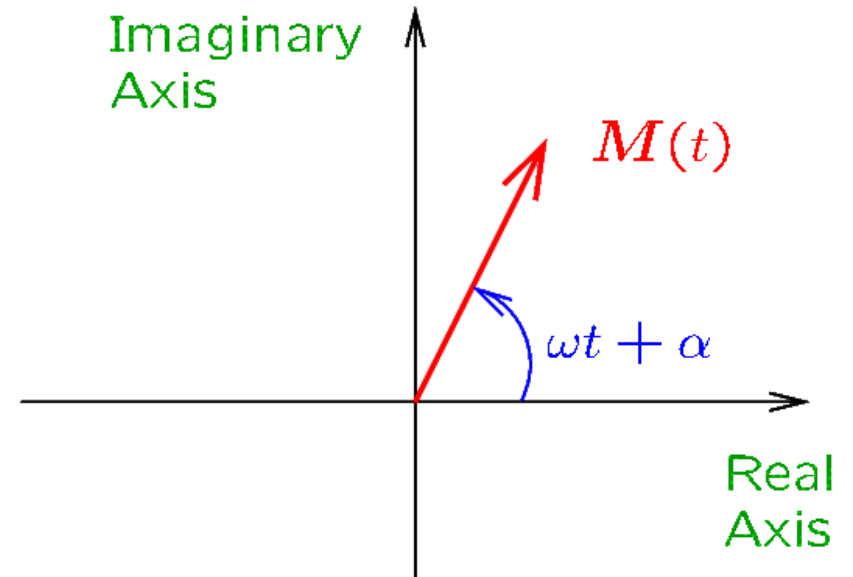


Impedance

- Assume a network with two terminals that has *no independent sources*.
- A voltage $v(t) = V_m \cos(\omega t + \alpha_v)$ will result in a sinusoidal steady-state current of the same frequency: $i(t) = I_m \cos(\omega t + \alpha_i)$.
- In the frequency domain, these correspond to the phasors


$$V(t) = V_m e^{j\omega t + j\alpha_v} \text{ and } I(t) = I_m e^{j\omega t + j\alpha_i}.$$

- For a linear network, the ratio $Z = V(t)/I(t)$ is a constant called **impedance**.

TIME DOMAIN

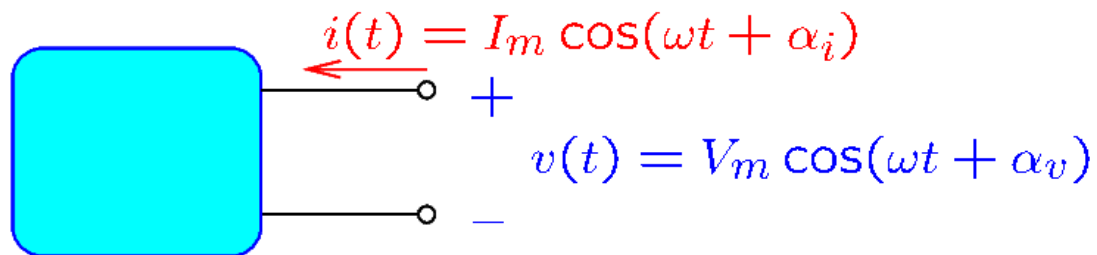

FREQUENCY DOMAIN

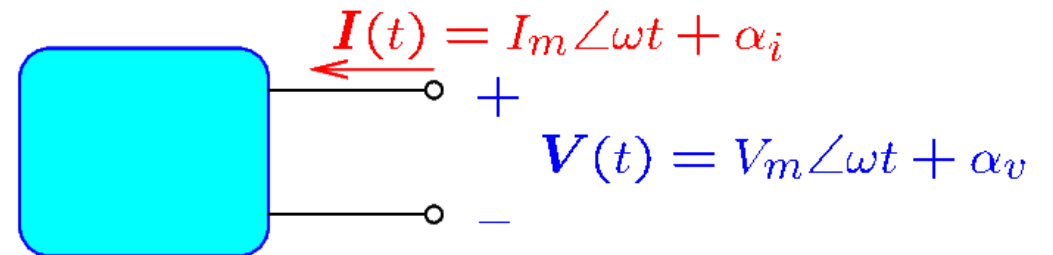

$$Z = \frac{V(t)}{I(t)} = \frac{V_m}{I_m} \angle \alpha_v - \alpha_i$$

Impedance

- Since $V(t) = V_m e^{j\omega t + j\alpha_v}$ and $I(t) = I_m e^{j\omega t + j\alpha_i}$, impedance is independent of time:




$$\mathbf{Z} = \frac{V(t)}{I(t)} = \frac{V_m}{I_m} e^{j(\alpha_v - \alpha_i)}$$

- *The impedance is a constant, not a phasor!*
- *Only voltages and currents are phasors.*
- The impedance unit is Ohms [Ω].
- *Impedance resembles resistance; it could be viewed as an “AC resistance”.*




Impedance of Common Components

Resistors, capacitors, and inductors are represented in the frequency domain by their impedance.

TIME DOMAIN

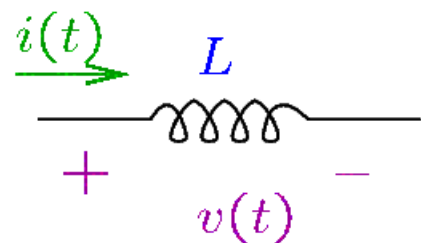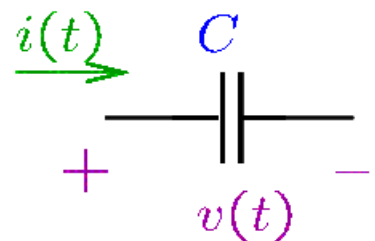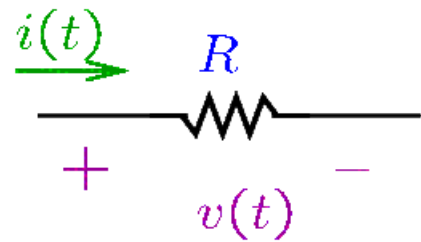

FREQUENCY DOMAIN

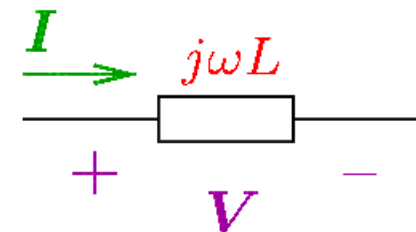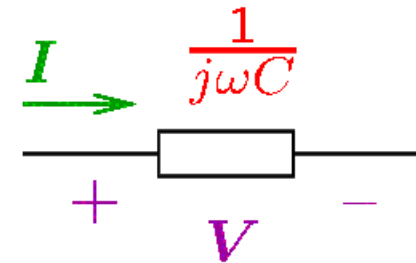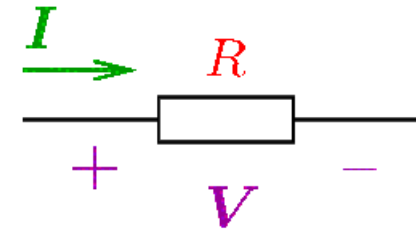

Phasors—Abbreviated Notation

- Assume all sources of a circuit have the same frequency.
- Every phasor $\mathbf{N}(t) = N_m \angle \omega t + \alpha_n$ will differ from any other phasor $\mathbf{P}(t) = P_m \angle \omega t + \alpha_p$ only in magnitude and angle.
- The term ωt is common for all phasors.
- From now on, we will drop the ωt term.
- $\mathbf{N}(t) = N_m \angle \omega t + \alpha_n$ will be abbreviated $\mathbf{N} = N_m \angle \alpha_n$.

Examples

Write $v_x(t) = 3 \cos(100t + 45^\circ)$ V in the frequency domain.


$$\mathbf{V}_x = 3\angle 45^\circ \text{ V.}$$

Write $I_x = 50\angle -45^\circ$ mA in the time domain.

$$i_x(t) = 50 \cos(\omega t - 45^\circ) \text{ mA.}$$

Find the impedance of the network.

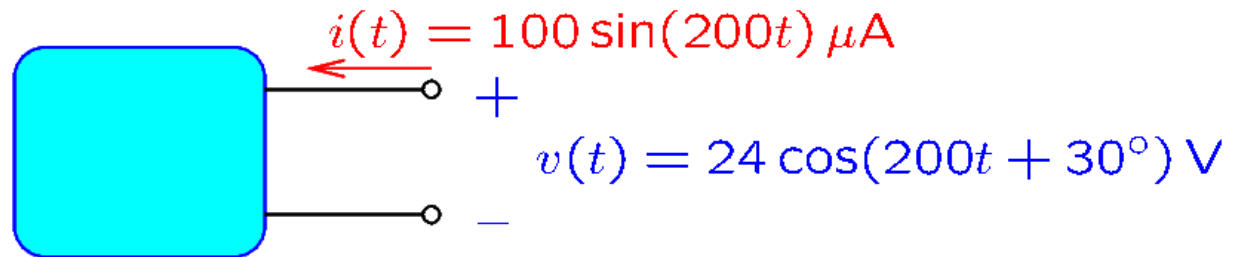- $i(t) = 100 \cos(200t - 90^\circ)$ μA .
- $\mathbf{I} = 100\angle -90^\circ$ μA .
- $\mathbf{V} = 24\angle 30^\circ$ V.
- $\mathbf{Z} = \frac{\mathbf{V}}{\mathbf{I}} = \frac{24\angle 30^\circ \text{ V}}{100\angle -90^\circ \mu\text{A}} = 240\angle 120^\circ \text{ k}\Omega.$



Example

Assume $v_1(t) = 3 \cos(200t + 30^\circ)$ V and $v_2(t) = 30 \cos(200t - 60^\circ)$ V. Write the total voltage $v_t(t) = v_1(t) + v_2(t)$ as a sinusoidal function of time.

- $V_1 = 3 \angle 30^\circ = 3 \cos(30^\circ) + j3 \sin(30^\circ) = 1.5\sqrt{3} + 1.5j$ V.
- $V_2 = 30 \angle -60^\circ = 30 \cos(-60^\circ) + j30 \sin(-60^\circ) = 15 - j15\sqrt{3}$ V.
- $V_t = V_1 + V_2 = 17.6 - 24.48j = \sqrt{17.6^2 + (-24.48)^2} \angle \alpha = 30.15 \angle \alpha$ V.
- The angle $\alpha = \tan^{-1} \left(-\frac{24.48}{17.6} \right) + k \cdot 180^\circ$,
where k could be 0 or ± 1 , depending on the quadrant.
- In this case $\alpha = -54.29^\circ + k \cdot 180^\circ$.
- The angle is in a quadrant with $k = 0$.
- Hence, $V_t = 30.15 \angle -54.29^\circ$ V.
- The final answer is
 $v_t(t) = 30.15 \cos(200t - 54.29^\circ)$ V.

