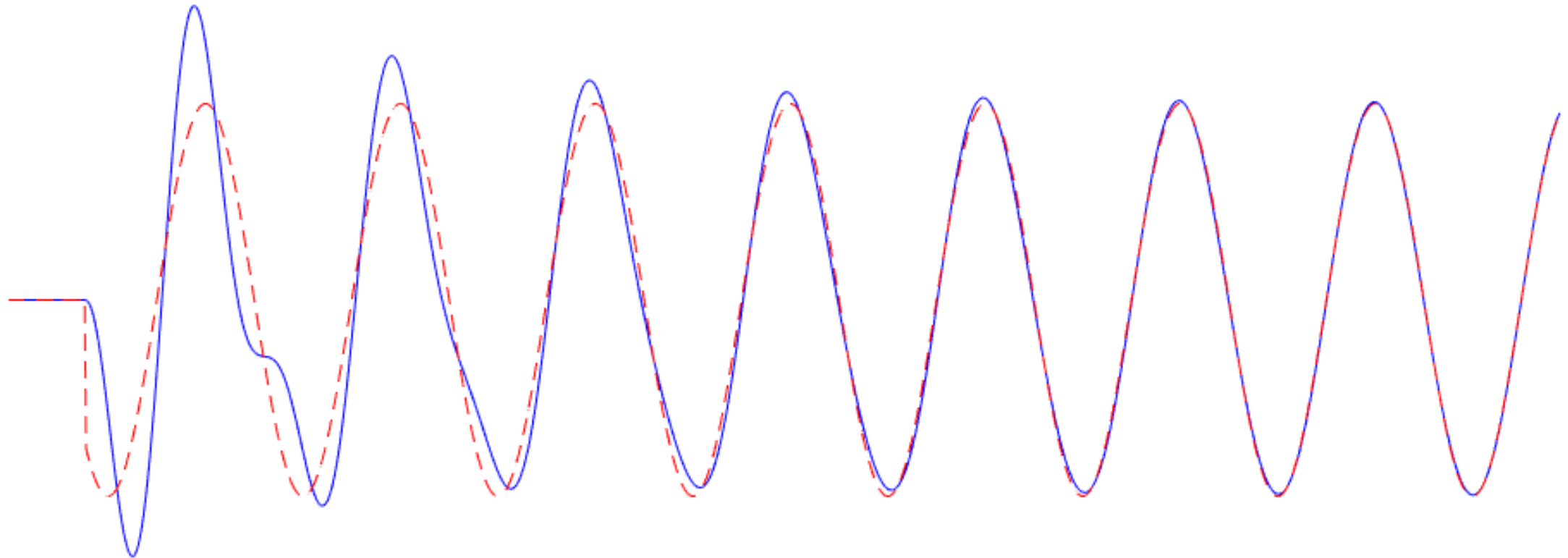


The Impedance

Impedance Review. Complex Number Review. Admittance. Application to Voltage and Current Division.

Review


- When an AC circuit is turned on, there are transients (the blue curve).
- *In time, voltages and currents converge to steady-state values (the red curve).*
- Phasor analysis is the fastest way to find steady-state voltages and currents.




Review—Phasors

- In the **time domain**, the signal $m(t) = M \cos(\omega t + \alpha)$ is a sinusoidal function.
- In the **frequency domain**, the signal is a vector $\mathbf{M}(t) = M \angle \omega t + \alpha$ that rotates counterclockwise in the complex plane at an angular velocity ω .
- Such rotating vectors are called **PHASORS**.
- We use an *abbreviated phasor notation*: $\mathbf{M} = M \angle \alpha$ (the ωt term is dropped).

TIME DOMAIN

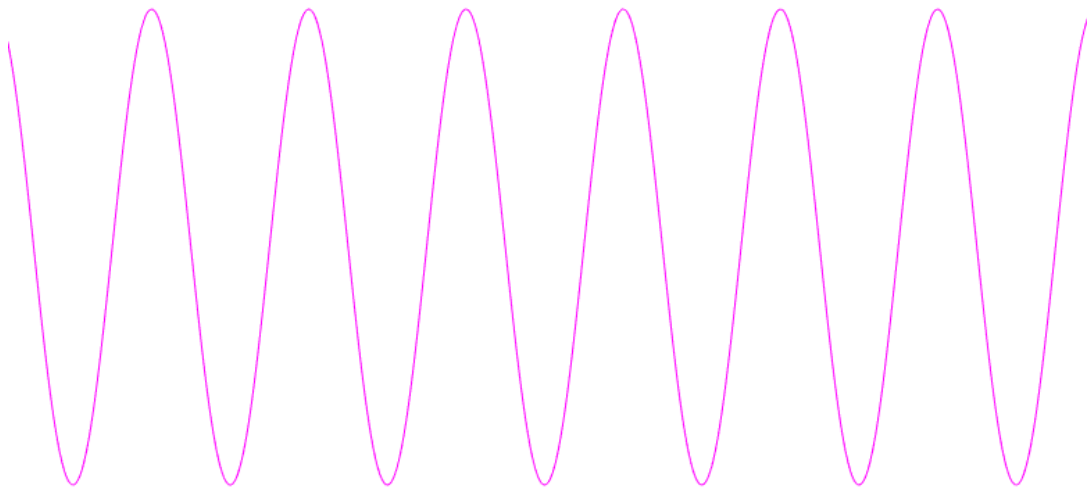

FREQUENCY DOMAIN

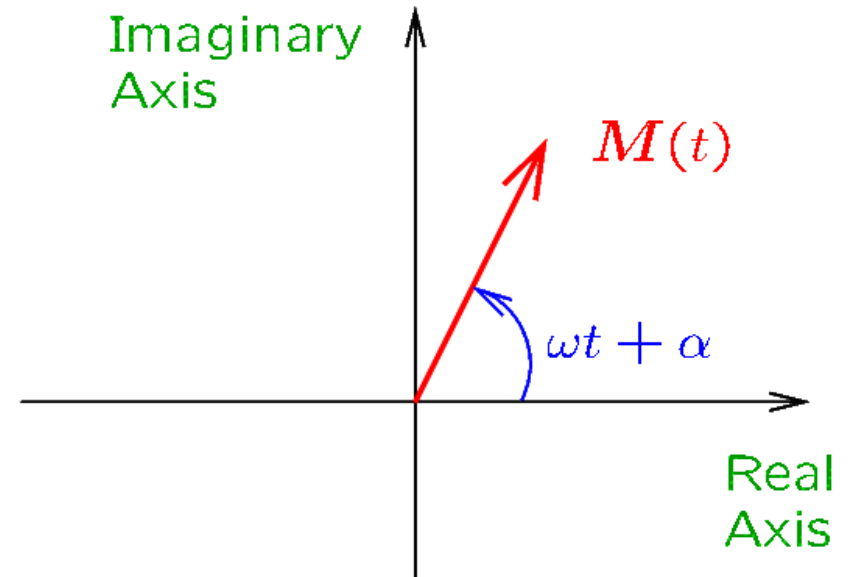


Review—Impedance

- Assume a network with two terminals that has *no independent sources*.
- A voltage $v(t) = V_m \cos(\omega t + \alpha_v)$ will result in a sinusoidal steady-state current of the same frequency: $i(t) = I_m \cos(\omega t + \alpha_i)$.
- In the frequency domain, these correspond to the phasors


$$V(t) = V_m e^{j\omega t + j\alpha_v} \text{ and } I(t) = I_m e^{j\omega t + j\alpha_i}.$$

- For a linear network, the ratio $Z = V(t)/I(t)$ is a constant called **impedance**.

TIME DOMAIN

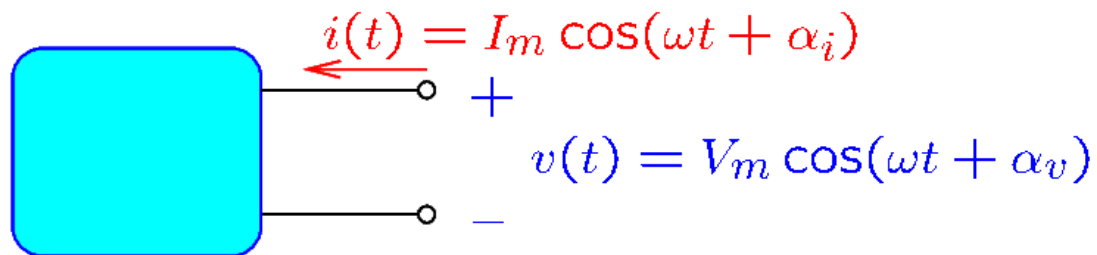

FREQUENCY DOMAIN

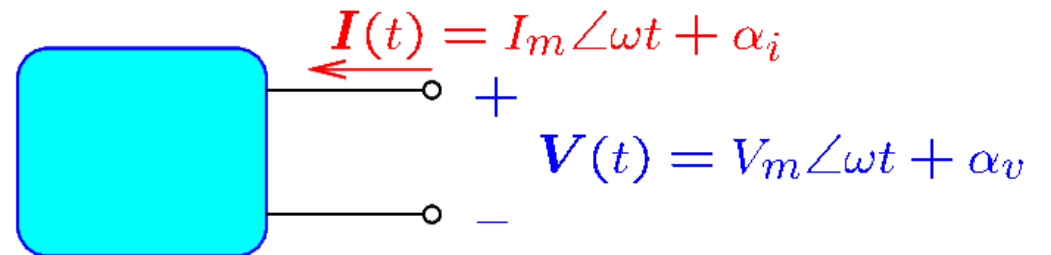

$$Z = \frac{V(t)}{I(t)} = \frac{V_m}{I_m} \angle \alpha_v - \alpha_i$$

Review—Impedance

- Since $V(t) = V_m e^{j\omega t + j\alpha_v}$ and $I(t) = I_m e^{j\omega t + j\alpha_i}$, impedance is independent of time:




$$\mathbf{Z} = \frac{V(t)}{I(t)} = \frac{V_m}{I_m} e^{j(\alpha_v - \alpha_i)}$$

- *The impedance is a constant, not a phasor!*
- *Only voltages and currents are phasors.*
- The impedance unit is Ohms [Ω].
- *Impedance resembles resistance; it could be viewed as an “AC resistance”.*




Review—Impedance

Resistors, capacitors, and inductors are represented in the frequency domain by their impedance. *Memorize the impedance formulas!*

TIME DOMAIN

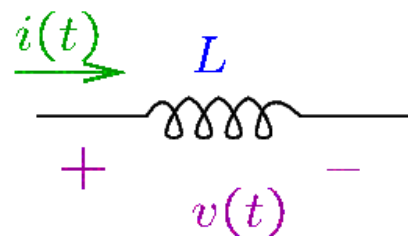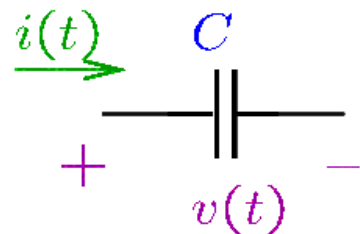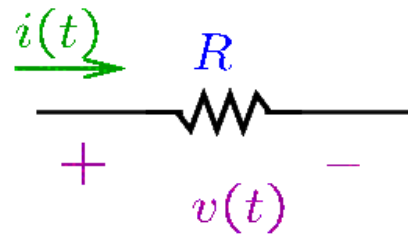

FREQUENCY DOMAIN

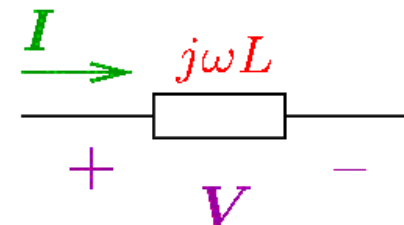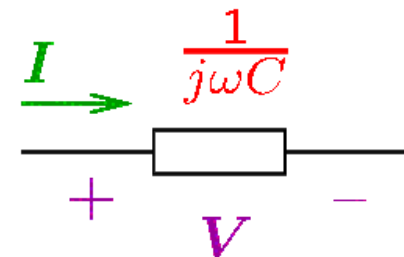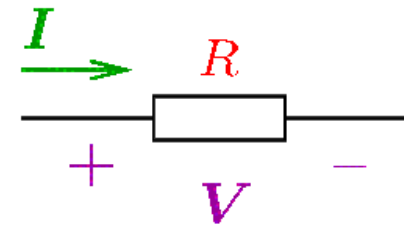


Impedance Combinations

- The methods learned for DC circuits apply also to AC circuits *in the frequency domain*.
- Series and parallel impedances are combined just like resistors.

Example: Find the impedance of the shown network. Assume $f = \frac{10}{2\pi}$ kHz.

- The angular frequency is: $\omega = 2\pi f$.
- The resistor impedance: $\mathbf{Z}_R = 1 \text{ k}\Omega$.
- The inductor has $\mathbf{Z}_L = j\omega L = j \text{ k}\Omega$.
- The capacitor has $\mathbf{Z}_C = \frac{1}{j\omega C} = \frac{1}{j} \text{ k}\Omega$.
- Overall, $\mathbf{Z} = \mathbf{Z}_L + (\mathbf{Z}_R || \mathbf{Z}_C)$.

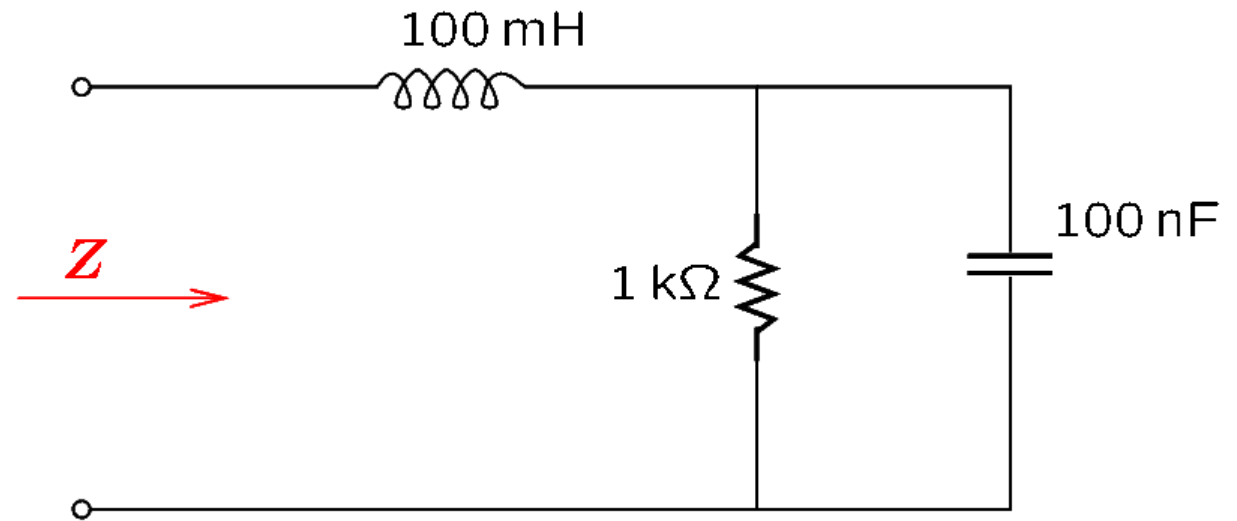

Complex Numbers—Review


To finish our example, let us review first some complex number concepts.

$$(m\angle\alpha) \cdot (n\angle\beta) = me^{j\alpha} ne^{j\beta} = mne^{j\alpha+j\beta} = mn\angle\alpha + \beta$$

$$\frac{m\angle\alpha}{n\angle\beta} = \frac{me^{j\alpha}}{ne^{j\beta}} = \frac{m}{n} e^{j\alpha-j\beta} = \frac{m}{n} \angle\alpha - \beta$$

In our example:
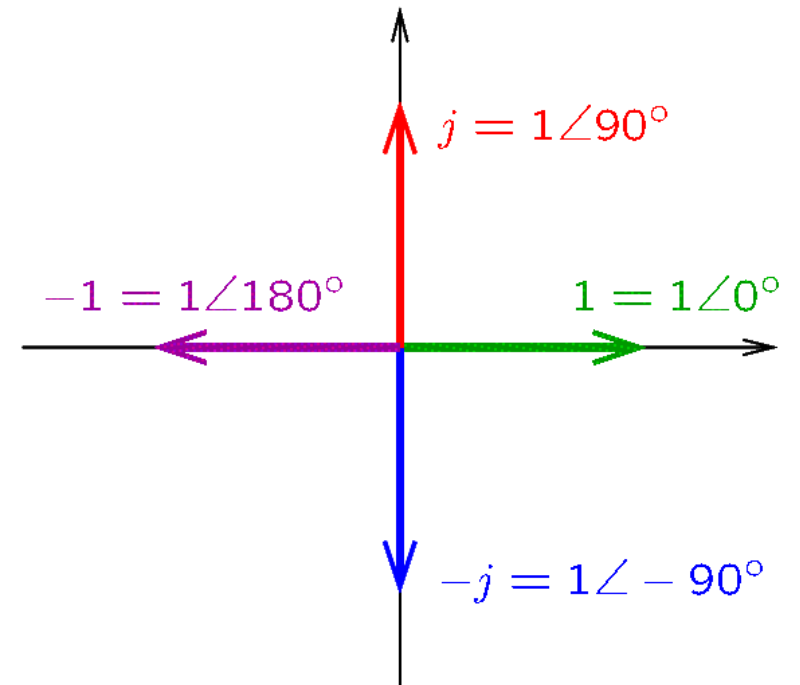
$$Z_C = \frac{1}{j} = \frac{1\angle 0^\circ}{1\angle 90^\circ} = 1\angle -90^\circ = -j \text{ k}\Omega$$



Complex Numbers—Review

$$\mathbf{Z}_C || \mathbf{Z}_R = \frac{1}{\frac{1}{\mathbf{Z}_C} + \frac{1}{\mathbf{Z}_R}} = \frac{1}{\frac{j}{10^3} + \frac{1}{10^3}} = \frac{10^3}{1+j} \Omega = \frac{1}{1+j} k\Omega$$

There are two ways to simplify this expression.

Method 1: *Convert $1 + j$ to polar form*

$$\frac{1}{1+j} = \frac{1}{\sqrt{1^2 + 1^2} \angle \tan^{-1} \frac{1}{1}} = \frac{1 \angle 0^\circ}{\sqrt{2} \angle 45^\circ} = \frac{1}{\sqrt{2}} \angle -45^\circ$$


Method 2: *Multiply numerator and denominator by complex conjugate*

$$\frac{1}{1+j} = \frac{1}{1+j} \cdot \frac{1-j}{1-j} = \frac{1-j}{1^2 + 1^2} = \frac{1-j}{2} = \frac{1}{\sqrt{2}} \angle -45^\circ$$

We conclude that $\mathbf{Z}_C || \mathbf{Z}_R = \frac{1}{\sqrt{2}} \angle -45^\circ k\Omega$.

Complex Numbers—Review

- Given a complex number $c = m + jn = |c|\angle\alpha$,
 - $|c| = \sqrt{m^2 + n^2}$ is the **magnitude** (aka *absolute value*) of c .
 - $m + jn$ is the **rectangular form** of c .
 - $|c|\angle\alpha$ is the **polar form** of c .
 - $c^* = m - jn = |c|\angle -\alpha$ is the **complex conjugate** of c .
 - Note that $c \cdot c^* = |c|^2$.

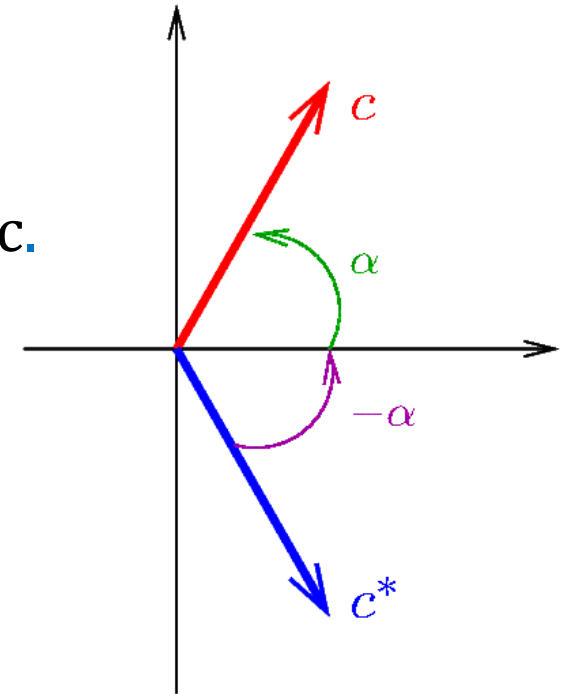

To finish our example:

$$\mathbf{Z} = \mathbf{Z}_L + (\mathbf{Z}_C || \mathbf{Z}_R) = j + \frac{1-j}{2} = \frac{1+j}{2} \text{ k}\Omega = 707.11\angle 45^\circ \Omega$$

Impedance Combinations

Example: Find $i(t)$. Assume $f = \frac{10}{2\pi}$ kHz.

- The source has a phasor voltage:

$$V_s(t) = 3\cos(\omega t) \text{ V}$$

- Using the abbreviated notation:

$$V_s = 3\angle 0^\circ \text{ V}$$


- The total impedance Z is known from the previous example:

$$Z = \frac{1}{\sqrt{2}}\angle 45^\circ \text{ k}\Omega$$

- The phasor current is

$$I = \frac{V_s}{Z} = \frac{3\angle 0^\circ}{\frac{1}{\sqrt{2}}\angle 45^\circ} = 4.24\angle -45^\circ \text{ mA}$$

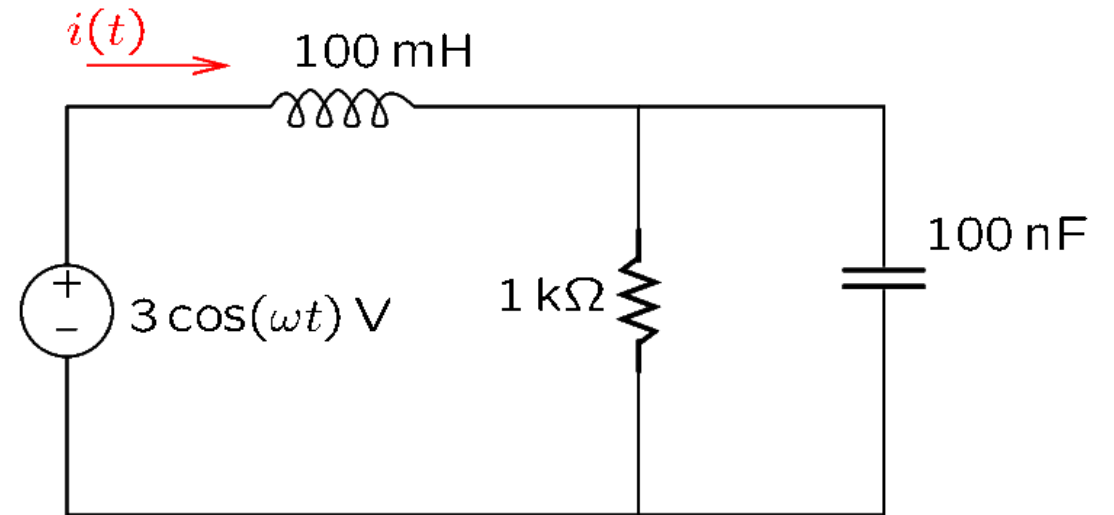- Therefore, in the time domain, $i(t) = 4.24\cos(\omega t - 45^\circ) \text{ mA}$.



Reactance

- Consider the rectangular form of the impedance:

$$\mathbf{Z} = R + jX$$

- The real part R is called **resistance**.
- The imaginary part X is called **reactance**.
- The unit of R and X is **Ohms $[\Omega]$** .

- **Example:** For an inductor, $\mathbf{Z} = j\omega L$. The reactance is $X = \omega L$.
- **Example:** For a capacitor, $\mathbf{Z} = \frac{1}{j\omega C} = -\frac{j}{\omega C}$. The reactance is $X = -\frac{1}{\omega C}$.

Admittance, Conductance, Susceptance

- The **admittance** is defined as

$$Y = \frac{1}{Z}$$

- Consider the rectangular form of the admittance:

$$Y = G + jB$$

- The real part G is called **conductance**.
- The imaginary part B is called **susceptance**.
- The unit of G and B is **Siemens [S]** or $[\Omega^{-1}]$.

Admittance, Conductance, Susceptance

Example: Find the conductance and the susceptance of $\mathbf{Z} = 4 - 3j \Omega$.


- The admittance is

$$Y = \frac{1}{4 - 3j} = \frac{1}{4 - 3j} \cdot \frac{4 + 3j}{4 + 3j} = \frac{4 + 3j}{4^2 + (-3)^2} = 160 + 120j \text{ mS}$$

- Therefore, $G = 160 \text{ mS}$ and $B = 120 \text{ mS}$.
- In this example the resistance is $R = 4 \Omega$ and the reactance is $X = -3 \Omega$.
- It is important to note that in general $G \neq \frac{1}{R}$ and always $B \neq \frac{1}{X}$.

Voltage and Current Division

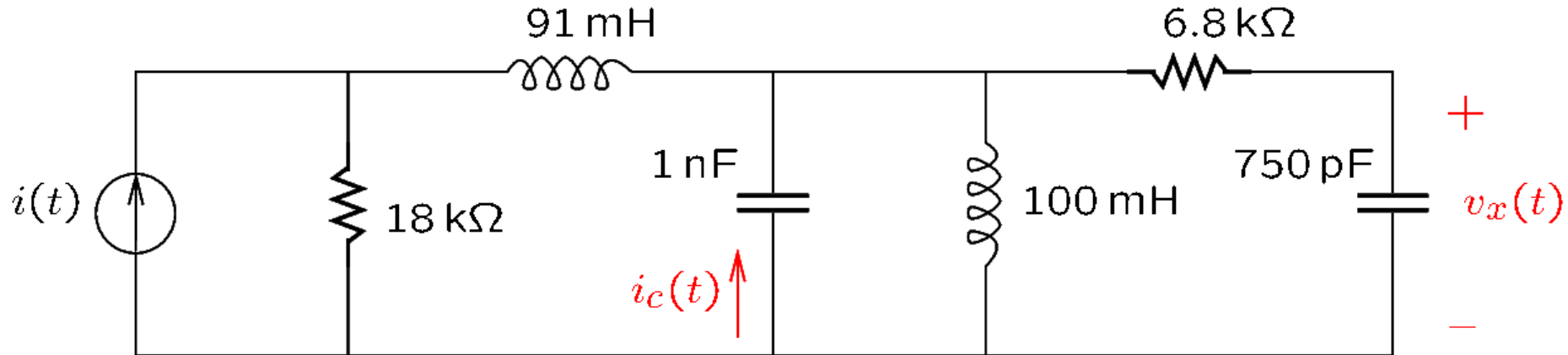- The methods learned for DC circuits apply also to AC circuits *in the frequency domain*.
- In particular, this is true of voltage and current division.




Example: Find $i_c(t)$ and $v_x(t)$. Assume $f = \frac{100}{2\pi} \text{ kHz}$ and $i(t) = 10 \cos(\omega t + 10^\circ) \mu\text{A}$.

- Since $\omega = 2\pi f = 10^5 \text{ rad/s}$, using the formulas $\mathbf{Z}_L = j\omega L$ and $\mathbf{Z}_C = \frac{1}{j\omega C}$:

$$\mathbf{Z}_{91m} = 9.1j \text{ k}\Omega, \mathbf{Z}_{100m} = 10j \text{ k}\Omega, \mathbf{Z}_{1n} = -10j \text{ k}\Omega, \text{ and } \mathbf{Z}_{750p} = -13.33j \text{ k}\Omega.$$

Voltage and Current Division

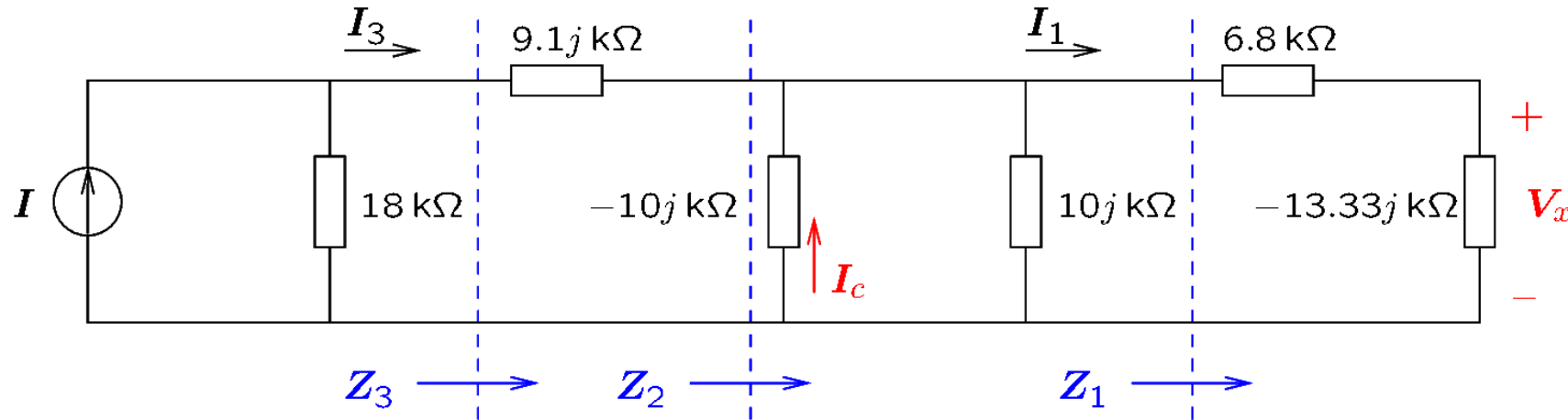
- The frequency domain circuit is shown in the figure.



The problem will be solved as follows.

- We will find first Z_1 , Z_2 , and Z_3 .
- Next, current division will be used to find I_3 , I_c , and I_1 .
- Next, Ohm's law will be used to find $V_x = -13.33j\text{ k}\Omega \cdot I_1$.
- The results will be converted to the time domain.

Voltage and Current Division

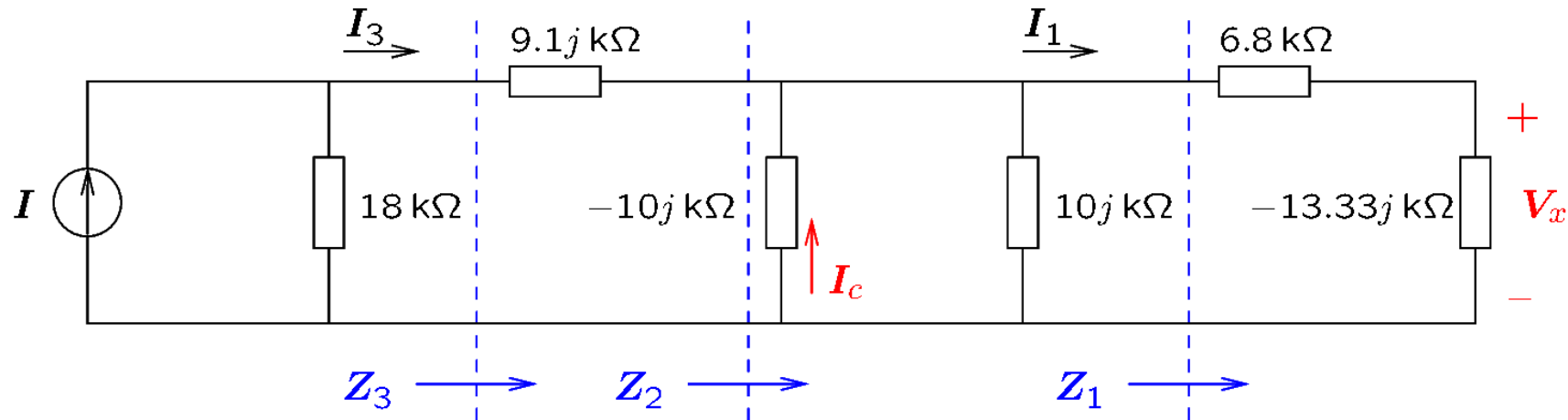


$$Z_1 = 6.8 - 13.33j \text{ k}\Omega$$

$$Z_2 = \frac{1}{\frac{1}{-10j \text{ k}\Omega} + \frac{1}{10j \text{ k}\Omega} + \frac{1}{Z_1}} = Z_1$$

$$Z_3 = 9.1j \text{ k}\Omega + Z_2 = 6.8 - 4.23j \text{ k}\Omega$$

Since $i(t) = 10 \cos(\omega t + 10^\circ) \mu\text{A}$, it follows that $I = 10 \angle 10^\circ \mu\text{A}$.

Voltage and Current Division

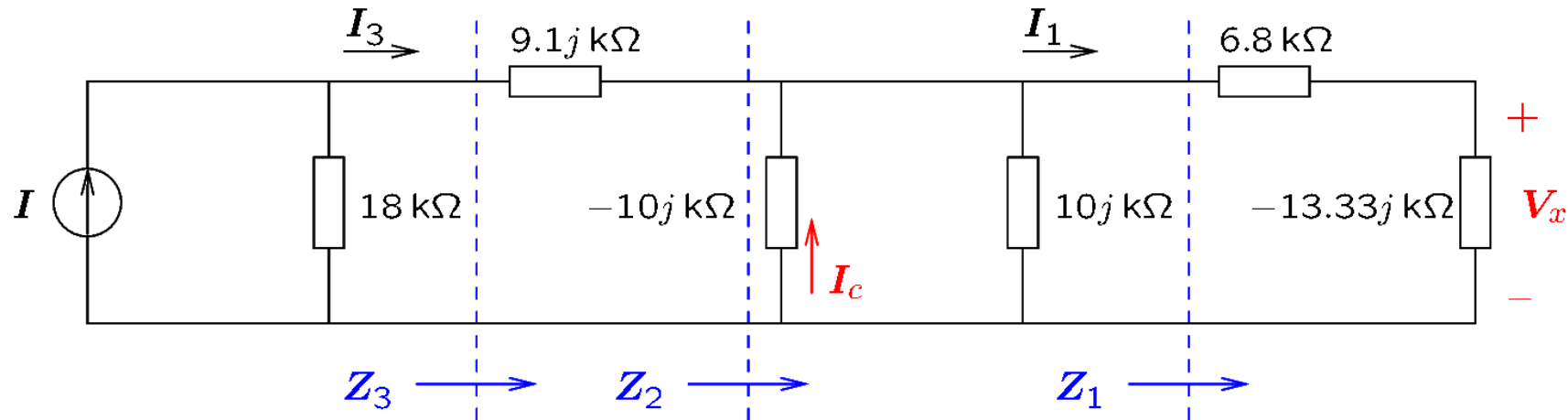


$$I_3 = I \frac{\frac{1}{Z_3}}{\frac{1}{18\text{ k}\Omega} + \frac{1}{Z_3}} = 10\angle 10^\circ \mu\text{A} \frac{18\text{ k}\Omega}{18\text{ k}\Omega + Z_3} = 10\angle 10^\circ \mu\text{A} \frac{18}{25.16\angle -9.68^\circ} = 7.15\angle 19.68^\circ \mu\text{A}$$

$$I_1 = I_3 \frac{\frac{1}{Z_1}}{\frac{1}{-10j\text{ k}\Omega} + \frac{1}{10j\text{ k}\Omega} + \frac{1}{Z_1}} = I_3 \Rightarrow V_x = -13.33j\text{ k}\Omega \cdot I_1 = 95.37\angle -70.32^\circ\text{ mV}$$

$$\Rightarrow v_x(t) = 95.37 \cos(\omega t - 70.32^\circ)\text{ mV}$$

Voltage and Current Division

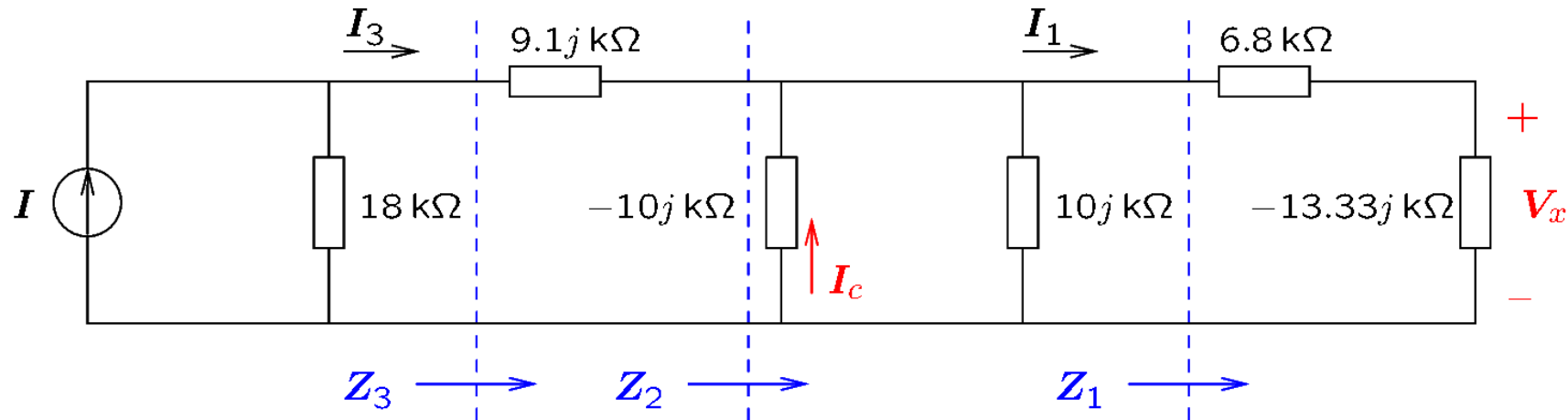

$$I_c = -I \frac{\frac{1}{-10j\text{ k}\Omega}}{\frac{1}{-10j\text{ k}\Omega} + \frac{1}{10j\text{ k}\Omega} + \frac{1}{Z_1}} = 10 \angle 10^\circ \mu\text{A} \frac{Z_1}{10j\text{ k}\Omega} = 14.96 \angle -142.97^\circ \mu\text{A}$$

$$\Rightarrow i_c(t) = 14.96 \cos(\omega t - 142.97^\circ) \mu\text{A}$$

Remarks

- In the previous example, the current source had $i(t) = 10 \cos(\omega t + 10^\circ) \mu A$, while the branch current $i_c(t)$ was $i_c(t) = 14.96 \cos(\omega t - 142.97^\circ) \mu A$.
- *In AC, currents/voltages do not have to be smaller than the value of the current/voltage source that causes them.*
- The previous example also illustrates that *an impedance can be infinite:*

$$(-10j \text{ k}\Omega) || (10j \text{ k}\Omega) = \frac{1}{\frac{1}{-10j} + \frac{1}{10j}} = \frac{1}{0} = \infty$$

- This impedance is infinite because the 1 nF capacitor and the 100 mH inductor cancel each other at the given frequency.