

# AC Analysis of Circuits—Part 2


Mesh Analysis. The Thevenin Equivalent.

# Analysis Methods

- The following apply **only in the frequency domain**.
  - *Nodal analysis*
  - *Mesh analysis*
  - *Voltage division*
  - *Current division*
  - *Source transformations*
- Superposition can be used in both frequency and time domains.
- The Thevenin equivalent is normally used in the frequency domain, but works also in the time domain.
- *Analysis methods are applied exactly the same way as for DC circuits.*
  - *The only difference is that we work with complex numbers.*


# Mesh Analysis

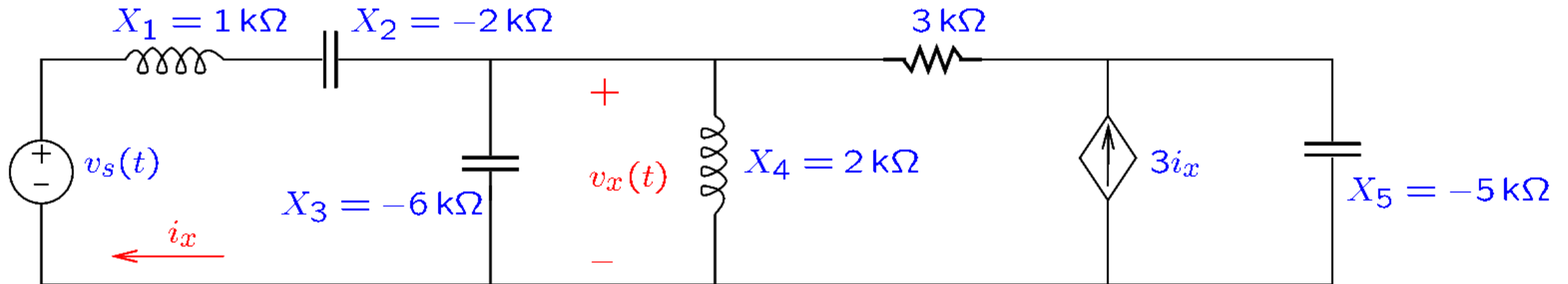Example: Find the voltage  $v_x(t)$  using *mesh* analysis. Assume  $v_s(t) = 5 \cos(\omega t + 30^\circ) \text{ V}$ . Reactance values are marked for each inductor and capacitor.




- In general, the first step is calculating inductor and capacitor impedances.
- This step is not carried out here, since the reactances are given.
- We will first draw the circuit in the frequency domain.

# Mesh Analysis—Example

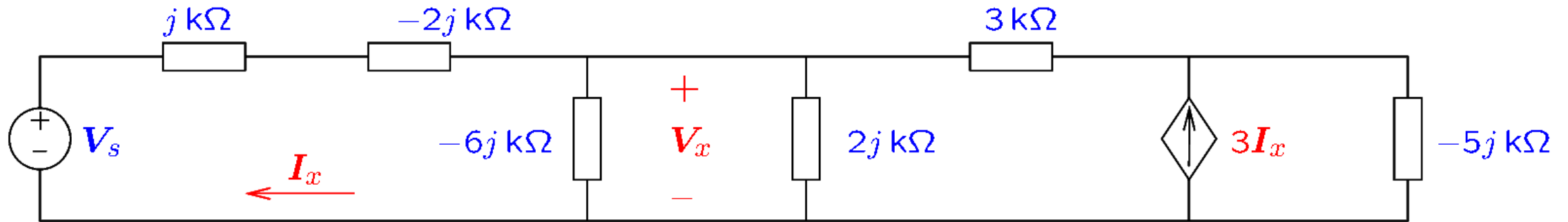

- *In the frequency domain:*
  - *Each resistor, inductor, and capacitor is replaced by an impedance.*
  - *$v_s(t) = 5 \cos(\omega t + 30^\circ) V$  becomes  $V_s = 5 \angle 30^\circ V$ .*
  - *$i_x(t)$  becomes  $I_x$ .*
- *Before applying mesh analysis, let's simplify the circuit as much as possible.*
  - *Let's combine the  $j k\Omega$  and  $-2j k\Omega$  impedances into  $Z_1 = j + (-2j) = -j k\Omega$ .*
  - *Let's combine the  $-6j k\Omega$  and  $2j k\Omega$  impedances into  $Z_2 = (-6j) || (2j) = 3j k\Omega$ .*

# Mesh Analysis—Example

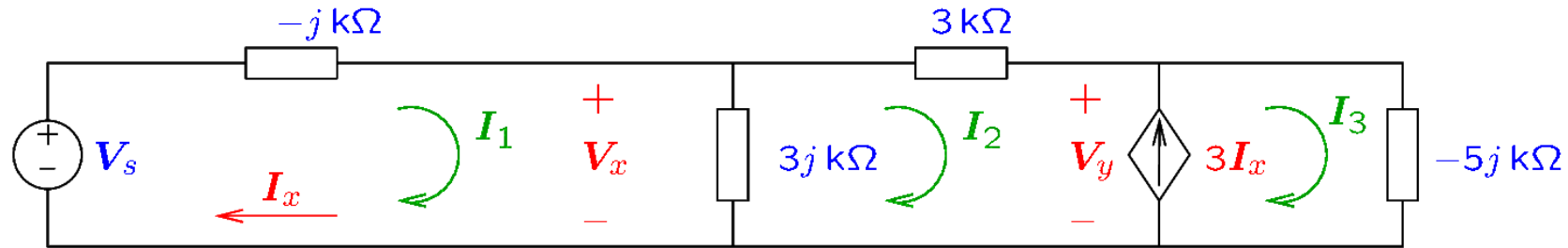

- *KVL on the first mesh is:*

$$-V_s + I_1(-j) + (I_1 - I_2)3j = 0$$

- *KVL on the supermesh is:*


$$(I_2 - I_1)3j + I_23 + I_3(-5j) = 0$$

- *The dependent source adds the constraint:*

$$I_3 - I_2 = 3I_x$$

where  $I_x = I_1$ .

# Mesh Analysis—Example

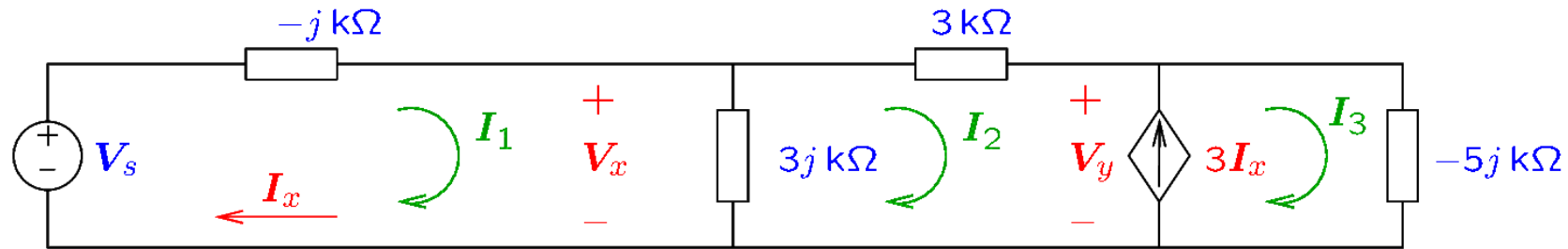

- The equations can be written in the form:

$$I_1 2j - I_2 3j = 5 \angle 30^\circ$$


$$-I_1 3j + I_2 (3 + 3j) + I_3 (-5j) = 0$$

$$3I_1 + I_2 - I_3 = 0$$

- Solving the equations and using  $V_x = 3j(I_1 - I_2)$  we obtain:

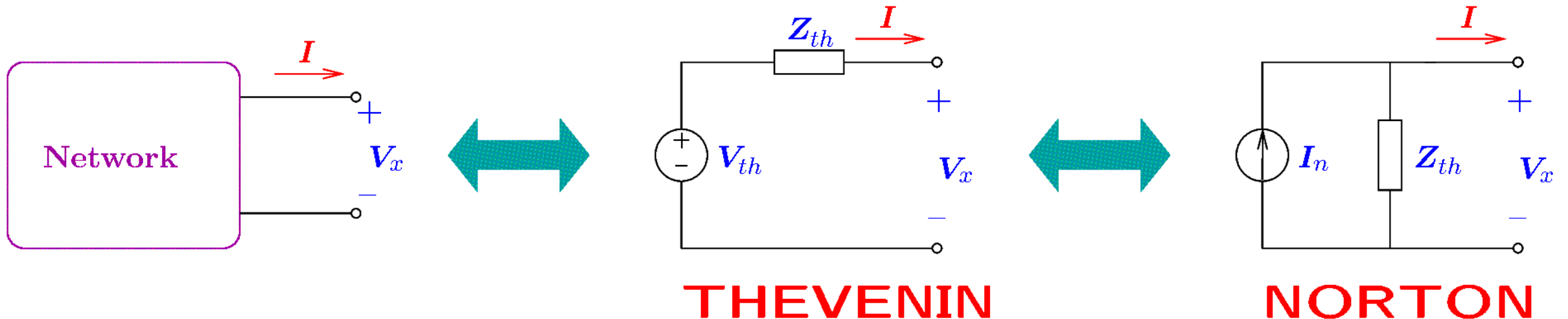
# Thevenin and Norton Equivalents

- Are obtained in the frequency domain.
- Can be converted to the time domain.
  - However, the time domain representation is frequency dependent.
- The equivalents are obtained using the same methods as in DC.
  - *However, note that we have a Thevenin impedance  $Z_{th}$  in the place of a Thevenin resistance  $R_{th}$ .*



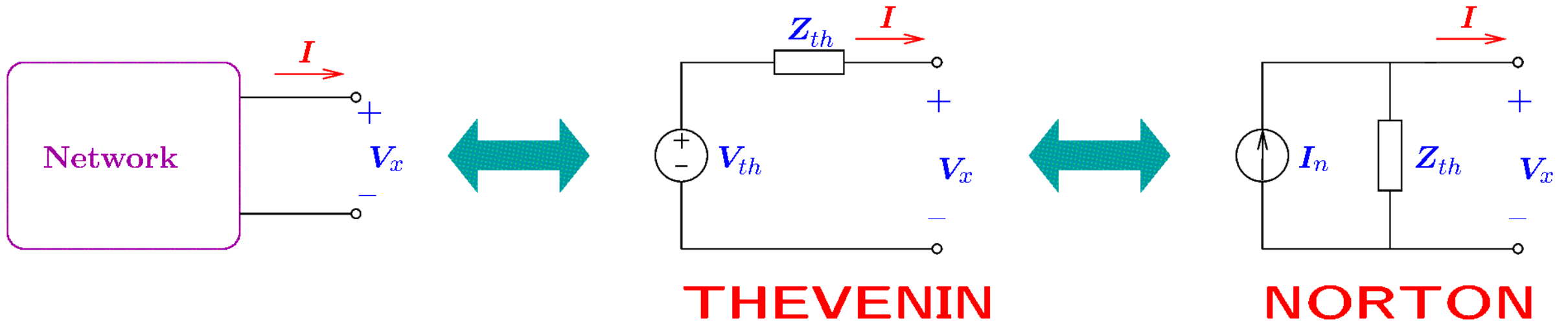
# Thevenin/Norton Equivalents—Review


- The original network and the Thevenin/Norton networks are equivalent in the sense that they will produce the same voltage and current when identically connected.
- *This does not mean that they will dissipate the same amount of power!*




# Thevenin/Norton Equivalents

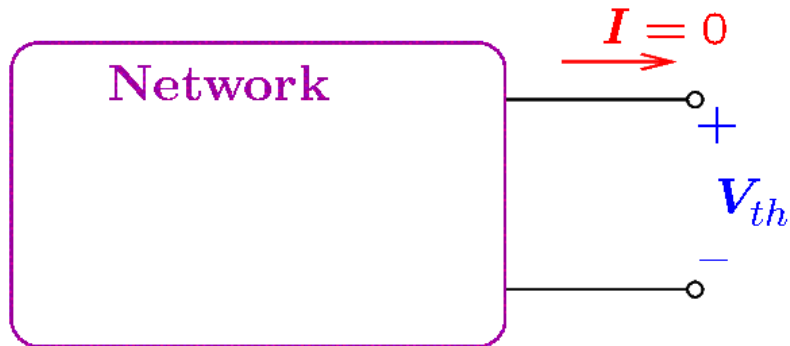

$V_{th}$  is the open-circuit voltage.

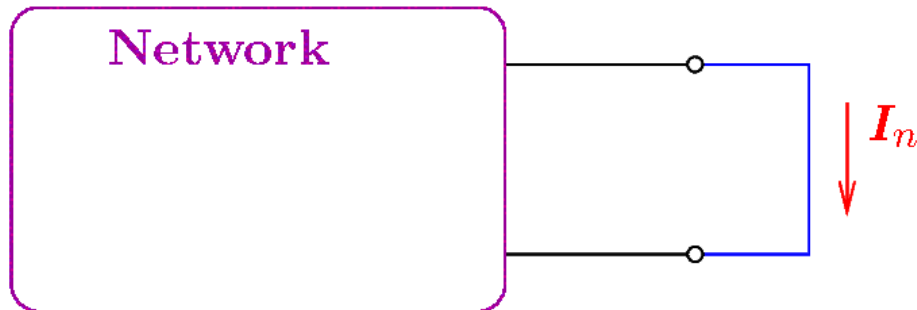

$I_n$  is the short-circuit current.

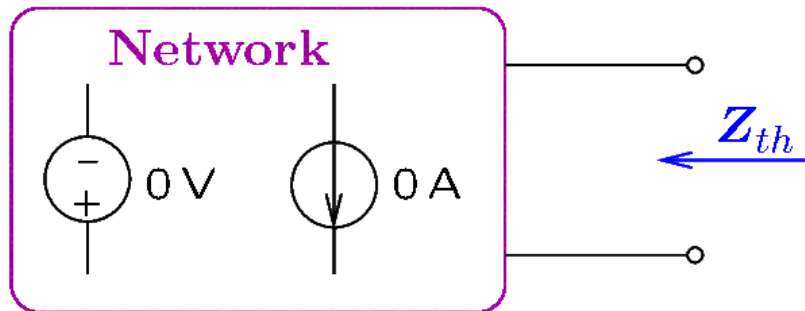


$Z_{th}$  is the impedance of the network when all **independent** sources are set to zero.


- *Dependent sources are not set to zero.*
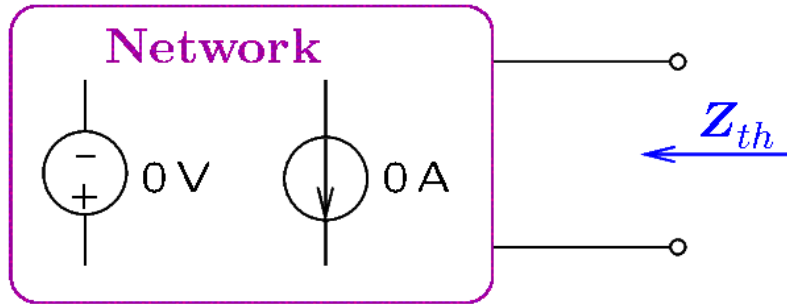
# Thevenin/Norton Equivalents—Finding $Z_{th}$

To find  $Z_{th}$ , set all independent sources to zero. Then:



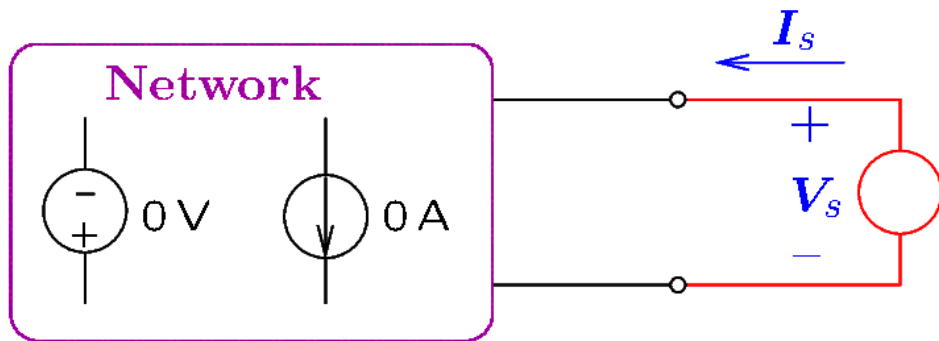
- Use *series and parallel combinations of impedances, if possible.*



- The general method is to **add an external source** and calculate  $Z_{th}$  with the formula:

$$Z_{th} = \frac{V_s}{I_s}$$
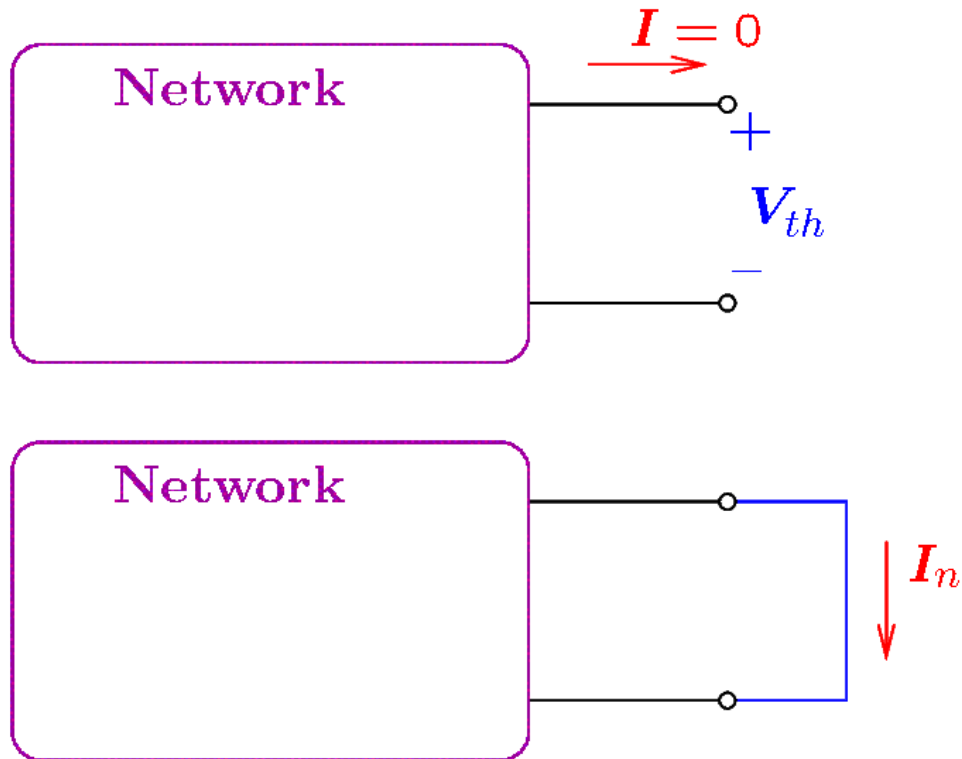
# Thevenin/Norton Equivalents—Finding $Z_{th}$




Another way to find  $Z_{th}$  is with the formula

$$Z_{th} = \frac{V_{th}}{I_n}$$

- This method can be used when the short-circuit current is not zero.
- Of course, all independent sources should be ON when finding  $V_{th}$  and  $I_n$ .

# Thevenin Equivalent—Example

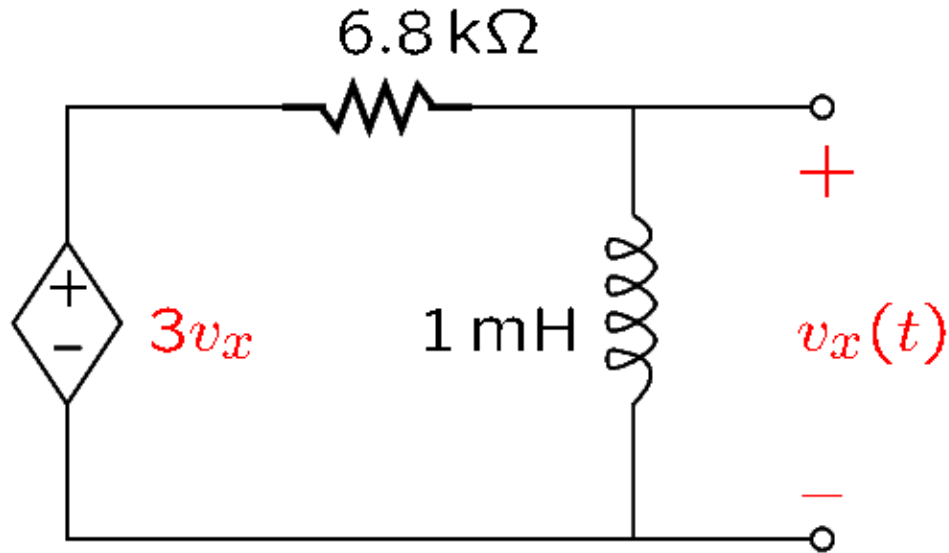

Find the Thevenin equivalent at the frequency  $f = \frac{1}{2\pi}$  MHz.


- The first step is to convert the circuit to the frequency domain.
- For this, we need to find the impedances.

$$\omega = 2\pi f = 10^6 \text{ rad/s}$$

$$Z_{6.8} = 6.8 \text{ k}\Omega$$

$$Z_{1m} = j\omega L = j \text{ k}\Omega$$

# Thevenin Equivalent—Example

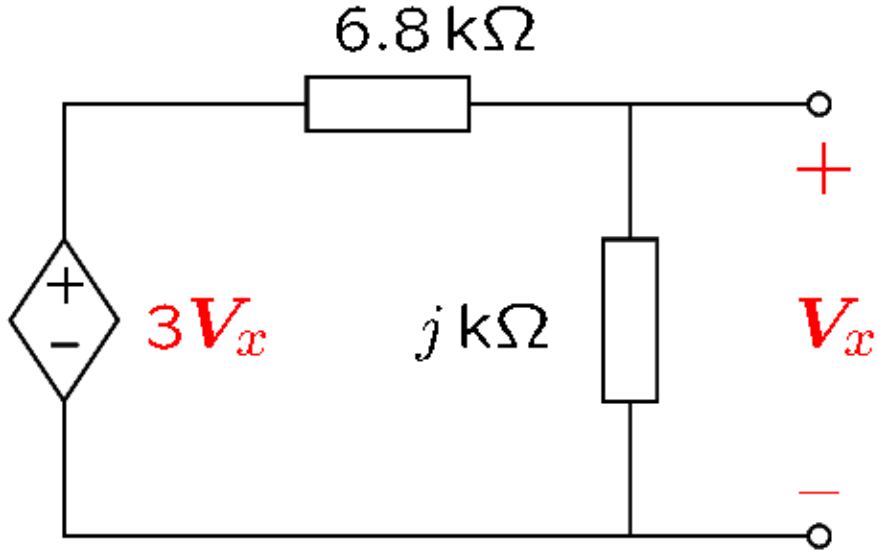

- The circuit has no independent source. Therefore,  $V_{th} = 0$ .
- For the same reason,  $I_n = 0$ . Therefore, the formula  $Z_{th} = V_{th}/I_n$  cannot be used.
- Impedance combinations cannot be done either, because of the dependent source.
  - Recall that dependent sources cannot be set to zero! Only independent sources are set to zero.
- Therefore, we will use the general method with an external source.



# Thevenin Equivalent—Example

- The formula  $\mathbf{Z}_{th} = \mathbf{V}_s / \mathbf{I}_s$  will be used.
- Note that  $\mathbf{V}_s = \mathbf{V}_x$ .
- By KCL:

$$\mathbf{I}_s = \frac{\mathbf{V}_x}{j} + \frac{\mathbf{V}_x - 3\mathbf{V}_x}{6.8}$$


$$\Rightarrow \frac{\mathbf{V}_x}{\mathbf{I}_s} = \frac{1}{\frac{1}{j} - \frac{2}{6.8}} = -0.2707 + 0.92038j \text{ k}\Omega$$

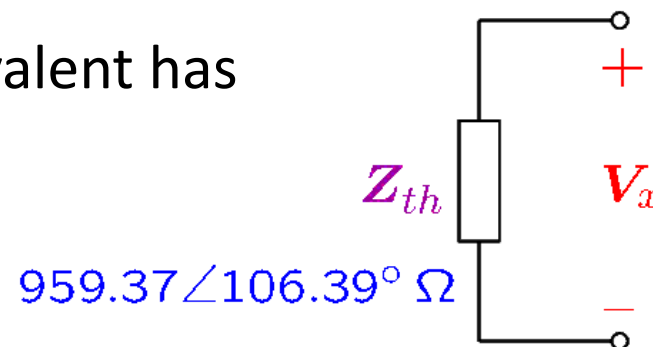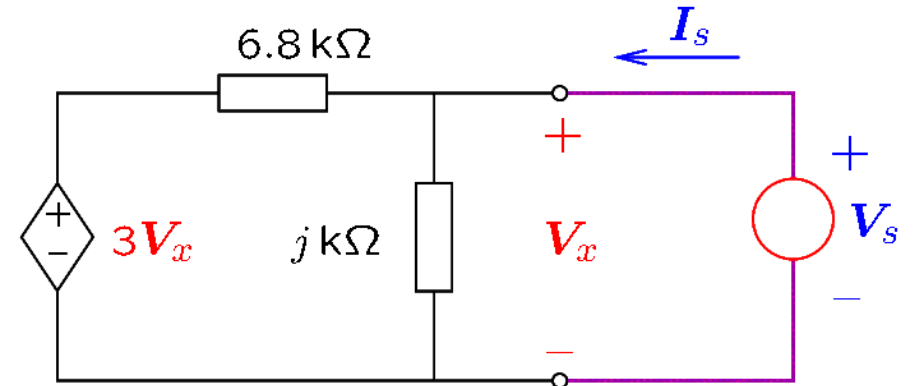- Therefore,  $\mathbf{Z}_{th} = -270.7 + 920.38 \Omega = 959.37 \angle 106.39^\circ \Omega$ .
- Since  $\mathbf{V}_{th} = 0$ , the Thevenin equivalent has the form shown in the figure.


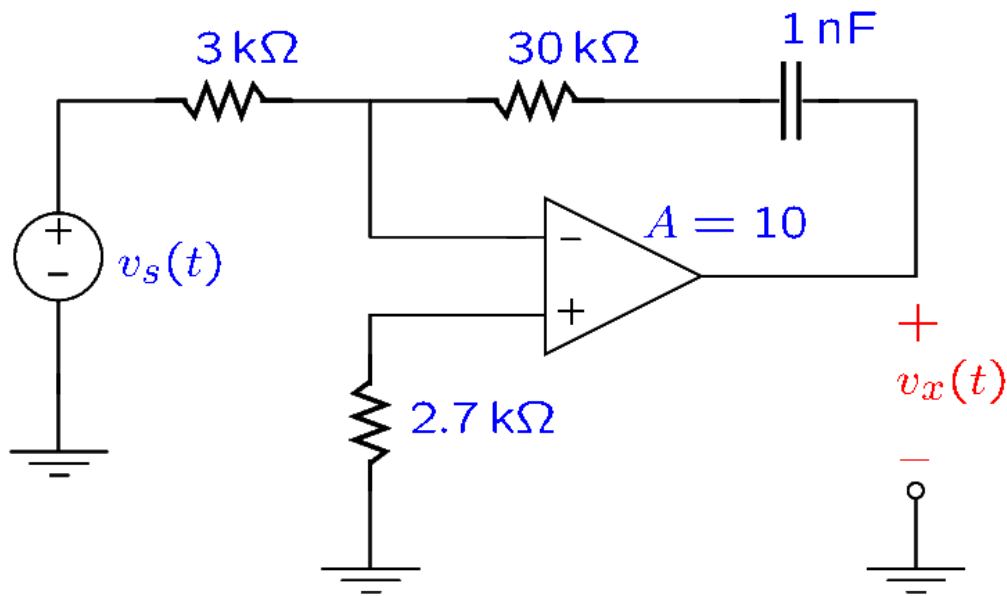
# Thevenin Equivalent—Example 2

Find the Thevenin equivalent assuming  $v_s(t) = 50 \cos(\omega t) \text{ mV}$ , a frequency  $f = 50 \text{ kHz}$ , and an operational amplifier with an output resistance of  $200 \Omega$ .



- The first step is to find the impedances.

$$\omega = 2\pi f = 314.1 \cdot 10^3 \text{ rad/s}$$


$$Z_{1n} = \frac{1}{j\omega C} = -3.18j \text{ k}\Omega$$

- The total impedance of the  $30 \text{ k}\Omega$  resistor and the capacitor is:

$$Z_t = 30 - 3.18j \text{ k}\Omega$$
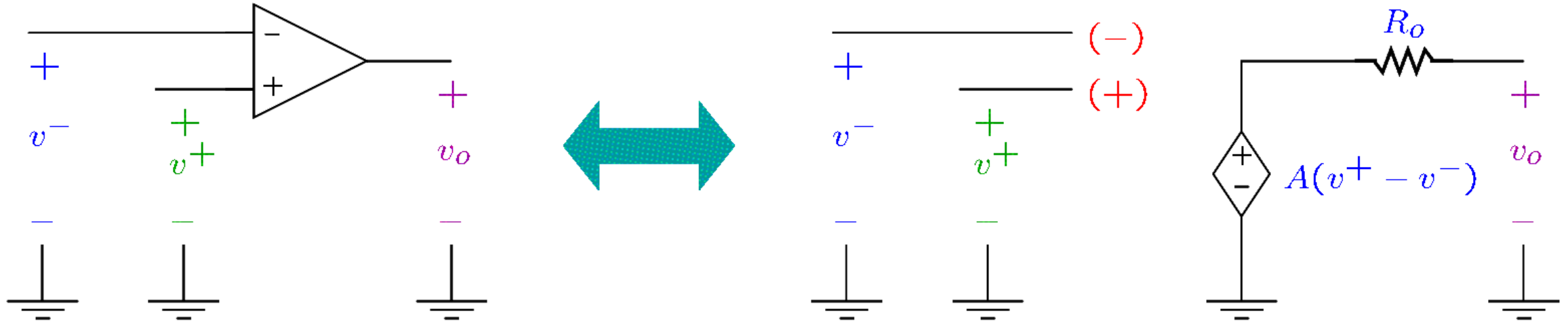
# Thevenin Equivalent—Example 2

- Here, the equivalent model of the operational amplifier includes also the output resistance  $R_o$ , which has been often neglected in homework problems.



# Thevenin Equivalent—Example 2


- To find the Thevenin equivalent, we will first derive  $V_{th}$ .

- Note that

$$V_s = 50 \angle 0^\circ \text{ mV}$$

$$V^+ = 0$$

$$A(V^+ - V^-) = -AV^-$$

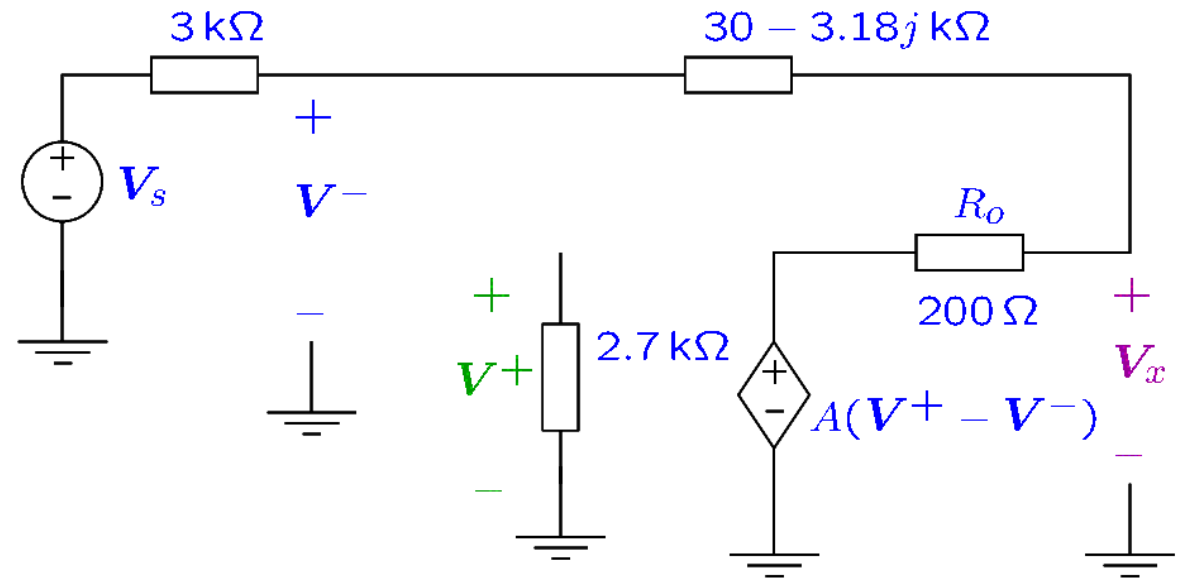

- The nodal equations are:

$$\frac{V_s - V^-}{3 \text{ k}\Omega} + \frac{(-AV^-) - V^-}{200 \Omega + 30 - 3.18j \text{ k}\Omega} = 0 \Rightarrow V^- = 23.99 \angle -3.13^\circ \text{ mV}$$

$$\frac{V_x - (-AV^-)}{200 \Omega} + \frac{V_x - V_s}{30 - 3.18j + 3 \text{ k}\Omega} = 0 \Rightarrow V_{th} = V_x = 238.21 \angle 176.83^\circ \text{ mV}$$

# Thevenin Equivalent—Example 2


- To find  $Z_{th}$ , note that series and parallel combinations of impedances will not work, due to the dependent source.
- The short-circuit current method is illustrated here.
- By voltage division,

$$V^- = V_s \cdot \frac{30 - 3.18j}{3 + 30 - 3.18j} = 45.50 \angle -0.55^\circ \text{ mV}$$

- The short-circuit current is:

$$I_n = \frac{V_s}{3 + 30 - 3.18j \text{ k}\Omega} + \frac{-AV^-}{200 \Omega} = 2.27 \angle 179.45^\circ \text{ mA}$$
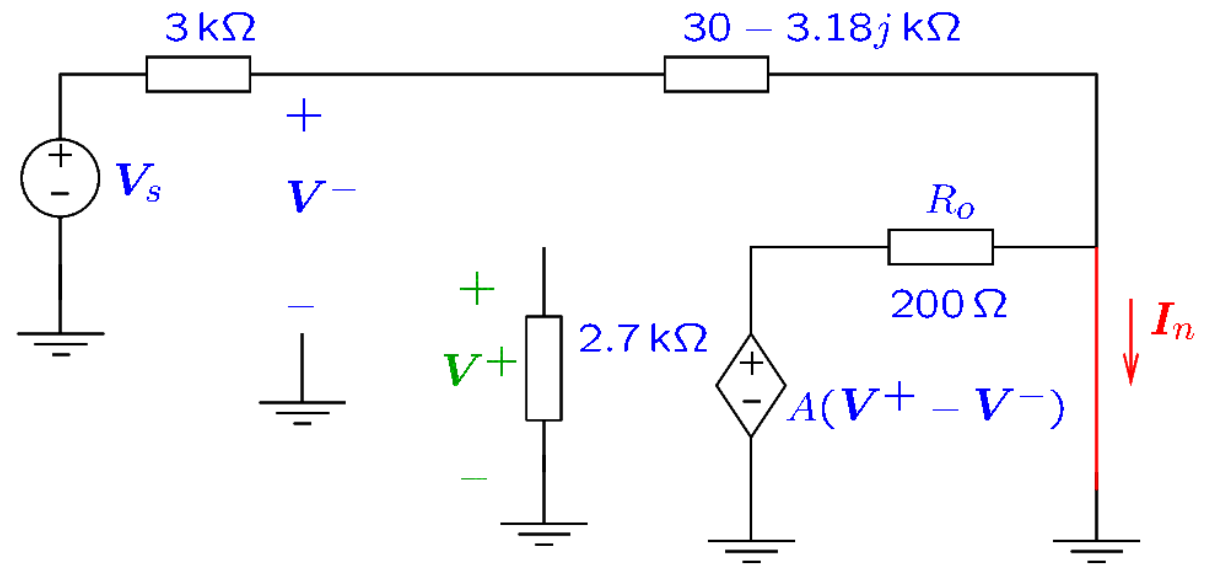
$$Z_{th} = \frac{V_{th}}{I_n} = 104.78 \angle -2.62^\circ \Omega$$



# Thevenin Equivalent—Example 2

- The general method of finding  $Z_{th}$  is with an external source.
- This method is illustrated here.
- By voltage division,

$$V^- = V_x \cdot \frac{3}{3 + 30 - 3.18j}$$


- By KVL,

$$I_x = \frac{V_x}{33 - 3.18j \text{ k}\Omega} + \frac{V_x - (-AV^-)}{200 \Omega}$$

- After substituting  $V^-$ :

$$I_x = V_x \left( \frac{1}{33 - 3.18j \text{ k}\Omega} + \frac{1}{200 \Omega} + \frac{A}{33 - 3.18j \text{ k}\Omega} \cdot \frac{3 \text{ k}\Omega}{200 \Omega} \right)$$
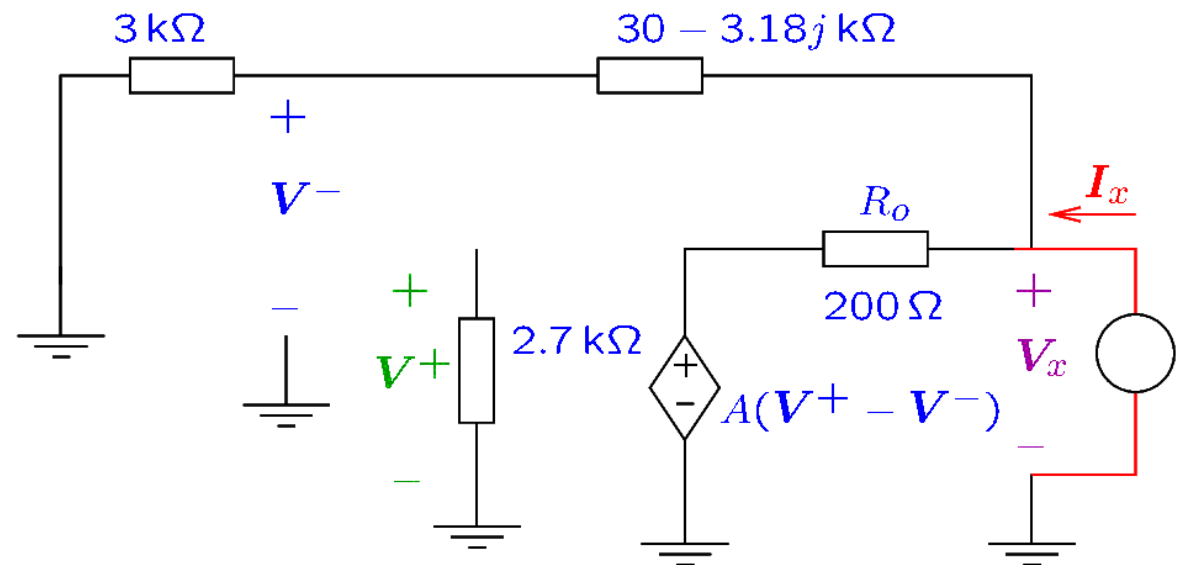
$$\Rightarrow Z_{th} = \frac{V_x}{I_x} = 104.78 \angle -2.62^\circ \Omega$$




# Thevenin Equivalent—Example 3

Repeat the previous example when  $A \rightarrow \infty$ .

- Note that practical operational amplifiers of high gain can be approximated reasonably well using  $A \rightarrow \infty$ .
- The approximation  $A \rightarrow \infty$  is used because it simplifies calculations.
- It implies that

$$V^+ - V^- = \frac{V_o}{A} = 0$$

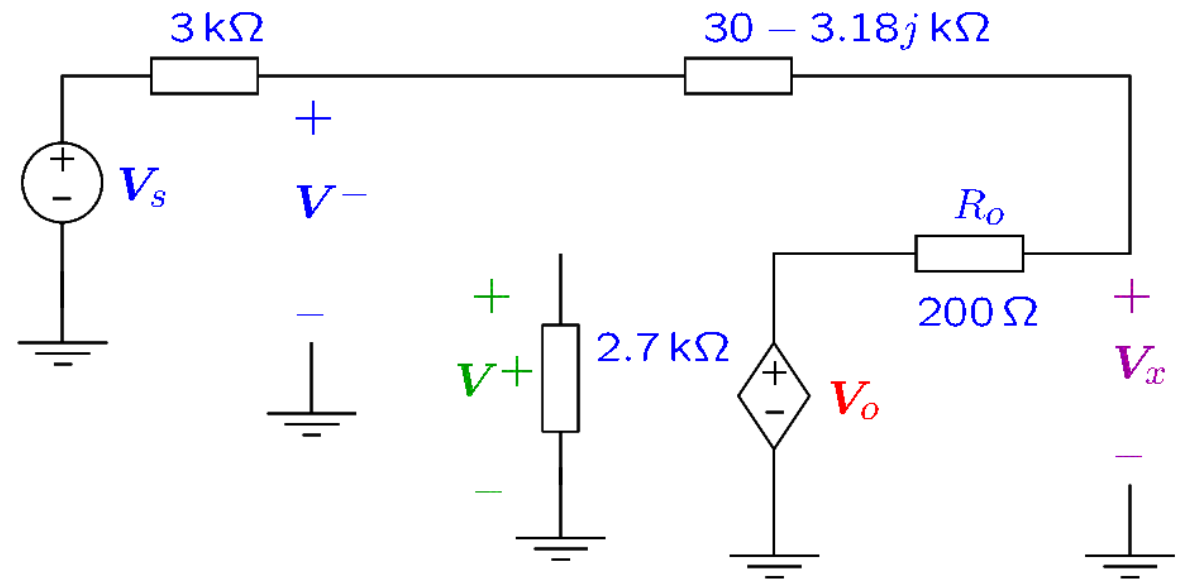- This does not mean that the (+) and (-) terminals of the operational amplifier are shorted!
- Rather, the circuit will adjust  $V_o$  so that  $V^+ = V^-$ .



# Thevenin Equivalent—Example 3


- To find  $V_{th}$ , note that:

$$V^- = V^+ = 0$$

- From nodal analysis:

$$\frac{V_x - 0}{30 - 3.18j} + \frac{V_s - 0}{3} = 0$$
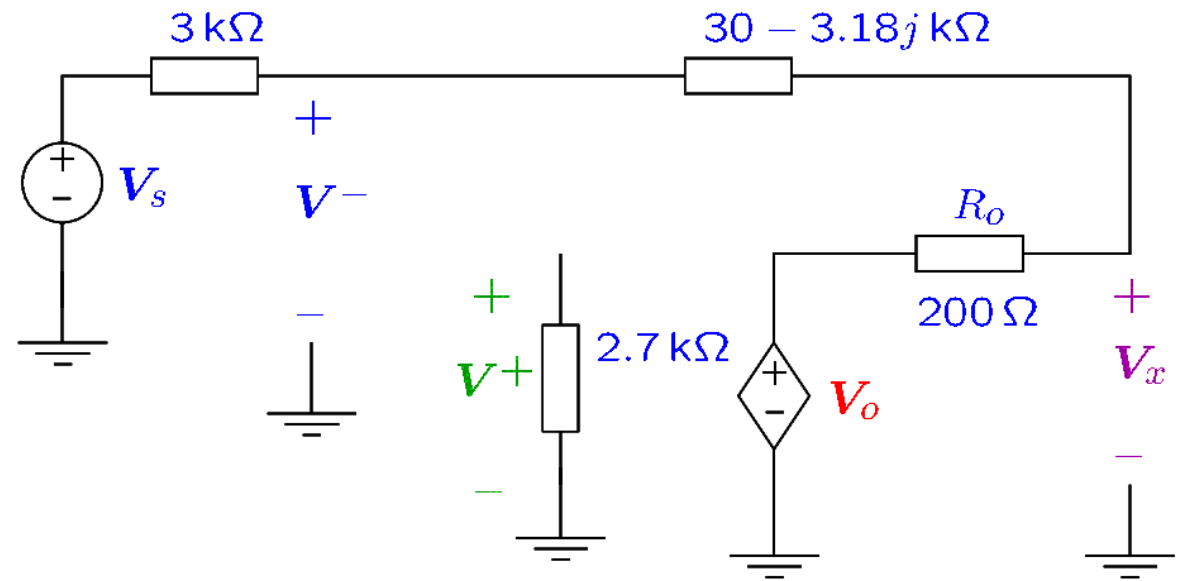
$$\Rightarrow V_{th} = V_x = 402.24 \angle 173.95^\circ \text{ mV}$$



# Thevenin Equivalent—Example 3

- To find  $Z_{th}$ , the short-circuit method will not work! This is because, as we will prove,  $Z_{th} = 0$ .
- The general method of finding  $Z_{th}$  is with an external source.
- This method is illustrated here.
- Voltage division implies that  $V^-$  is a fraction of  $V_x$ . However,  $V^- = V^+ = 0$ . It follows that  $V_x = 0$ .
- The source does not have to output  $I_x = 0$ ; for example, it could be a current source of 1 A. Therefore,

$$Z_{th} = \frac{V_x}{I_x} = 0 \Omega$$

