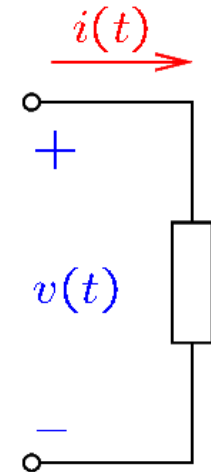


# AC Power

Instantaneous Power, Average Power, RMS Values.

# Instantaneous Power

- The **instantaneous power**  $p(t)$  is the power at time  $t$ .
- It is calculated the same way as for DC circuits:  
$$p(t) = v(t)i(t)$$
- In the figure, since  $i(t)$  enters the component at the terminal where  $v(t)$  has the + sign,  $v(t)i(t)$  is **absorbed** power.
- In the figure, the generated power is  $-v(t)i(t)$ .



---

**Example:**  $v(t) = 30 \cos(\omega t)$  V and  $i(t) = 10 \cos(\omega t + 30^\circ)$  A.


If  $\omega = 400$  rad/s, then the absorbed power at time  $t = 1.2$  s is

$$p(1.2) = 30 \cos(400 \cdot 1.2) \cdot 10 \cos\left(400 \cdot 1.2 + \frac{\pi}{6}\right) = 234 \text{ W.}$$

# Instantaneous Power—Example

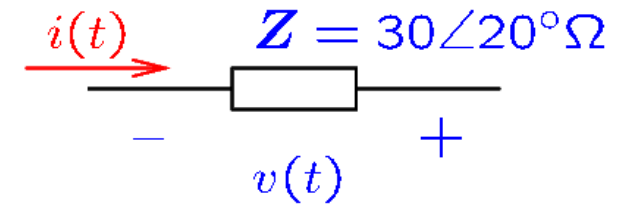*Example:  $i(t) = 10 \cos(\omega t + 30^\circ)$  A. Find the instantaneous generated power at time  $t = 2$  s. Assume  $\omega = 500$  rad/s.*

- $V = -ZI$ , where the minus sign is due to the fact that  $i(t)$  enters the component at the terminal where  $v(t)$  has the  $-$  sign.
- $V = -30\angle 20^\circ \cdot 10\angle 30^\circ = 300\angle -130^\circ$  V.
- $\Rightarrow v(t) = 300 \cos(\omega t - 130^\circ)$  V.
- The absorbed power is  $p(t) = -v(t)i(t)$ .
- The minus sign is because  $i(t)$  enters the component at the terminal where  $v(t)$  has the  $-$  sign.



# Instantaneous Power—Example

- The absorbed power is  $p(t) = -v(t)i(t)$ .

- The generated power is

$$-p(t) = 300 \cos(\omega t - 130^\circ) \cdot 10 \cos(\omega t + 30^\circ)$$


- Substituting  $t = 2$  s and  $\omega = 500$  rad/s,

$$-p(2) = 3000 \cos\left(500 \cdot 2 - 130^\circ \cdot \frac{\pi}{180^\circ}\right) \cos\left(500 \cdot 2 + \frac{\pi}{6}\right)$$

- Therefore, the generated power is  $p_g(2) = 60$  W.

- In other words, the absorbed power is  $p(2) = -60$  W.

# Instantaneous Power

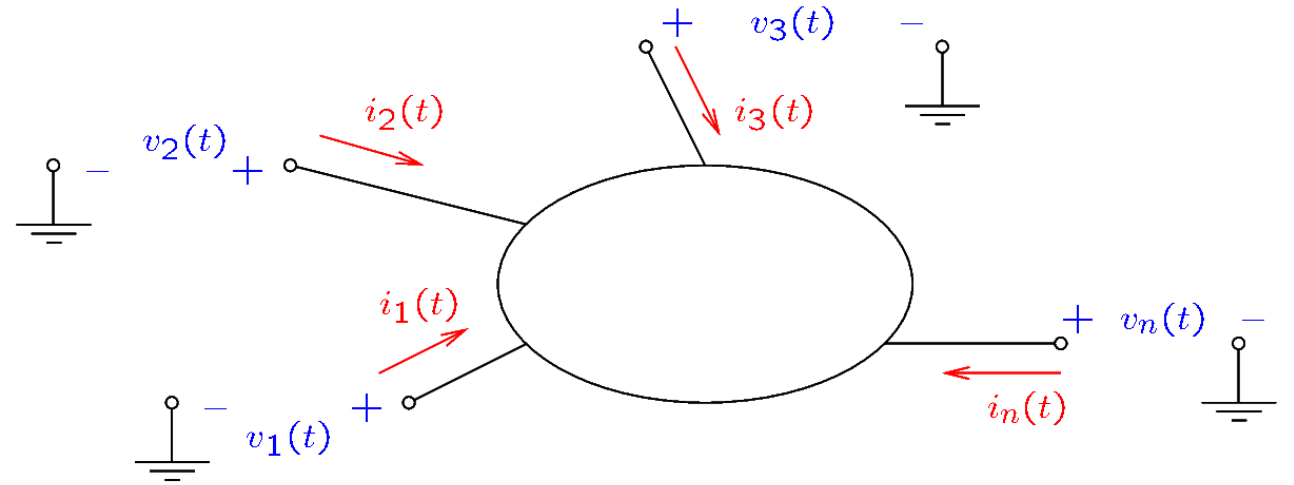


- For components with multiple terminals, the absorbed instantaneous power is

$$p(t) = \sum_{k=0}^n v_k(t) i_k(t)$$

- The product  $v_k(t) i_k(t)$  has the plus sign when the current  $i_k$  enters the component at the terminal where  $v_k$  has the + sign.
- Note that all voltages  $v_k(t)$  are with respect to the *same* GND reference.

# Instantaneous Power—Example

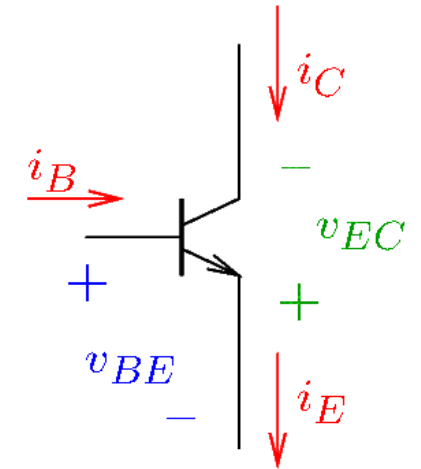*Example: The component shown in the figure is a bipolar transistor operating at  $i_E = 1.04 - 0.502 \cos(\omega t)$  A,  $i_B = 40 - 20 \cos(\omega t)$  mA,  $v_{BE} = 0.7$  V, and  $v_{EC} = -5 \cos(\omega t) - 10$  V. Find the dissipated power when  $i_E$  is maximum.*



- *Using the lower terminal as a reference, the instantaneous power is*

$$p(t) = i_B v_{BE} - i_C v_{EC}.$$

- *By KCL,*

$$i_C = i_E - i_B = 1 - 0.5 \cos(\omega t) \text{ A}.$$

- *$i_E$  is maximum when  $\cos(\omega t) = -1$ , which results in an absorbed power*

$$p = 0.06 \cdot 0.7 - 1.5 \cdot (-5) = 7.54 \text{ W}.$$

# Average Power

- Assuming  $v(t) = V_m \cos(\omega t + \alpha_v)$  and  $i(t) = I_m \cos(\omega t + \alpha_i)$ , the instantaneous power is:

$$p(t) = V_m \cos(\omega t + \alpha_v) I_m \cos(\omega t + \alpha_i)$$

- Applying the formula  $\cos(x) \cos(y) = \frac{1}{2} \cos(x - y) + \frac{1}{2} \cos(x + y)$ :

$$p(t) = \frac{V_m I_m}{2} \cos(\alpha_v - \alpha_i) + \frac{V_m I_m}{2} \cos(2\omega t + \alpha_v + \alpha_i)$$


- We could write  $p(t)$  as

$$p(t) = P + \frac{V_m I_m}{2} \cos(2\omega t + \alpha_v + \alpha_i)$$

where  $P = \frac{V_m I_m}{2} \cos(\alpha_v - \alpha_i)$  is the average of  $p(t)$  and is called **average power**.
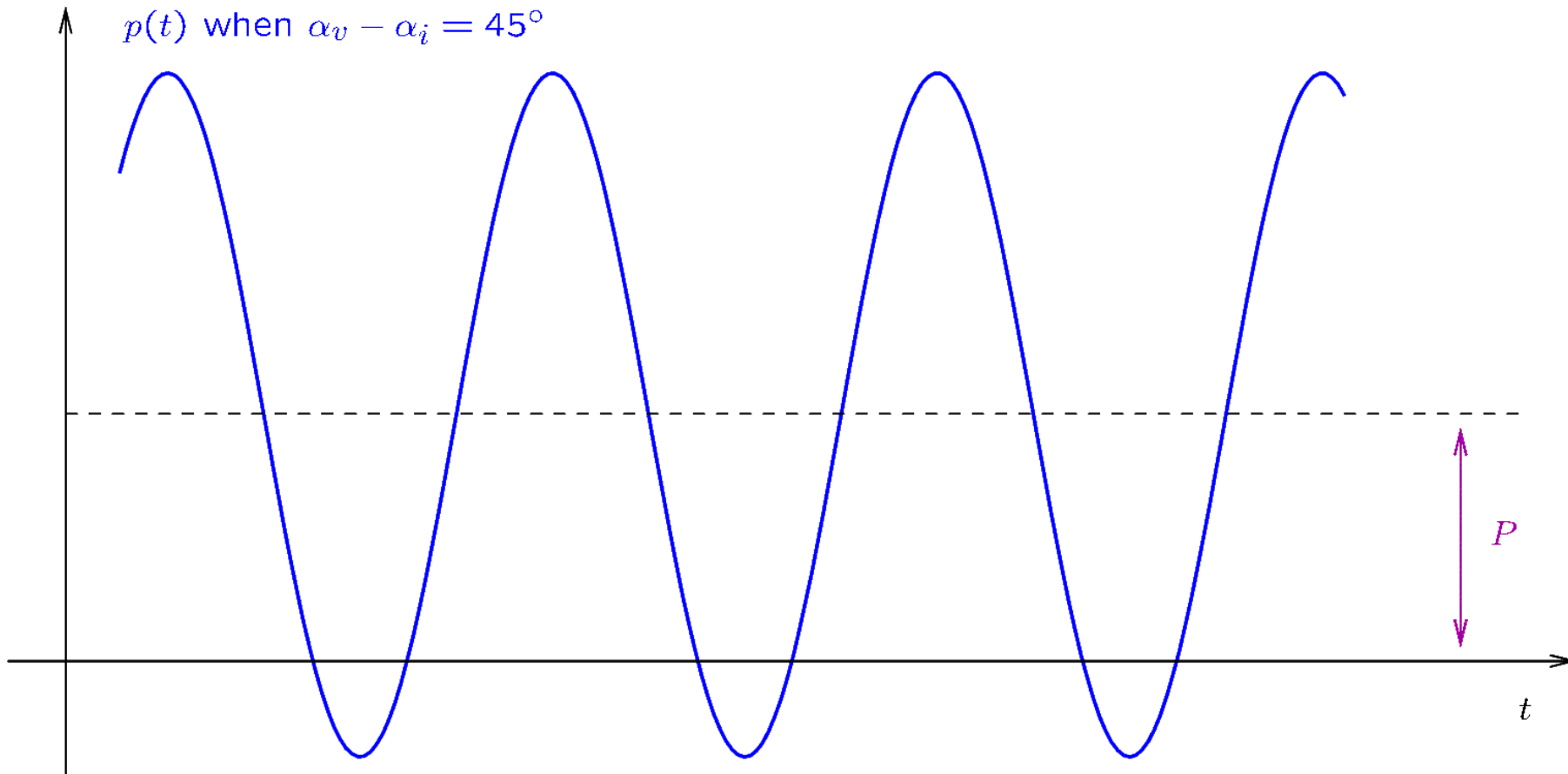
# Average Power

- The instantaneous power  $p(t)$  may have both positive and negative values.
- $P$  is its average of  $p(t)$ .



# Average Power

- In the case of signals that are not periodic, the average power can be calculated with the formula

$$P = \lim_{T \rightarrow \infty} \frac{1}{T} \int_{-T/2}^{T/2} p(t) dt$$

- In the case of periodic signals of period  $T$ , the formula can be simplified to

$$P = \frac{1}{T} \int_{-T/2}^{T/2} p(t) dt$$

- We have shown that if  $v(t) = V_m \cos(\omega t + \alpha_v)$  and  $i(t) = I_m \cos(\omega t + \alpha_i)$ , the average power is:

$$P = \frac{V_m I_m}{2} \cos(\alpha_v - \alpha_i)$$

- This formula is simplest when written in terms of *rms voltages and currents*.

# RMS Voltages and Currents

- Let  $u(t)$  be a current or a voltage.
- The *root mean square value* of  $u(t)$ , also known as *rms value* or *effective value* is informally defined as

$$U_{rms} = \sqrt{\text{Average of } u(t)^2}$$

- Formally,

$$U_{rms} = \sqrt{\lim_{T \rightarrow \infty} \frac{1}{T} \int_{-T/2}^{T/2} u(t)^2 dt}$$

- If  $u(t)$  is periodic and has the period  $T$ , the formula can be simplified to

$$U_{rms} = \sqrt{\frac{1}{T} \int_{-T/2}^{T/2} u(t)^2 dt}$$

- If  $u(t) = U_m \cos(\omega t + \alpha)$ , then  $U_{rms} = U_m / \sqrt{2}$ .

# RMS Voltages and Currents

- Let  $V_{rms}$  be the rms value of  $v(t) = V_m \cos(\omega t + \alpha_v)$  and  $I_{rms}$  the rms value of  $i(t) = I_m \cos(\omega t + \alpha_i)$ . Then:

$$V_{rms} = \frac{V_m}{\sqrt{2}} \text{ and } I_{rms} = \frac{I_m}{\sqrt{2}}$$

- The **average power** is:

$$P = \frac{V_m I_m}{2} \cos(\alpha_v - \alpha_i) = V_{rms} I_{rms} \cos(\alpha_v - \alpha_i)$$

# RMS Voltages and Currents

- *The rms value of a signal  $u(t)$  is the DC value that would produce the same average power on a resistor as  $u(t)$ .*
  - *The rms value is the DC equivalent of an AC signal.*
- *The wall outlet voltage is 120 V **rms**!*
  - *The amplitude of the wall outlet voltage is therefore  $120\sqrt{2} = 169.71$  V.*
- *When measuring the value of AC signals, multimeters display the **rms** value.*


# RMS Voltages and Currents—Examples

Example: Assume  $v(t) = 50 \cos(\omega t + 30^\circ)$  V and  $i(t) = 4 \cos(\omega t + 75^\circ)$  A.

- The rms value of  $i(t)$  is  $I_{rms} = \frac{4}{\sqrt{2}} = 2.83$  A.
- The rms value of  $v(t)$  is  $V_{rms} = \frac{50}{\sqrt{2}} = 35.35$  V.
- The average absorbed power is  $P = -V_{rms}I_{rms}\cos(\alpha_v - \alpha_i)$ .
- The minus sign is due to the fact that  $i(t)$  enters the component at the terminal where  $v(t)$  has the minus sign.
- Substituting  $\alpha_v = 30^\circ$  and  $\alpha_i = 75^\circ$ :

$$P = -\frac{50}{\sqrt{2}} \cdot \frac{4}{\sqrt{2}} \cdot \cos(30^\circ - 75^\circ) = -70.71 \text{ W}.$$

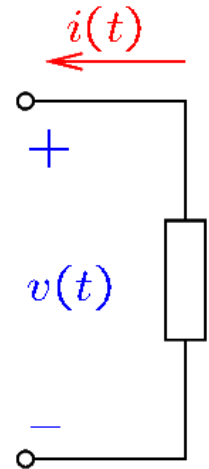- Thus, the component generates on the average  $P_g = -P = 70.71$  W.



# RMS Voltages and Currents—Examples


*Example: Find the rms value of the DC voltage  $v(t) = 3\text{ V}$ .*

- $V_{rms} = \sqrt{\text{Average of } 3^2} = \sqrt{3^2} = 3\text{ V}.$

---

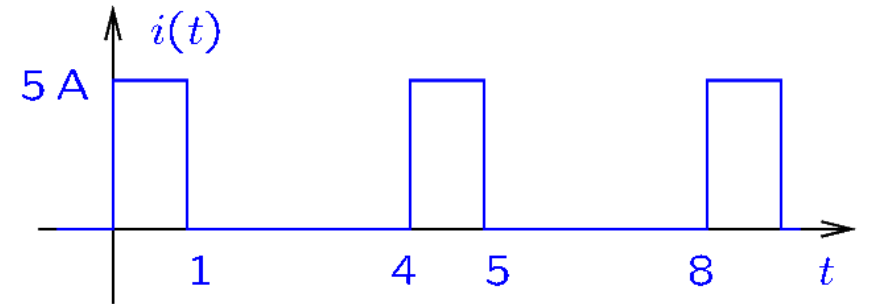
*Example: Find the rms value of the shown current.*

- $I_{rms} = \sqrt{\text{Average of } i^2} = \sqrt{5^2 \cdot 1/4} = 2.5\text{ A}.$



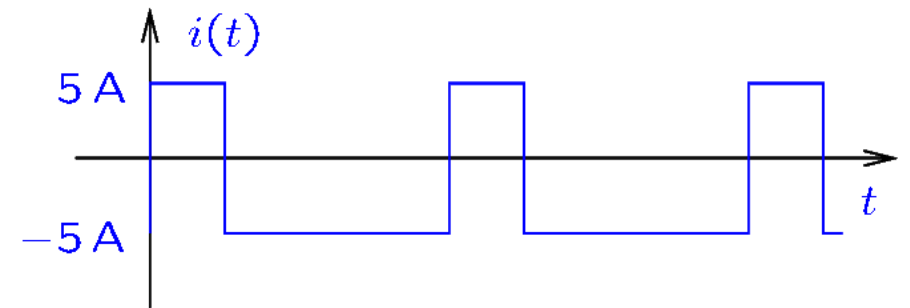*Example: Find the rms value of the shown current.*

- $I_{rms} = \sqrt{\text{Average of } i^2} = \sqrt{\text{Average of } 5^2} = \sqrt{5^2} = 5\text{ A}.$



# RMS Voltages and Currents—Examples

*Example: Find the rms value of the DC voltage  $v(t) = 5 \cos(\omega t) + 3 \text{ V}$ .*

- $$\begin{aligned} V_{rms} &= \sqrt{\text{Average of } (5 \cos(\omega t) + 3)^2} \\ &= \sqrt{\text{Average of } 25 (\cos(\omega t))^2 + 9 + 30 \cos(\omega t)} \\ &= \sqrt{\frac{25}{2} + 9 + 0} = 4.63 \text{ V}. \end{aligned}$$