

AC Power—Part 3

Apparent Power, Power Factor, and Power Factor Correction

Power—Review

- Let $v(t) = V_m \cos(\omega t + \alpha_v)$ and $i(t) = I_m \cos(\omega t + \alpha_i)$.
- The **instantaneous power** $p(t)$ is the power at time t .
- The absorbed instantaneous power is:

$$p(t) = v(t)i(t)$$


- The **apparent power** is measured in $V \cdot A$ (Volt-Amperes) and has the formula:

$$S = V_{rms} I_{rms}$$

- The average of $p(t)$ is the **average power**:

$$P = S \cdot \cos(\alpha_v - \alpha_i)$$

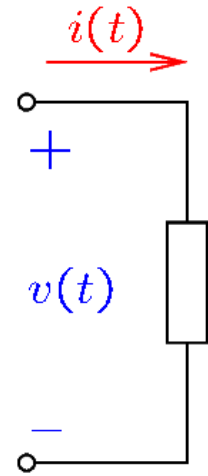- The **power factor** is $PF = \cos(\alpha_v - \alpha_i)$.
- When specifying the power factor, we indicate whether the current $i(t)$ is **lagging** or **leading** the voltage $v(t)$.




Power—Physical Meaning

- Let $v(t) = V_m \cos(\omega t + \alpha_v)$ and $i(t) = I_m \cos(\omega t + \alpha_i)$.
- The instantaneous power $p(t) = v(t)i(t)$ can also be written as:


$$p(t) = \frac{V_m I_m}{2} \cos(\alpha_v - \alpha_i) + \frac{V_m I_m}{2} \cos(2\omega t + \alpha_v + \alpha_i)$$
$$\Rightarrow p(t) = P + S \cdot \cos(2\omega t + \alpha_v + \alpha_i)$$

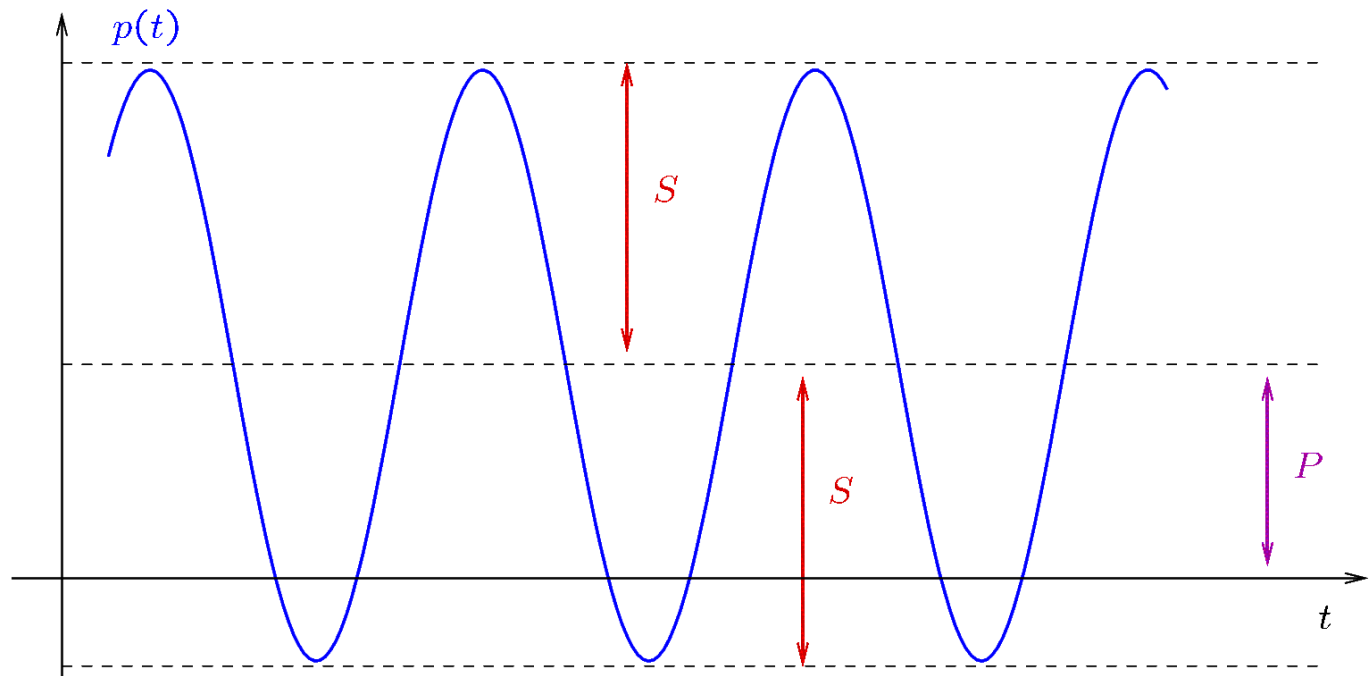- P is the *average* of $p(t)$.
- S is the *amplitude* of $p(t)$.




Power—Physical Meaning

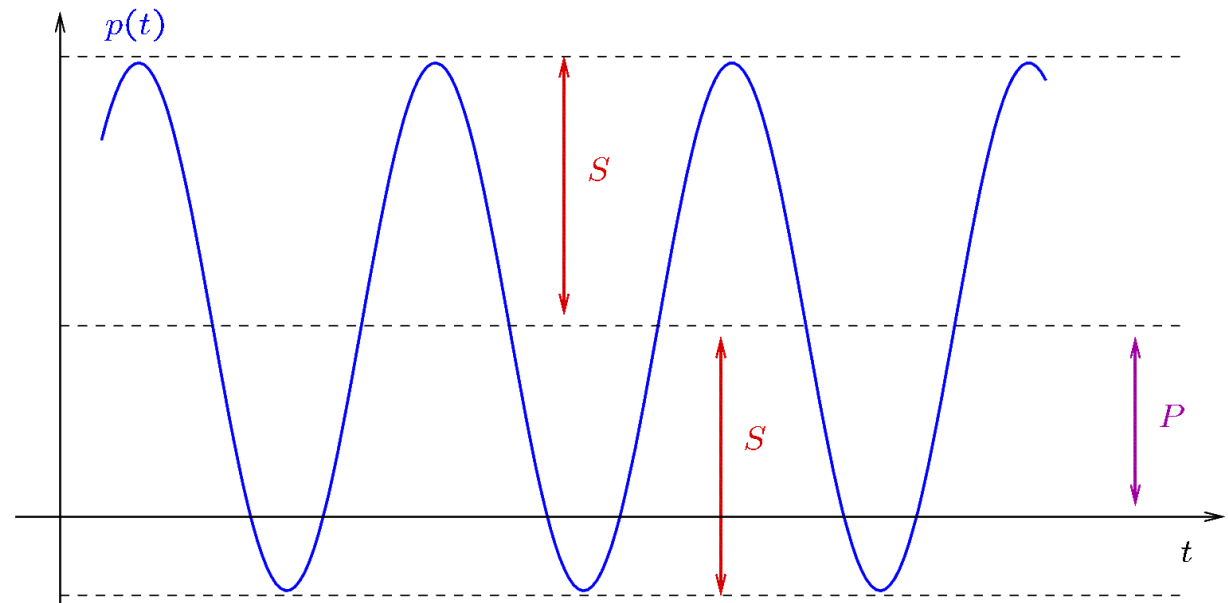- When $p(t) > 0$, energy is transferred from the source to the load.
- When $p(t) < 0$, energy is transferred backwards, from the load to the source.
- On the average, energy is transferred from the source to the load at the rate P .
- Practical systems cannot transfer energy without losses.
- A system in which energy keeps going back and forth between the source and the load is wasteful!




Power—Physical Meaning

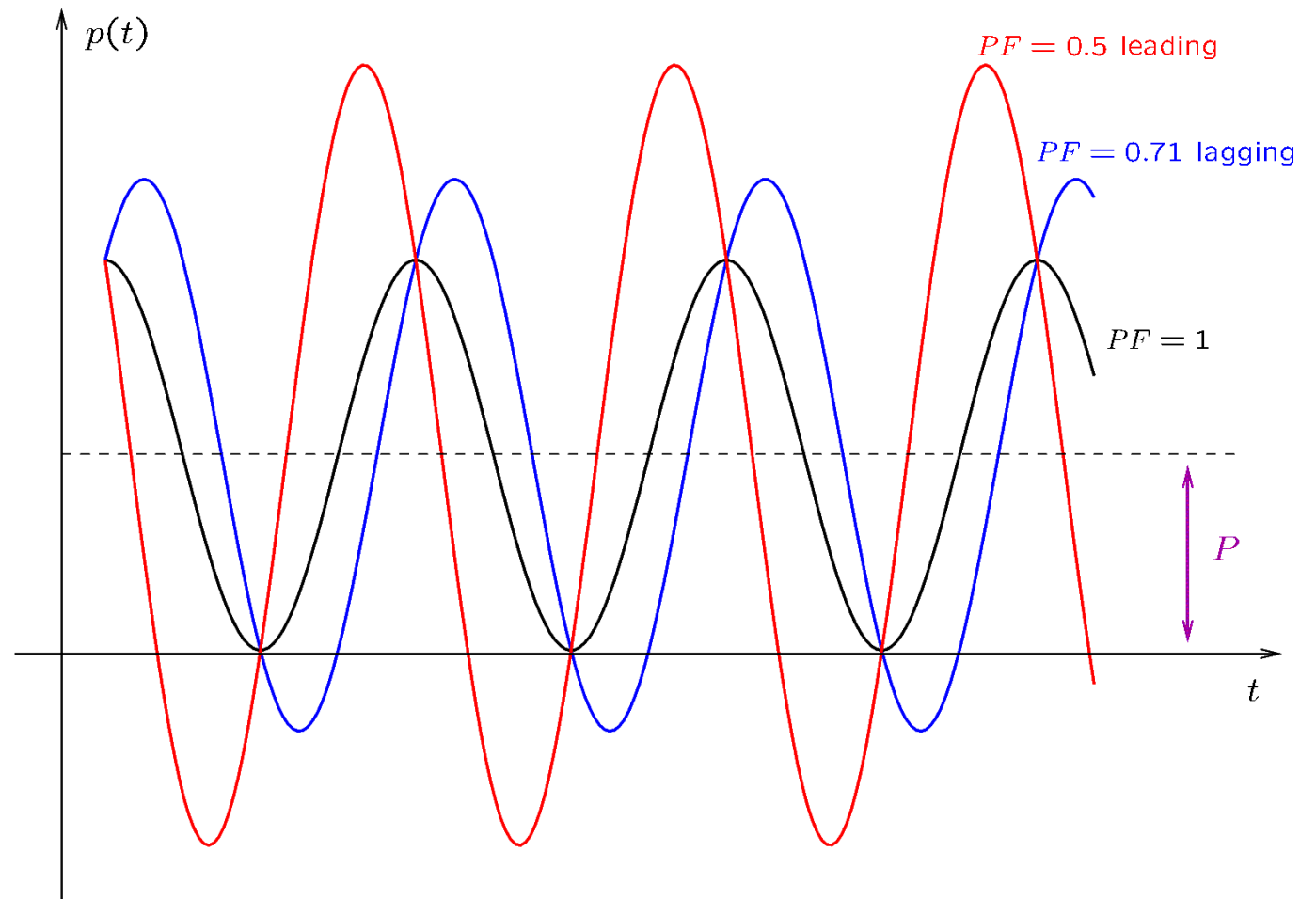- A given average power P can be delivered at any non-zero power factor.
- The lower the power factor, the bigger the amplitude of $p(t)$.
- A big amplitude of $p(t)$ indicates a big current.
- Transmission losses are proportional to the square of the current.
- Clearly, the best curve is the one with $PF = 1$.
- When $PF = 1$, the energy goes from the source to the load and never backwards.



Power Factor Correction

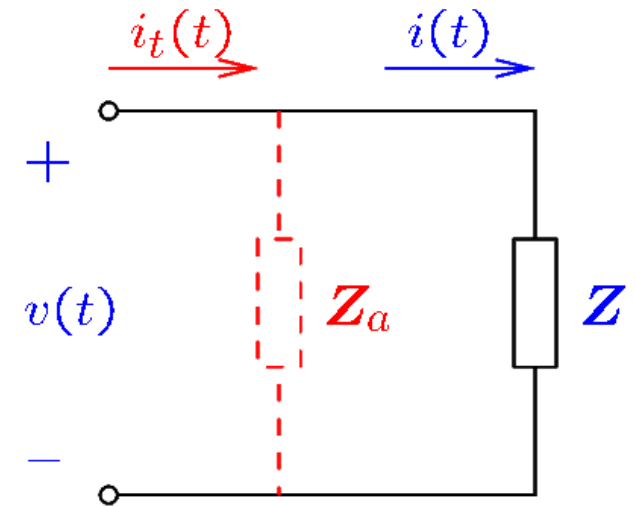- In power factor correction, an additional component Z_a is connected in parallel to a load Z so as to ensure an overall $PF = 1$.
- Power factor correction minimizes the current: the total current i_t will be smaller than i and will have the least value when $PF = 1$.
- Because power factor correction reduces losses, it is important in practice.





Power Factor Correction Methods

Method 1: Using V as a reference, sketch a phasor diagram. Select Z_a so that $I_Y = -I_a$.

Method 2: Use $Z_a = -\frac{1}{jB}$, where B is the susceptance of Z .

Method 3: Select Z_a so as to cancel the *reactive power* of Z . This method will be studied in a future lecture.

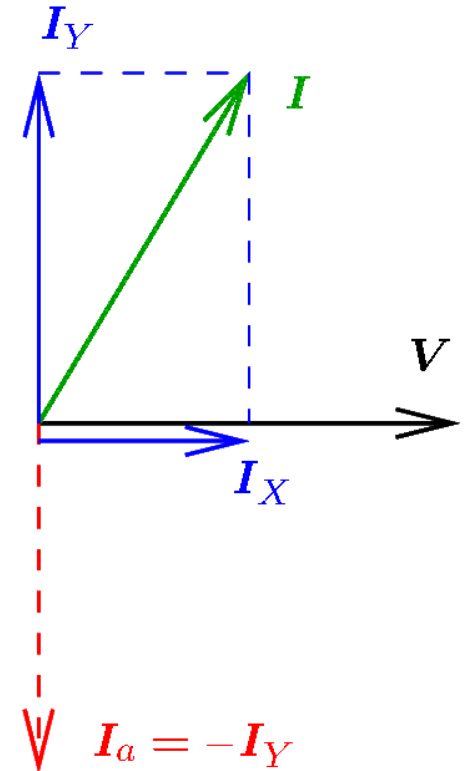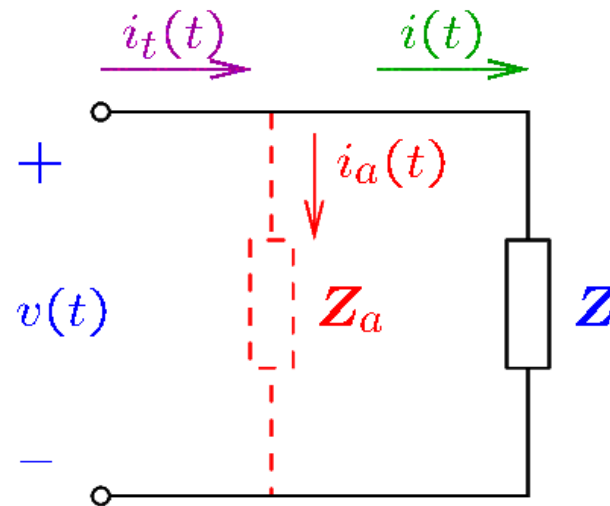



Example 1

Assume $v(t) = 200 \cos(\omega t) V$ and $i(t) = 20 \cos(\omega t + 60^\circ) A$.
The frequency is 60 Hz. Find Z_a that corrects the power factor.

- Note that $I = 20 \angle 60^\circ$.
- Therefore, $I_X = 20 \cos 60^\circ = 10 A$ and $I_Y = 20 \sin 60^\circ \angle 90^\circ = 10\sqrt{3} \angle 90^\circ A$.
- $I_a = -I_Y = 10\sqrt{3} \angle -90^\circ A$.
- $Z_a = \frac{V}{I_a} = \frac{200 \angle 0^\circ}{10\sqrt{3} \angle -90^\circ} = \frac{20j}{\sqrt{3}}$.
- Z_a corresponds to an inductor of value

$$L = \frac{Z_a}{j\omega} = \frac{20}{2\pi 60 \sqrt{3}} = 30.63 \text{ mH}.$$

- By power factor correction, the total current was reduced to $i_t(t) = i_x(t) = 10 \cos(\omega t) A$, two times smaller than $i(t)$!

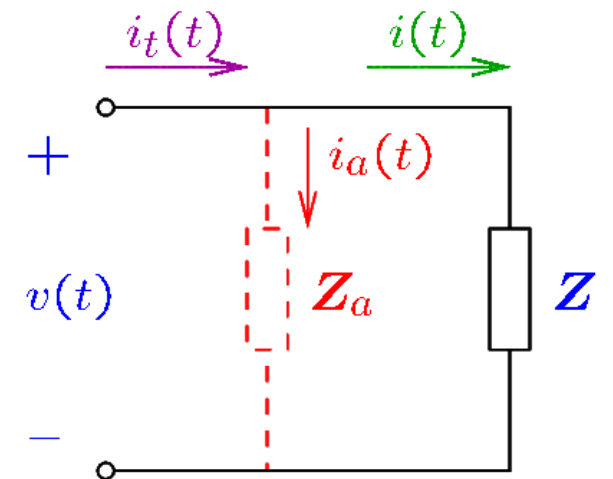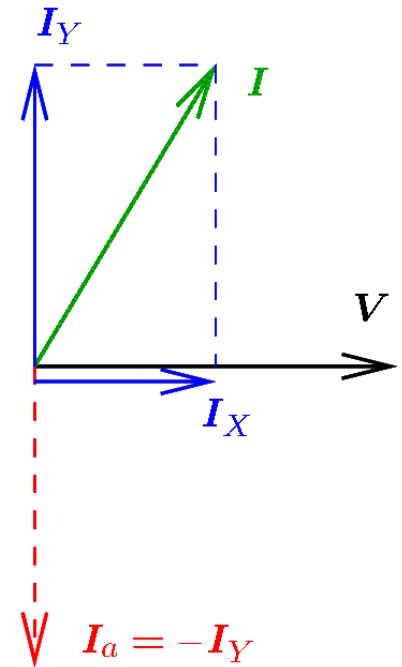


Example 2

Assume $v(t) = 200 \cos(\omega t)$ V and $i(t) = 20 \cos(\omega t - 60^\circ)$ A. The frequency is 60 Hz. Find Z_a that corrects the power factor using the second method.

- Note that $I = 20 \angle -60^\circ$.
- The admittance is $Y = \frac{I}{V} = \frac{20 \angle -60^\circ}{200 \angle 0^\circ} = 0.1 \angle -60^\circ \Omega^{-1}$.
- The susceptance is $B = 0.1 \sin(-60^\circ) \Omega^{-1}$.
- $Z_a = -\frac{1}{jB} = \frac{1}{j0.1\sqrt{3}/2} \Omega$.
- Z_a corresponds to a capacitor of value

$$C = \frac{1}{j\omega Z_a} = \frac{0.1\sqrt{3}/2}{2\pi 60} = 229.72 \mu\text{F}.$$

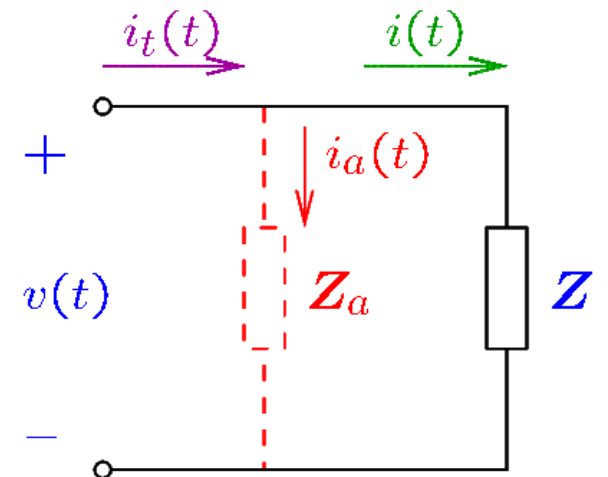

Example 3

Assume $v(t) = 200 \cos(\omega t)$ V and $i_1(t) = 20 \cos(\omega t - 45^\circ)$ A. The second load absorbs 5 kW at a power factor of 0.5 lagging. What is the power factor of the source?

- $\frac{|I_2|}{\sqrt{2}} = \frac{5 \text{ kW}}{\frac{200 \text{ V}}{\sqrt{2}} \cdot 0.5} \Rightarrow |I_2| = 100 \text{ A}.$
- The angle of I_2 is derived from
$$\alpha_v - \alpha_{i_2} = \cos^{-1} 0.5 = \pm 60^\circ.$$
- Since I_2 is lagging, $\alpha_v - \alpha_{i_2} = +60^\circ.$
- Thus, $I_2 = 100 \angle -60^\circ \text{ A}.$
- $I = I_1 + I_2 = 20 \angle -45^\circ + 100 \angle -60^\circ = 119.43 \angle -57.52^\circ \text{ A}.$
- The power factor is

$$PF = \cos(57.52^\circ) = 0.537 \text{ lagging}.$$

