

THREE PHASE SYSTEMS

An Introduction

Introduction


- Power is usually transmitted in AC form using three phases.
- The voltage of each phase with respect to the common reference (called *neutral*) is the same, excepting the phase angle.
- Denoting by **a**, **b**, and **c** the three phases:

$$v_{an}(t) = V_m \cos(\omega t)$$

$$v_{bn}(t) = V_m \cos(\omega t - 120^\circ)$$

$$v_{cn}(t) = V_m \cos(\omega t + 120^\circ)$$

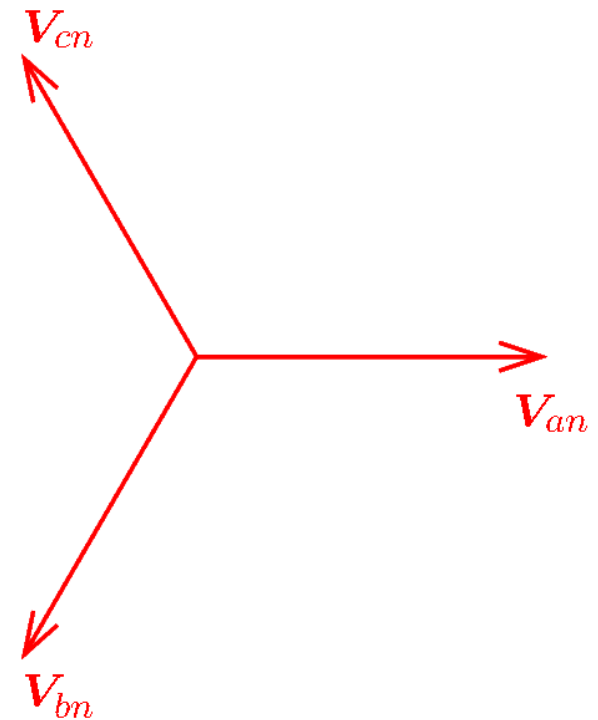- In a phasor diagram, the three voltages are three vectors at 120° each from the other.




Introduction

- From a practical standpoint, three phase voltage is easily generated.
 - In a synchronous generator, coils at 120° from each other will naturally generate three phase voltage.
- For the same amount of power, a three phase power transmission system needs less copper than a single phase system.
 - This means that a three phase power transmission system is cheaper than a single phase system.


Definitions

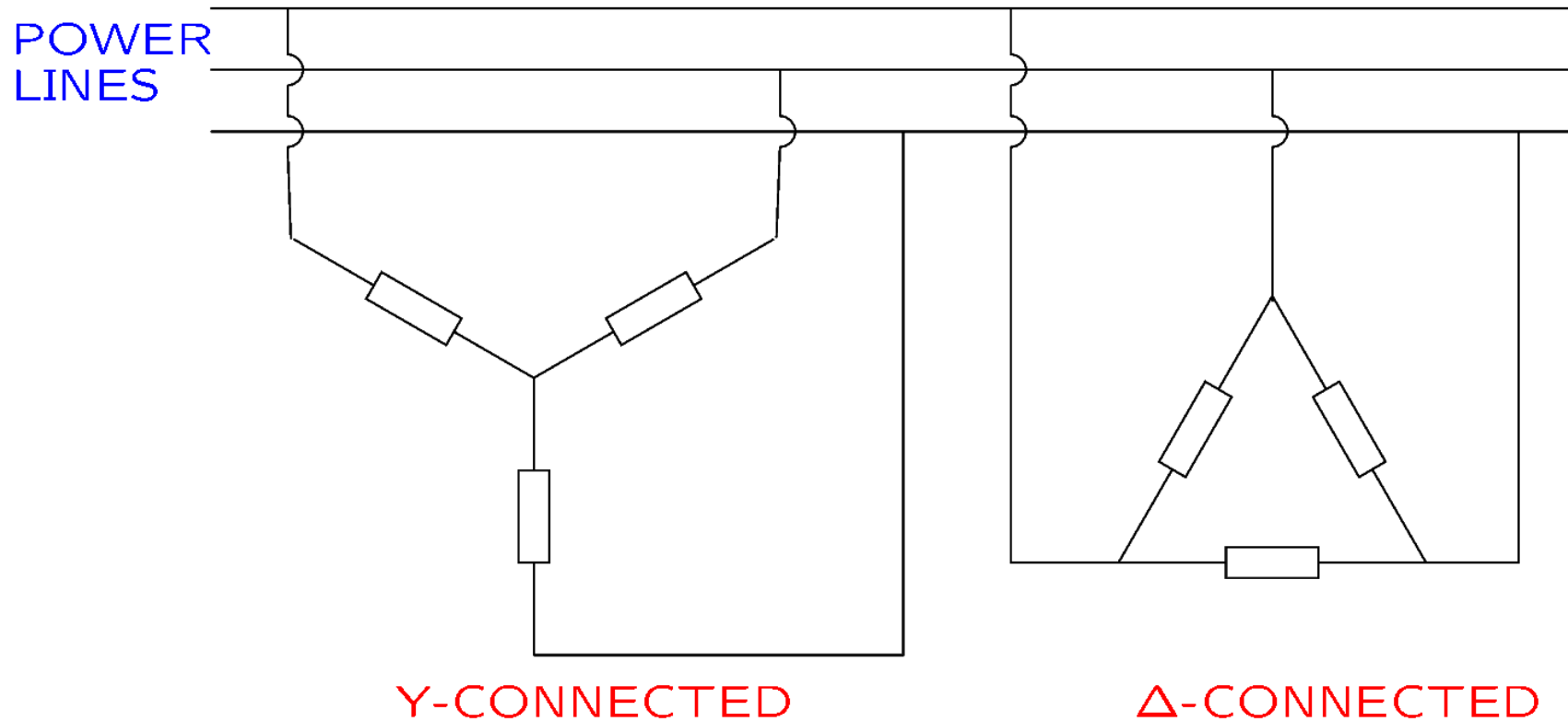- In a three phase system, sources and loads are connected in the *wye (Y) configuration* or the *delta (Δ) configuration*.



Definitions

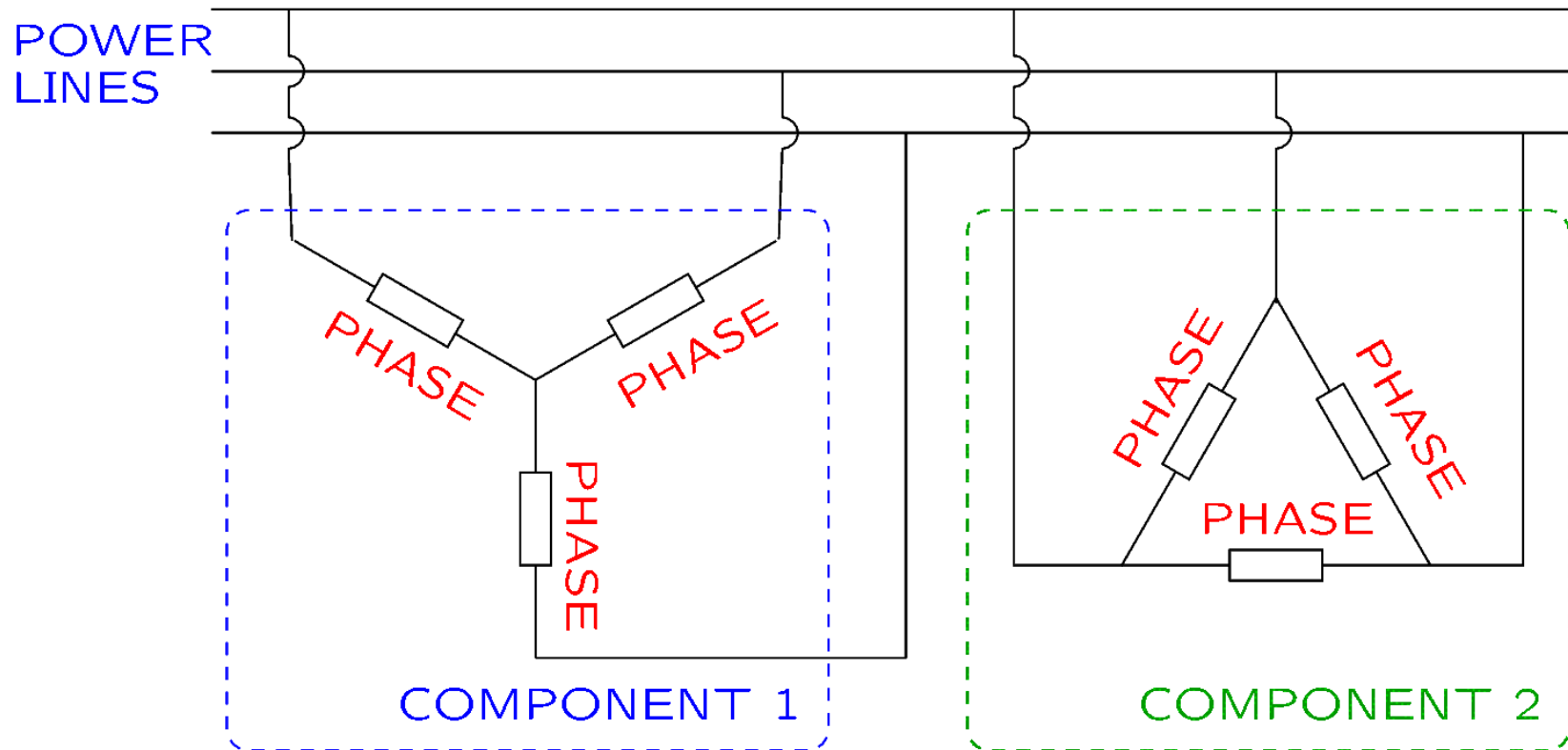
- A three phase component can be represented with three subcomponents, called *phases*, connected in Y or Δ .



Definitions—Currents

- The current flowing through a phase is called *phase current*.
- The current flowing through a conductor that powers a component is called *line current*.

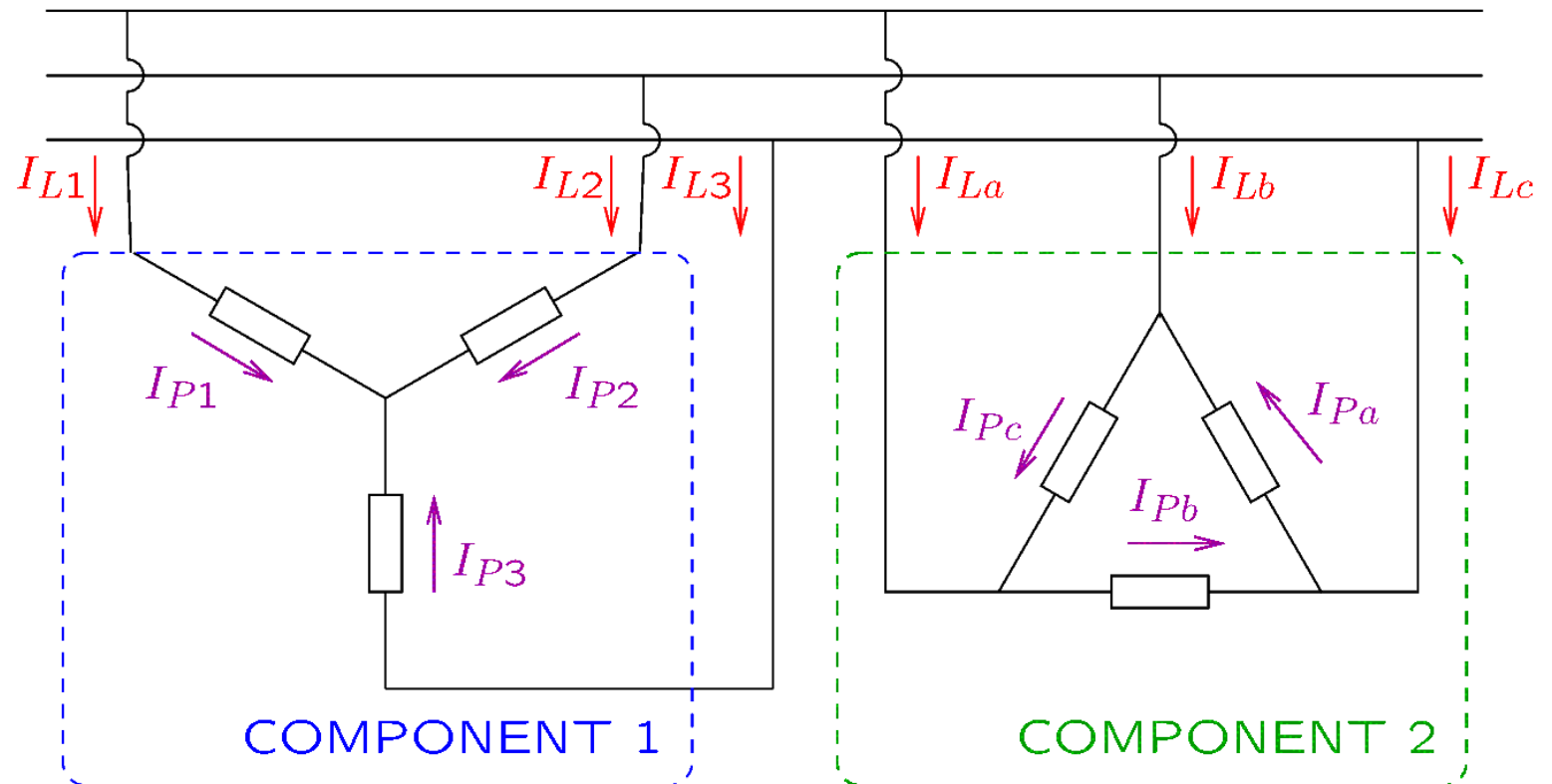
- In the figure, the phase currents are:
 - I_{P1}, I_{P2}, I_{P3}
 - I_{Pa}, I_{Pb}, I_{Pc}
- The line currents are:
 - I_{L1}, I_{L2}, I_{L3}
 - I_{La}, I_{Lb}, I_{Lc}



Definitions—Currents

- For a Y -connected component, phase and line currents are identical.
- For a Δ -connected component, the rms values are related by $I_L = \sqrt{3}I_P$.

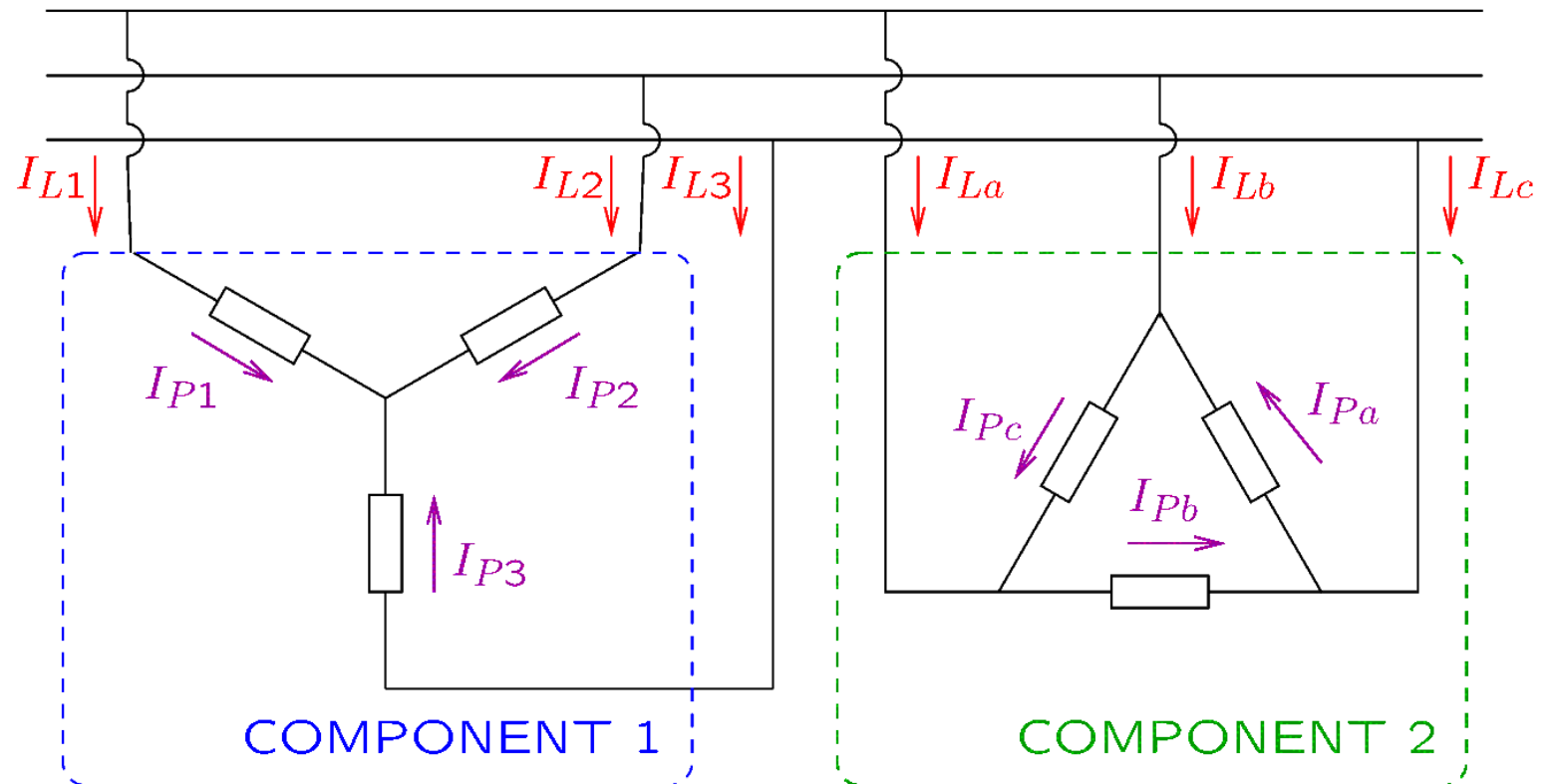
- In the figure, the phase currents are:
 - I_{P1}, I_{P2}, I_{P3}
 - I_{Pa}, I_{Pb}, I_{Pc}
- The line currents are:
 - I_{L1}, I_{L2}, I_{L3}
 - I_{La}, I_{Lb}, I_{Lc}



Definitions—Voltages

- The voltage on a phase is called *phase voltage*.
- The voltage between two power lines is called *line-to-line voltage*, or shortly, *line voltage*.

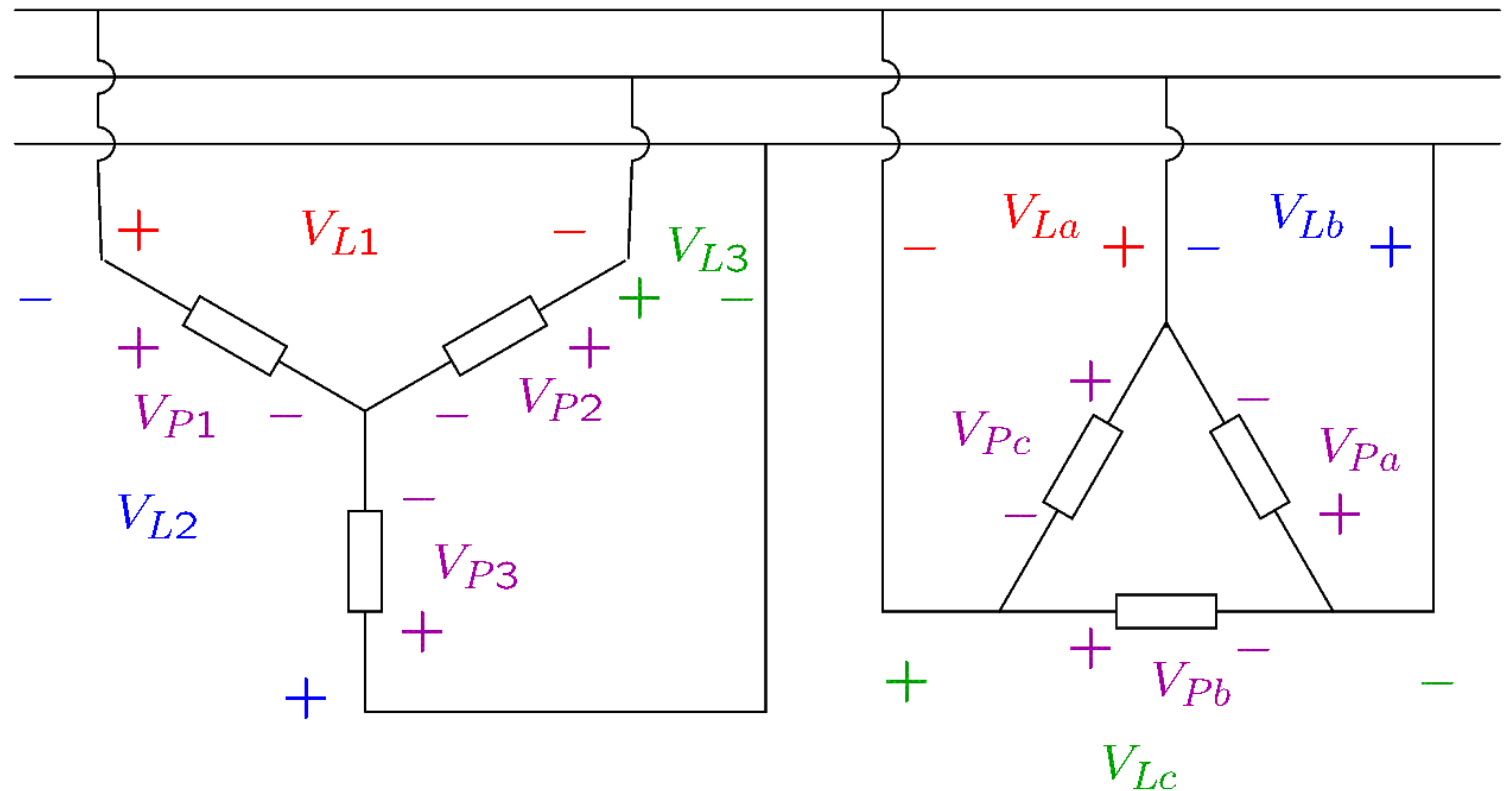
- In the figure, the phase voltages are:
 - V_{P1}, V_{P2}, V_{P3}
 - V_{Pa}, V_{Pb}, V_{Pc}
- The line voltages are:
 - V_{L1}, V_{L2}, V_{L3}
 - V_{La}, V_{Lb}, V_{Lc}



Definitions—Voltages

- For a Δ -connected component, phase and line voltages are identical.
- For a Y -connected component, the rms values are related by $V_L = \sqrt{3}V_P$.

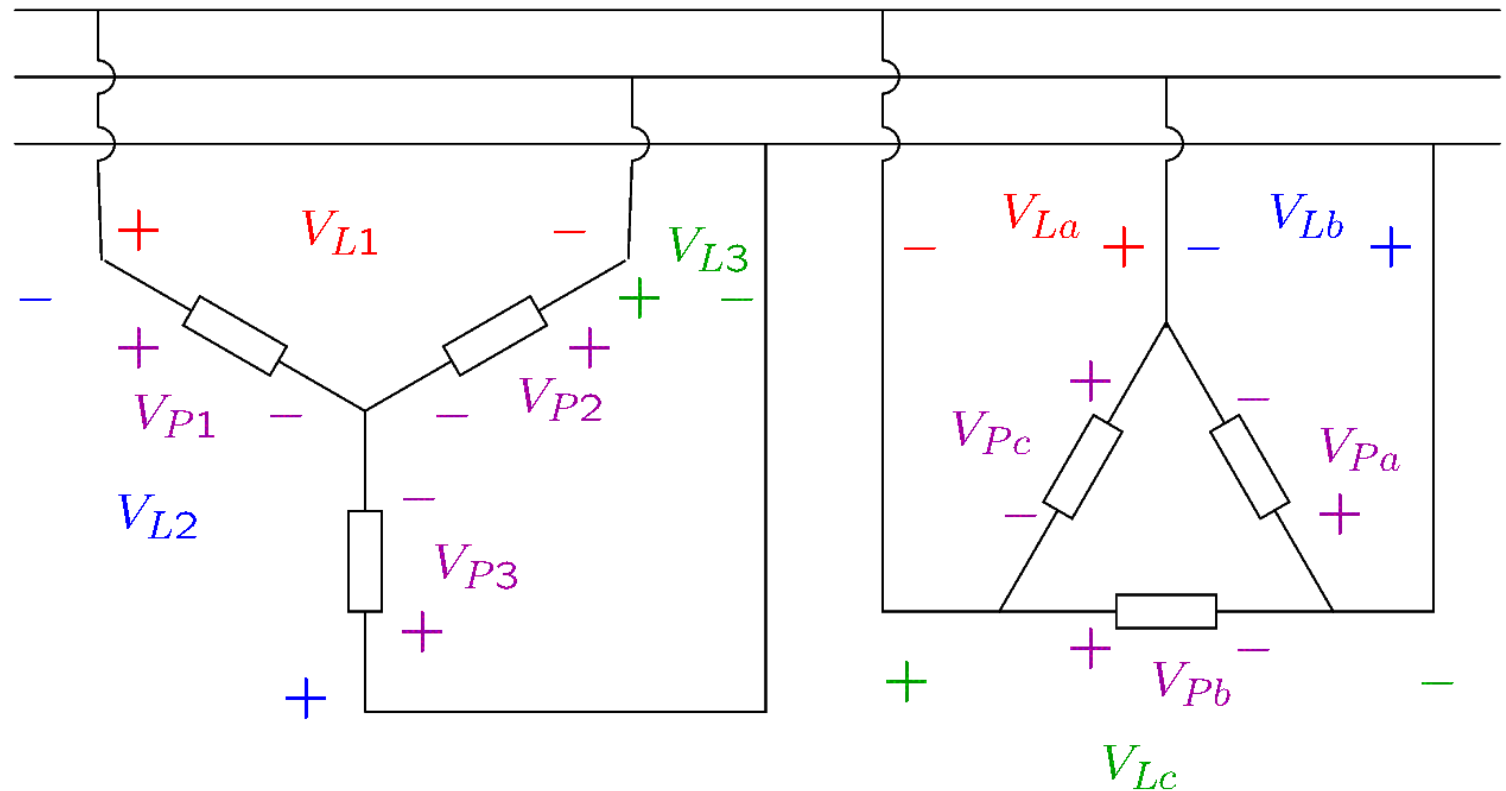- In the figure, the phase voltages are:
 - V_{P1}, V_{P2}, V_{P3}
 - V_{Pa}, V_{Pb}, V_{Pc}
- The line voltages are:
 - V_{L1}, V_{L2}, V_{L3}
 - V_{La}, V_{Lb}, V_{Lc}



Definitions—Balanced System


A three phase system is **balanced** if all of the following apply:

- The phases of the source are 120° out of phase.
- The phases of the source are identical, except for being 120° out of phase.
- The phases of the load are identical.


We will normally assume balanced systems.

Notation

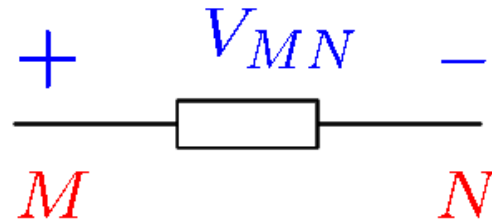- Let M and N denote the terminals of a circuit element.
- V_{MN} will be the voltage between M and N with $+$ at M and $-$ at N .



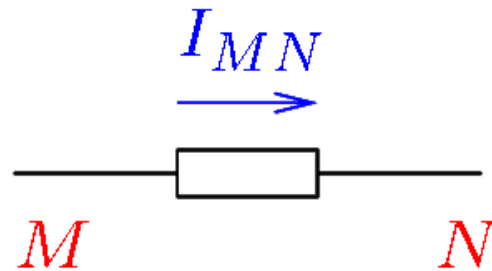- I_{MN} will be the current flowing from M to N .



Convention


- For three phase source of voltage, we will use the convention:

$$v_{an}(t) = V_m \cos(\omega t)$$

$$v_{bn}(t) = V_m \cos(\omega t - 120^\circ)$$


$$v_{cn}(t) = V_m \cos(\omega t + 120^\circ)$$

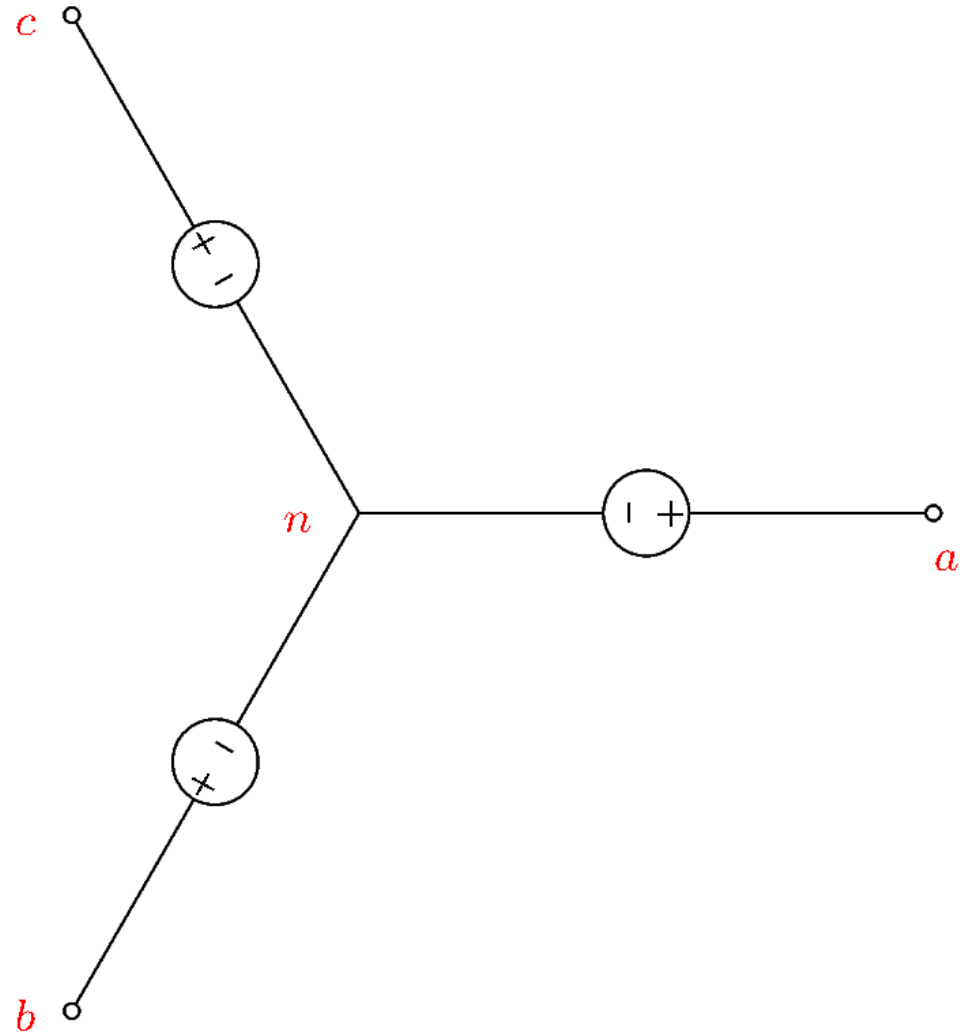- This naming convention is known as the *positive phase sequence*.
- The negative phase sequence has $b \leftrightarrow c$.
- For a Y -connected source, the node n is called *neutral*.



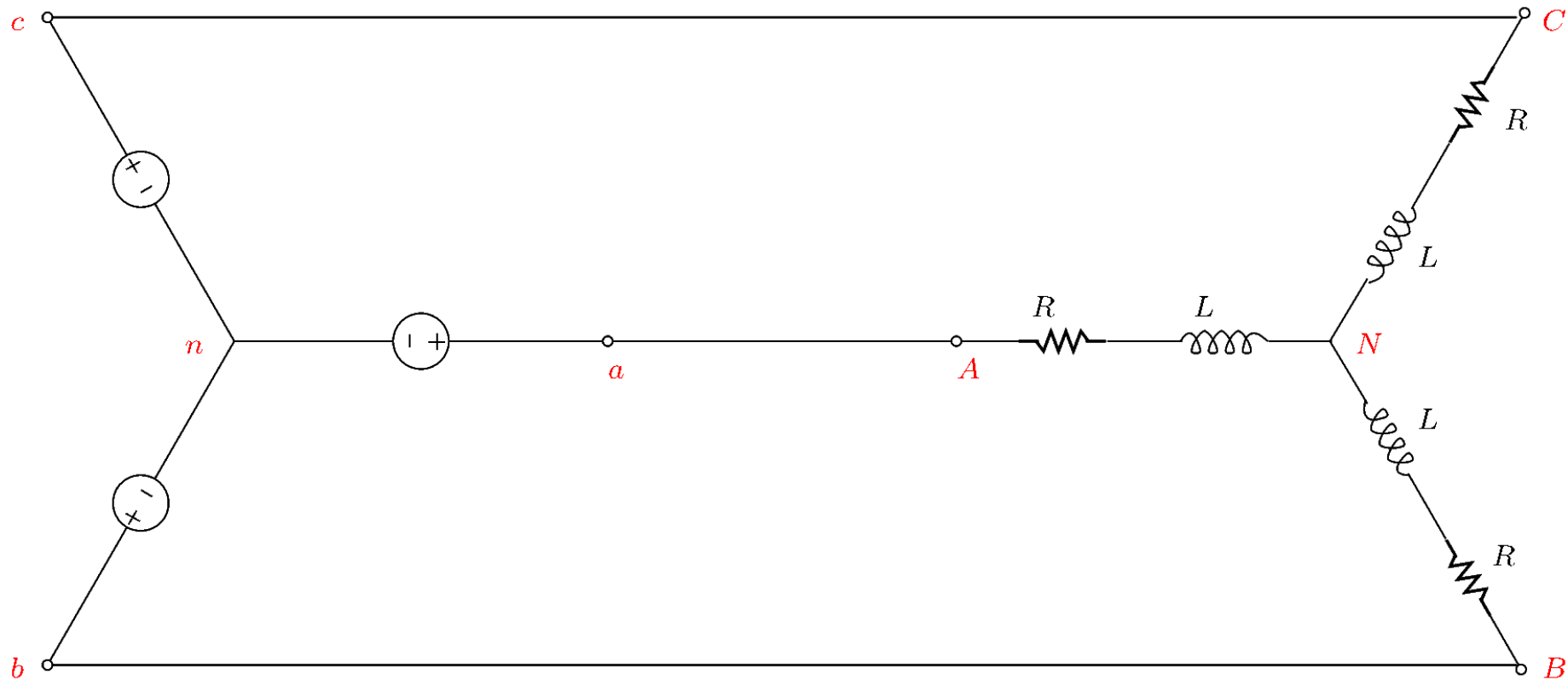
Example

The following balanced system has a line voltage of 500 V rms , $R = 10\ \Omega$, and inductors of reactance $X_L = 20\ \Omega$. Find the current $i_{AN}(t)$.



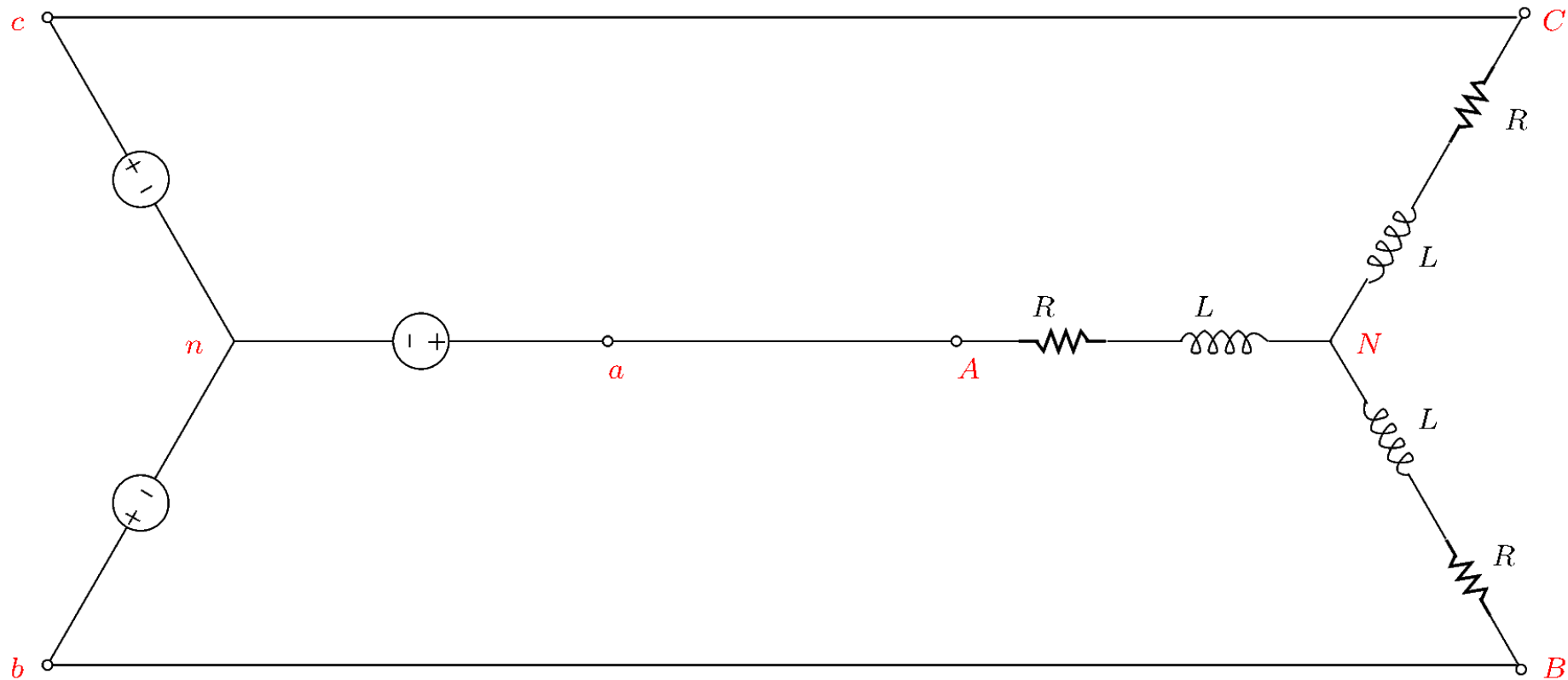Example (Continued)

- Note that for a balanced system, the nodes n and N are at the same potential: $V_{nN} = 0$.
- For a balanced system, the equivalent circuit per phase may be used.



Example (Continued)

- *In the equivalent circuit per phase:*
 - *The nodes n and N are connected.*
 - *We draw only one phase of the source and of the load.*
- *Let's find first the rms phase voltage.*

$$V_p = \frac{V_L}{\sqrt{3}} = \frac{500}{\sqrt{3}} \text{ V rms}$$

- *Therefore, converting rms to peak amplitude:*

$$V_{AN} = \frac{500\sqrt{2}}{\sqrt{3}} \angle 0^\circ \text{ V}$$

$$\Rightarrow I_{AN} = \frac{V_{AN}}{R + jX_L} = \frac{500\sqrt{2}/\sqrt{3}}{10 + 20j}$$

$$\Rightarrow i_{AN}(t) = 18.26 \cos(\omega t - 63.43^\circ) \text{ A}$$

