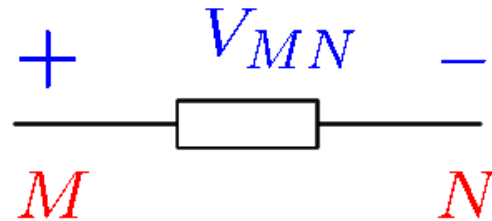



# THREE PHASE SYSTEMS— PART 2
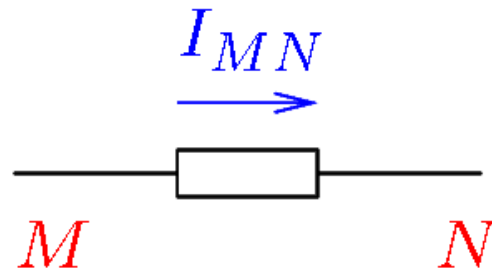
# Notation

- Let  $M$  and  $N$  denote the terminals of a circuit element.
- $V_{MN}$  will be the voltage between  $M$  and  $N$  with  $+$  at  $M$  and  $-$  at  $N$ .




- $I_{MN}$  will be the current flowing from  $M$  to  $N$ .


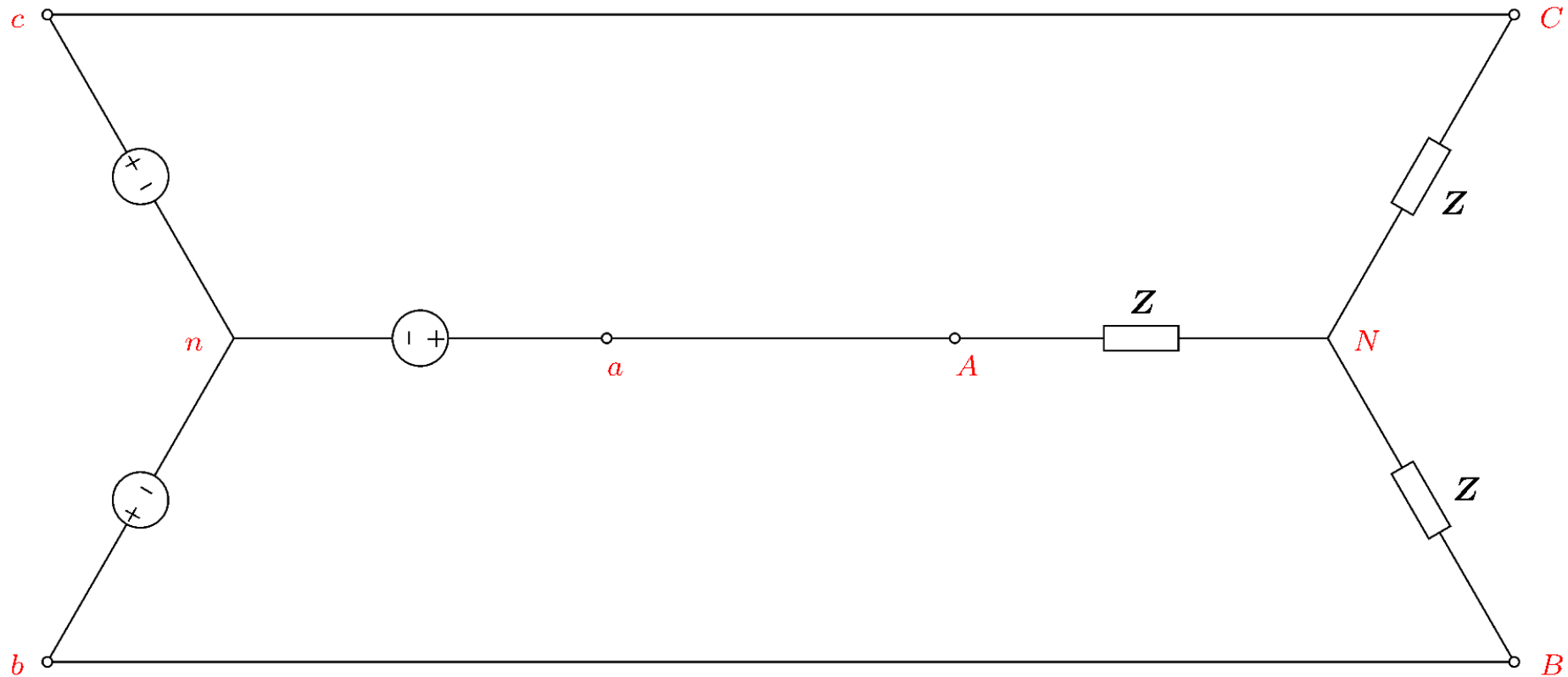
# Example 1

Assume  $v_{an}(t) = 200 \cos(\omega t)$  V and  $\mathbf{Z} = 25 \angle 20^\circ \Omega$ . Find the voltage  $v_{ac}(t)$  and the current  $i_{bB}(t)$ .




# Example 1 (Continued)

By KVL:  $v_{ab} = v_{an} - v_{bn}$

$$v_{ca} = v_{cn} - v_{an}$$

$$v_{bc} = v_{bn} - v_{cn}$$

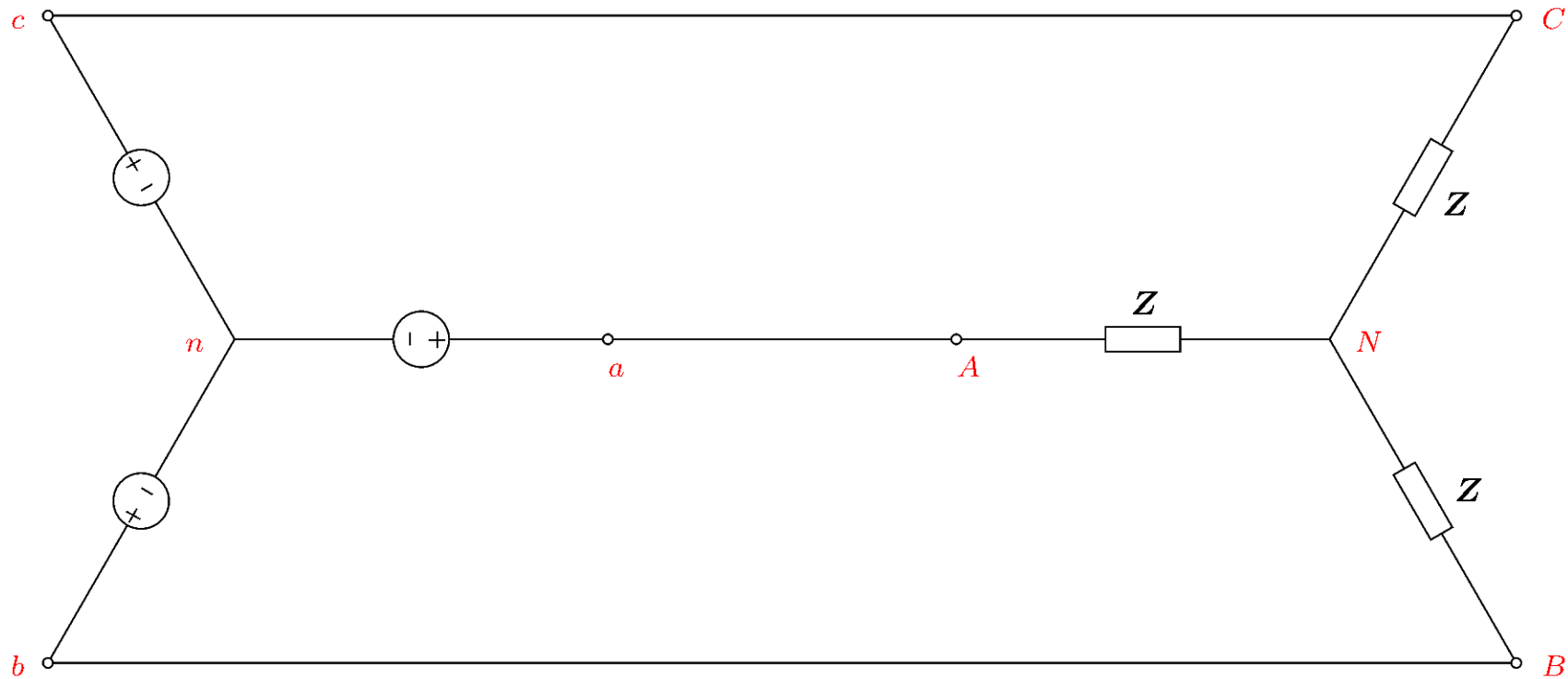

# Example 1 (Continued)

The phase voltage phasors are:

$$V_{an} = 200\angle 0^\circ V$$

$$V_{bn} = 200\angle -120^\circ V$$

$$V_{cn} = 200\angle 120^\circ V.$$



The line voltage phasors  $V_{ab}$ ,  $V_{bc}$ ,  $V_{ca}$  are:

$$V_{ab} = V_{an} - V_{bn}$$

$$V_{bc} = V_{bn} - V_{cn}$$

$$V_{ca} = V_{cn} - V_{an}$$

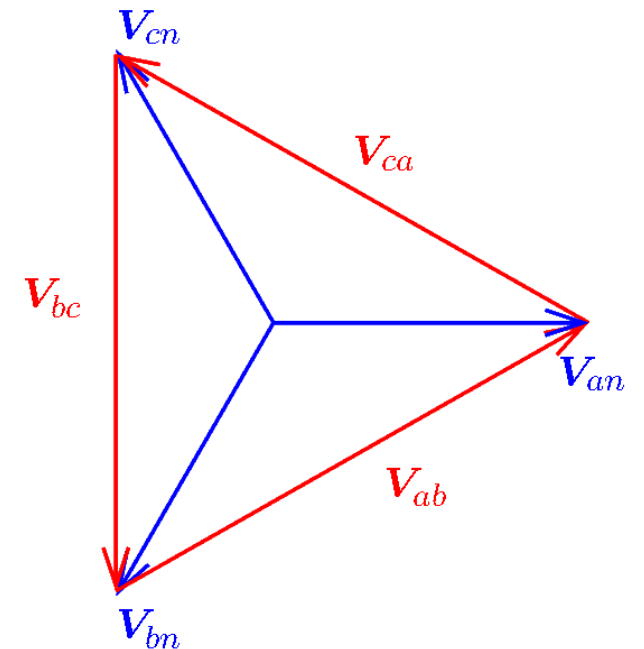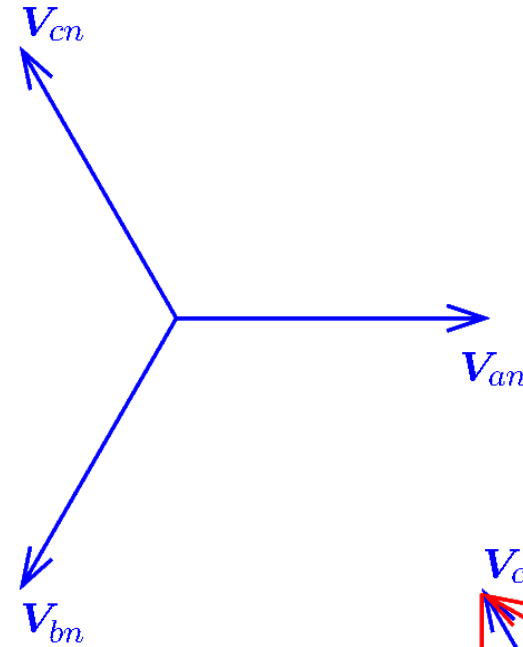The line voltages can be easily obtained graphically.



# Example 1 (Continued)

Graphically, we can see that:

$$V_{ab} = 200\sqrt{3}\angle 30^\circ V$$


$$V_{ca} = 200\sqrt{3}\angle 150^\circ V$$

$$V_{bc} = 200\sqrt{3}\angle -90^\circ V.$$

Therefore,

$$v_{ac}(t) = -v_{ca}(t) = -200\sqrt{3} \cos(\omega t + 150^\circ) V$$

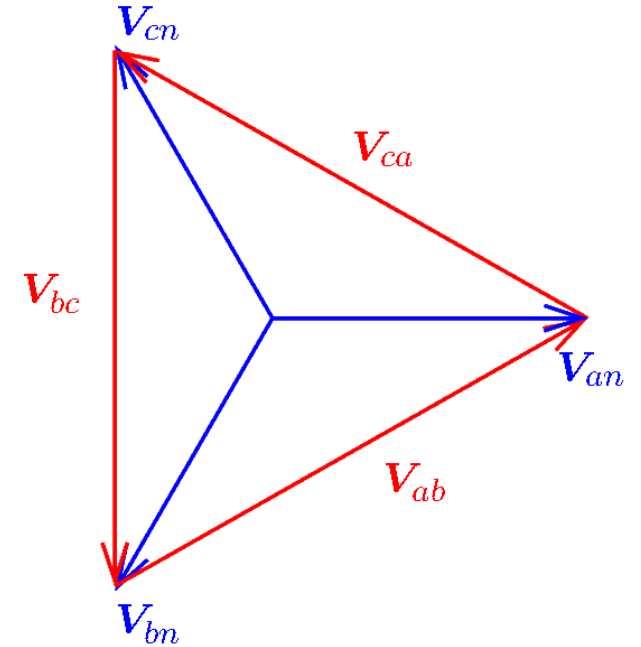
$$v_{ac}(t) = 346.41 \cos(\omega t - 30^\circ) V.$$



The current  $i_{bB}$  can be obtained immediately from a per-phase equivalent.
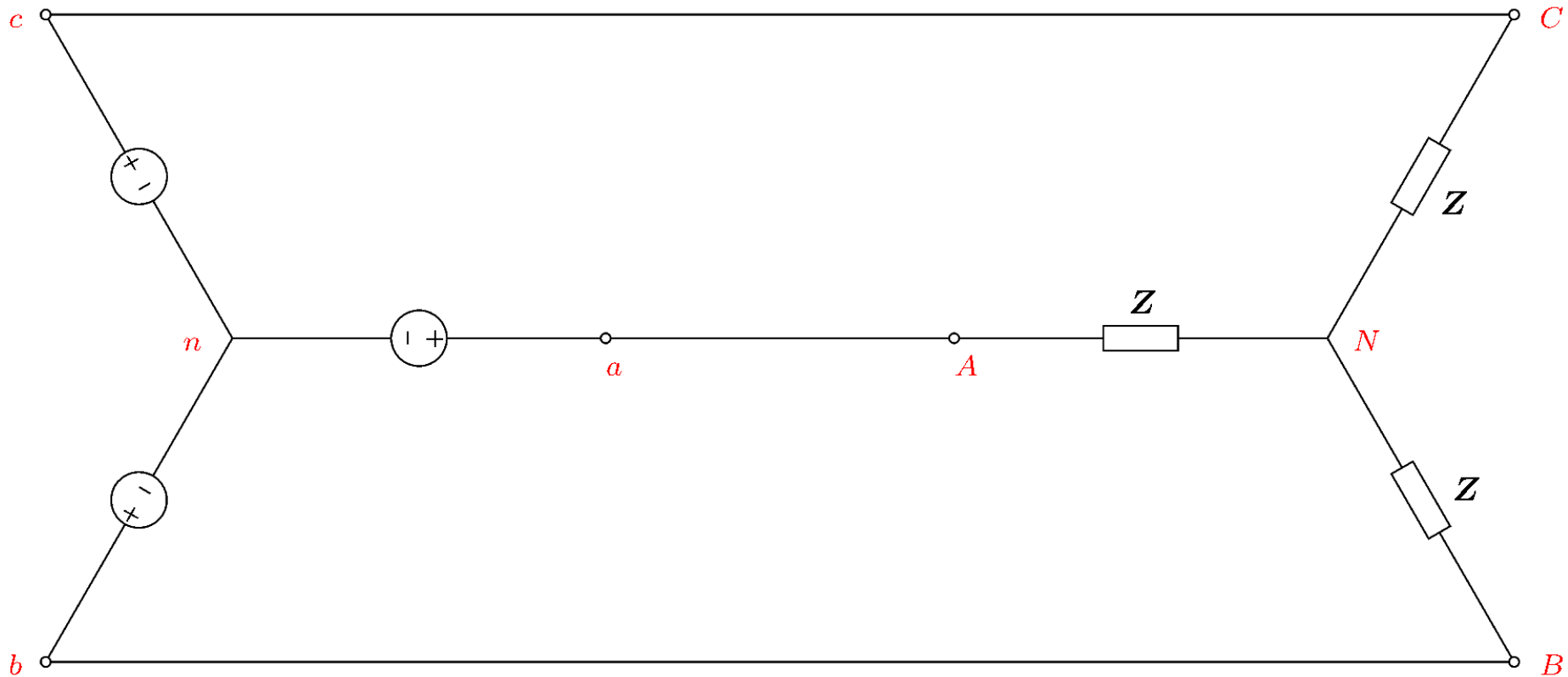
# Example 1 (Continued)


- *Since the system is balanced, the middle points  $n$  and  $N$  are at the same potential.*
- *Therefore, a per-phase equivalent may be used.*


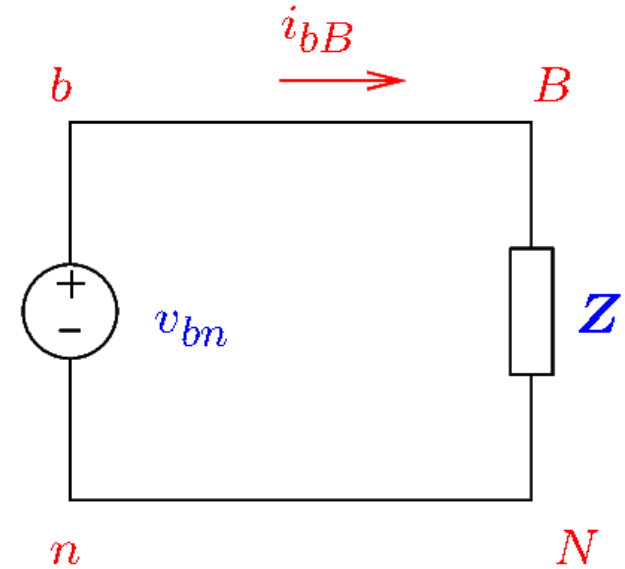
# Example 1 (Continued)

$$I_{bB} = \frac{V_{bn}}{\mathbf{Z}} = \frac{200\angle -120^\circ}{25\angle 20^\circ} = 8\angle -140^\circ \text{ A}$$

$$i_{bB}(t) = 8 \cos(\omega t - 140^\circ) \text{ A}$$



# Line and Phase Voltages

The general relationship between line and phase voltages is

$$V_{line} = V_{phase} \cdot \sqrt{3} \angle \varphi$$

where the angle  $\varphi$  depends on which line and phase voltages we compare.

The possible values of  $\varphi$  are:

$$\varphi = \pm 30^\circ, \pm 90^\circ, \pm 150^\circ$$


*Examples:*

$$V_{ac} = V_{an} \cdot \sqrt{3} \angle -30^\circ$$

$$V_{ab} = V_{an} \cdot \sqrt{3} \angle +30^\circ$$


$$V_{cb} = V_{an} \cdot \sqrt{3} \angle +90^\circ$$
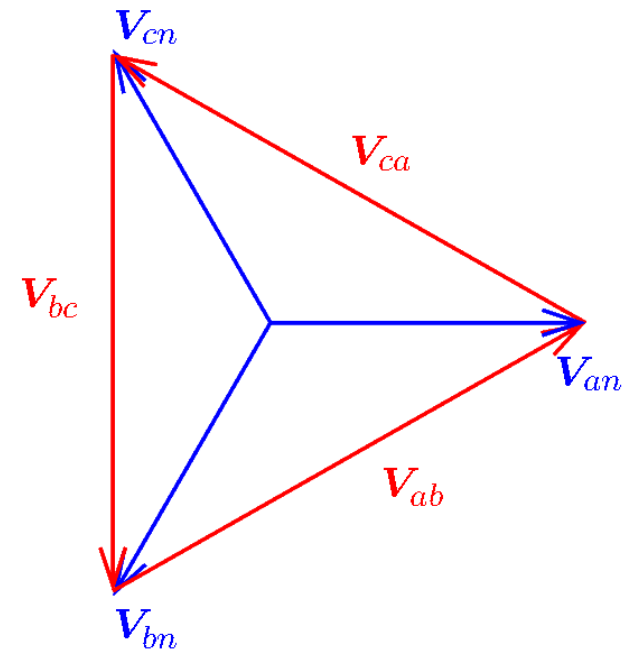
$$V_{bc} = V_{an} \cdot \sqrt{3} \angle -90^\circ$$



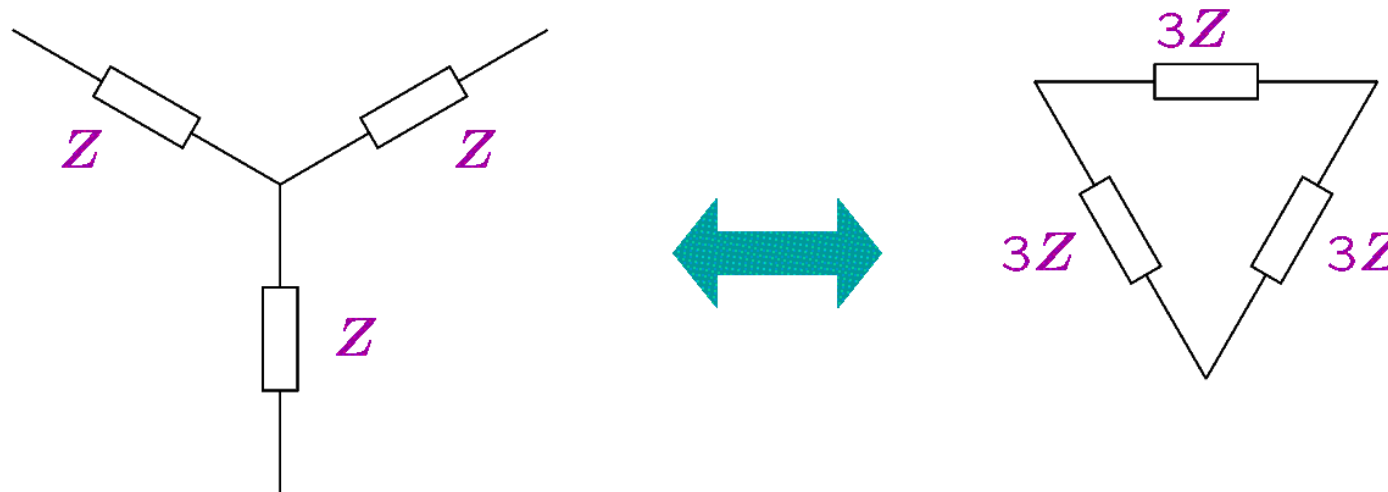
# Conversions between $Y$ and $\Delta$

- It is sometimes convenient to substitute a  $Y$ -connected load with a  $\Delta$ -connected load, or vice-versa.
- For balanced loads, the impedance per phase of the equivalent  $\Delta$ -connected load is triple.


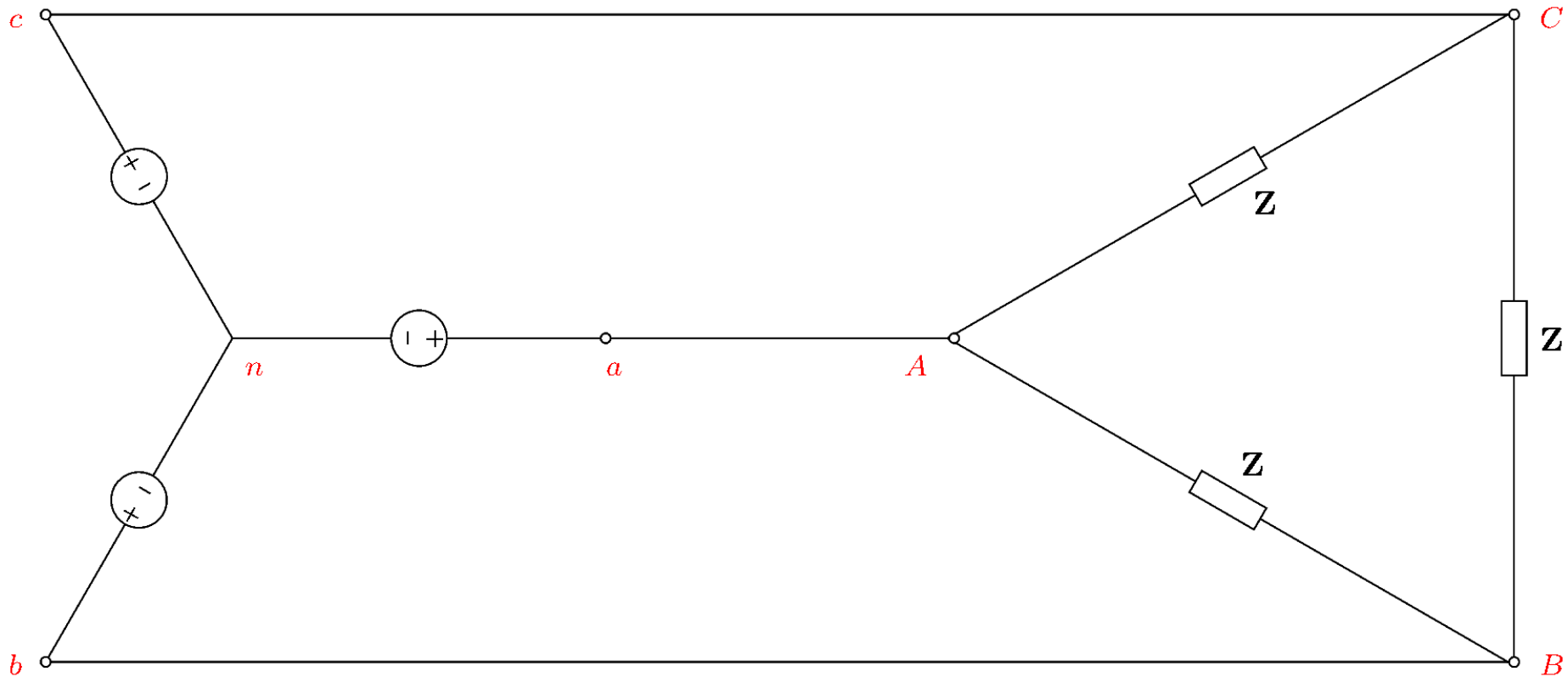
# Example 2

Assume  $v_{an}(t) = 300 \cos(\omega t)$  V and  $\mathbf{Z} = 24 \angle 20^\circ \Omega$ . Find the phasor currents  $\mathbf{I}_{CB}$  and  $\mathbf{I}_{bB}$ .




## Example 2 (Continued)

From the figure, we can see that  $V_{CB} = 300\sqrt{3}\angle 90^\circ$ .

$$I_{CB} = \frac{V_{CB}}{Z} = 21.65\angle 70^\circ \text{ A}$$

Converting the load to the equivalent  $Y$ -connected load, the impedance per phase becomes  $\frac{Z}{3} = 8\angle 20^\circ \Omega$ .
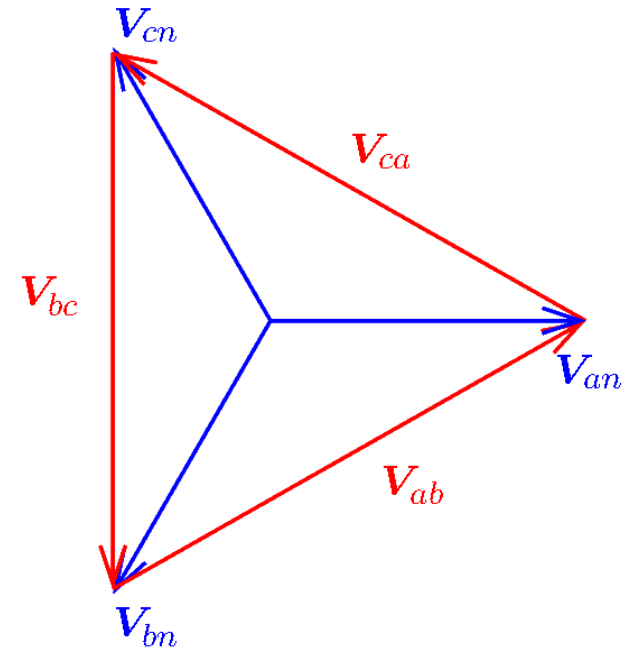
$$I_{bB} = \frac{V_{bn}}{Z/3} = \frac{300\angle -120^\circ}{24\angle 20^\circ/3} = 37.5\angle -140^\circ \text{ A}$$



## Example 3

*Find additional circuit elements that correct the power factor in the previous example. Assume a 60 Hz frequency.*

- *Since the system is balanced, the reactive power is the same on all three phases.*
- *Let's calculate the reactive power on one of the phases.*
- *The complex power on the impedance between B and C is:*

$$S_{CB} = V_{CB,rms} I_{CB,rms}^* = 300\sqrt{3}/\sqrt{2} \angle 90^\circ (21.65/\sqrt{2} \angle 70^\circ)^*$$

$$S_{CB} = 5.625 \angle 20^\circ \text{ kVA}$$

$$Q_{CB} = 5.625 \sin(20^\circ) = 1.92 \text{ kVAR}$$

- *Thus, we need a balanced Y-connected or  $\Delta$ -connected load that has a total reactive power  $Q = -3Q_{CB}$ .*

## Example 3 (Continued)

- *Let's choose a  $\Delta$ -connected load.*
- *Capacitors generate reactive power, so we will have identical capacitors on each phase of the load.*
- *Let  $X_c$  be the reactance of a capacitor,  $V_{c,rms}$  its rms voltage, and  $Q_c$  the reactive power of the capacitor.*

- *Recall that  $X_c = -\frac{1}{C\omega}$ .*

$$Q_c = \frac{V_{c,rms}^2}{X_c} \Rightarrow C = -\frac{Q_c}{V_{c,rms}^2 \omega}$$

- *$V_{c,rms}$  is the line voltage  $\frac{300\sqrt{3}}{\sqrt{2}}$  V,  $Q_c = -Q/3$ , and  $\omega = 2\pi 60$ , so  $C = 72.73 \mu F$ .*
- *If capacitors were connected in the Y-configuration, their value would be triple. Can you tell why?*