

Transformers

Introduction

- A transformer is an **AC** device that transfers energy between electrically isolated circuits by means of magnetically coupled inductors.
- Transformers have relatively low losses; energy is transferred efficiently.
- Typically, transformers transfer energy at different voltage levels; a transformer is capable of reducing or increasing the input voltage.

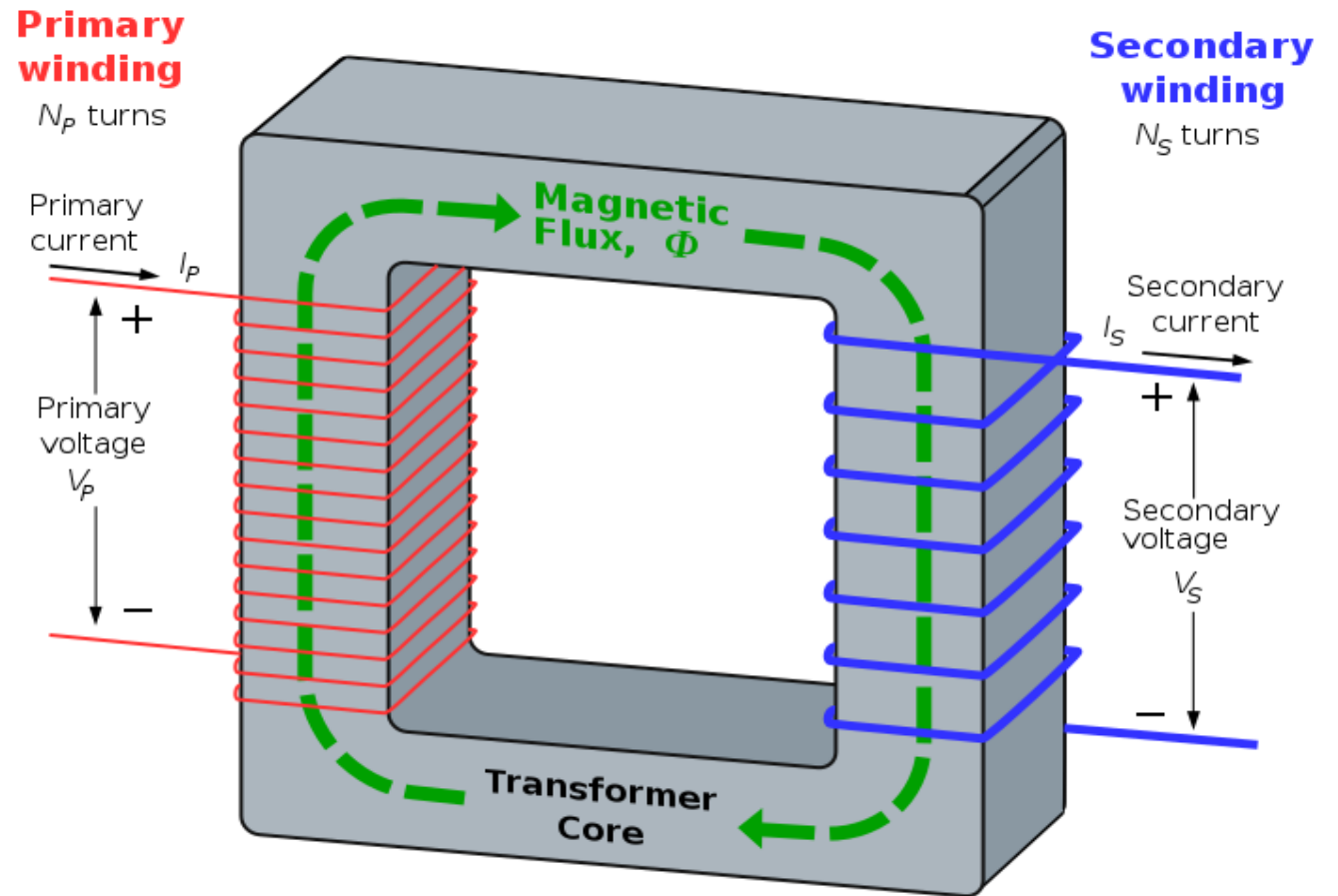


Figure downloaded from <http://en.wikipedia.org/wiki/Transformer>

Introduction

- The transformer coil to which power is applied is called *primary*.
- Any other coil of the transformer is a *secondary*.
- Consider a transformer with a single secondary operating, of course, with AC.
- Ideally,

$$\frac{V_P}{V_S} = \frac{I_S}{I_P} = \frac{N_P}{N_S}$$


where

- V_P and V_S are the rms values of the primary and secondary voltages.
- I_P and I_S are the rms values of the primary and secondary currents.
- N_P and N_S are the number of turns of the primary and secondary coils.
- The equations can be written also in terms of phasor voltages.
- However, we need to define first the *dot* notation, so that we write the signs right.

Symbol

- The symbol of a transformer

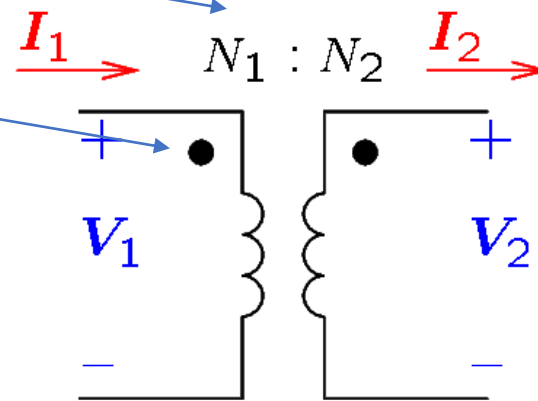- Specifies the turns ratio
- Has a dot next to one of the terminals of each coil.





- For example, a 3: 2 turns ratio could mean:

- $N_1 = 300$ and $N_2 = 200$
- $N_1 = 600$ and $N_2 = 400$
- $N_1 = 3000$ and $N_2 = 2000$
- ...

- Practical transformers resemble ideal transformers when they have a sufficiently large number of turns.

Symbol

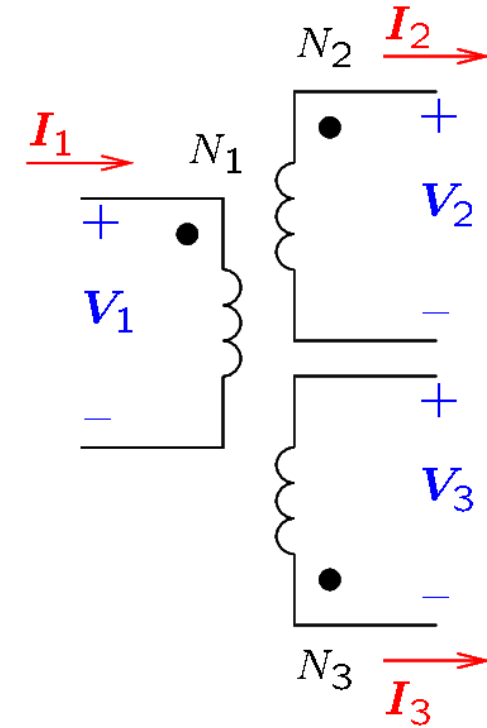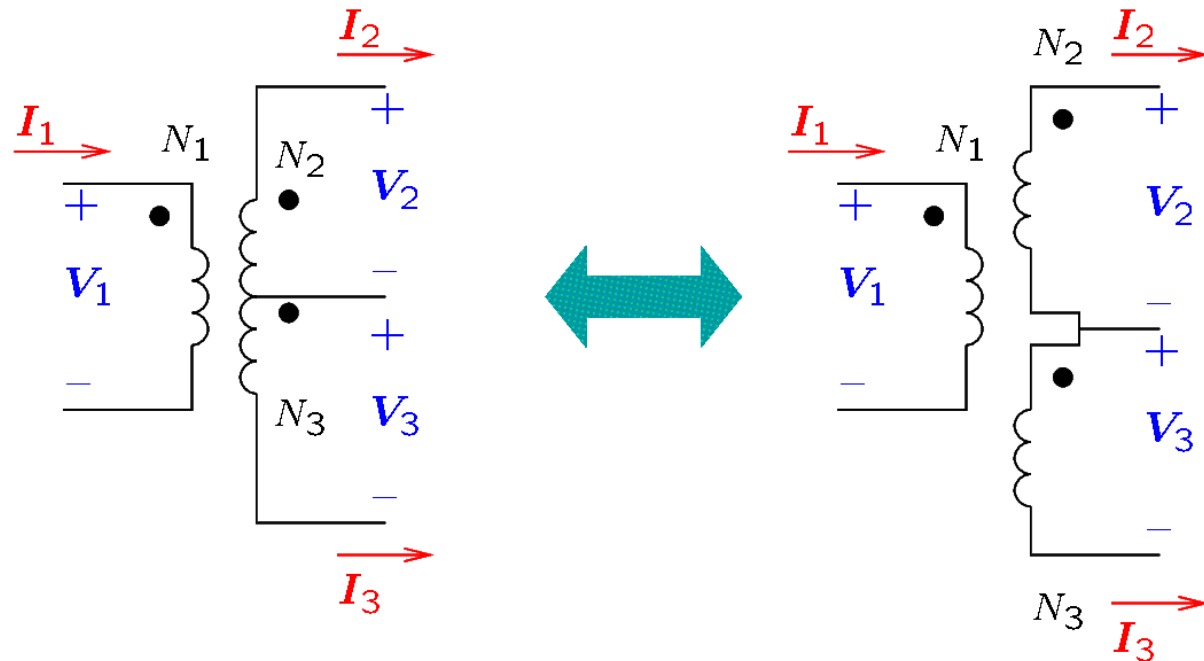- A transformer may have more than two windings.
- When more than two windings are present, we specify the number of turns for each coil.
- A coil may have more than one terminal.
- For example a coil with three terminals can be seen as consisting of two coils connected together.




Equations

- Ideally, the voltage ratio is the turns ratio.
- *If the + sign of the voltage is at the dot, write the voltage with the + sign; otherwise, write it with the – sign.*
- Examples:

$$\frac{V_2}{V_1} = \frac{N_2}{N_1}$$

$$\frac{-V_3}{V_2} = \frac{N_3}{N_2}$$

$$\frac{V_1}{-V_3} = \frac{N_1}{N_3}$$


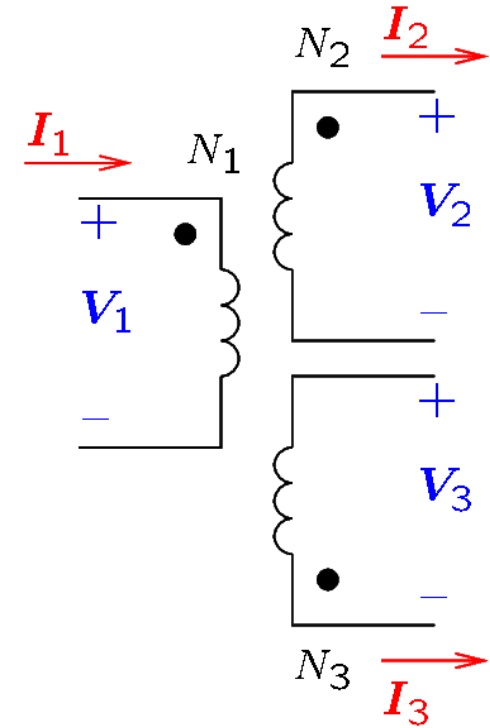


Equations

- Ideally, the algebraic sum of currents weighted by the number of turns is zero.
- *If a current enters the transformer at a dotted terminal, write it with the + sign; otherwise, write it with the – sign.*
- Examples:

$$N_1 I_1 - N_2 I_2 - N_3 I_3 = 0$$


$$N_p I_p + N_s I_s = 0$$

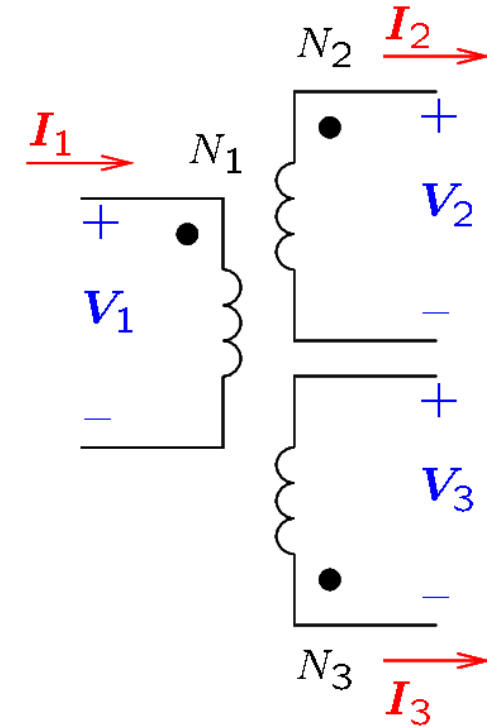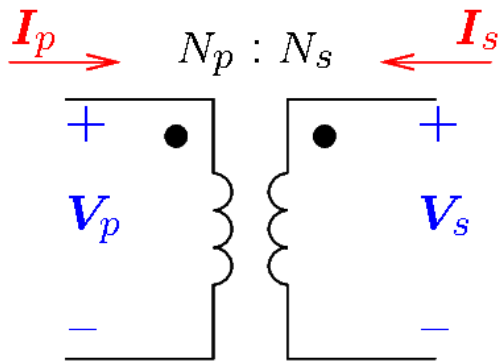


Power

- Ideally, a transformer does not absorb power.
- *This is can be seen easily from the ideal voltage and current equations of a transformer.*
- For example, assuming rms phasor currents and voltages, in terms of the absorbed complex power:
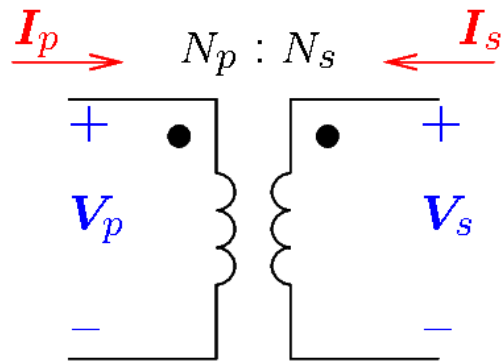
$$V_1 I_1^* - V_2 I_2^* - V_3 I_3^* = 0$$



$$V_p I_p^* + V_s I_s^* = 0$$

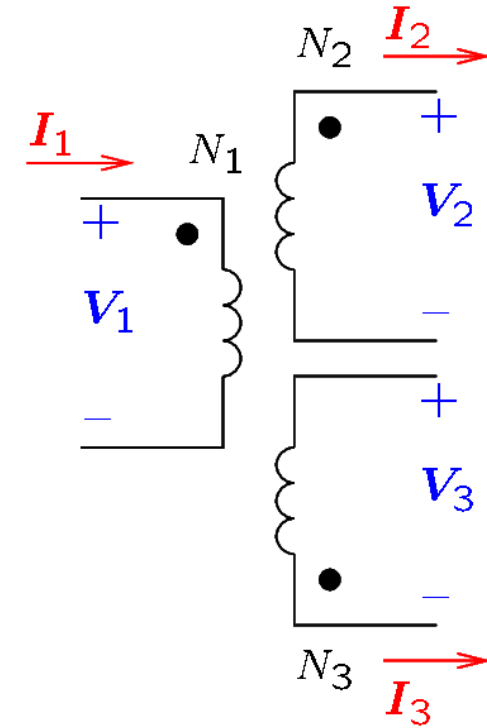

Example

The transformer has $N_1 = 1000$, $N_2 = 500$, and $N_3 = 200$. The frequency is 60 Hz and the source has 120 V rms. Find $i_1(t)$.

- Let $Z_2 = 100 \Omega$ be the impedance connected to the second winding.
- Let $Z_3 = j\omega 100 \text{ mH} + \frac{1}{j\omega 10 \mu\text{F}} = -227.56j \Omega$ be the impedance connected to the third winding.

- The equations are:

$$N_1 I_1 + N_2 I_2 - N_3 I_3 = 0$$


$$\frac{V_2}{V_1} = \frac{N_2}{N_1} \text{ and } \frac{-V_3}{V_1} = \frac{N_3}{N_1}$$

$$V_2 = -I_2 Z_2 \text{ and } V_3 = -I_3 Z_3$$

$$V = 47 I_1 + V_1$$

- Solving for I_1 , the result is: $I_1 = 269.11 \angle 3.6^\circ + \alpha_v \text{ mA rms}$
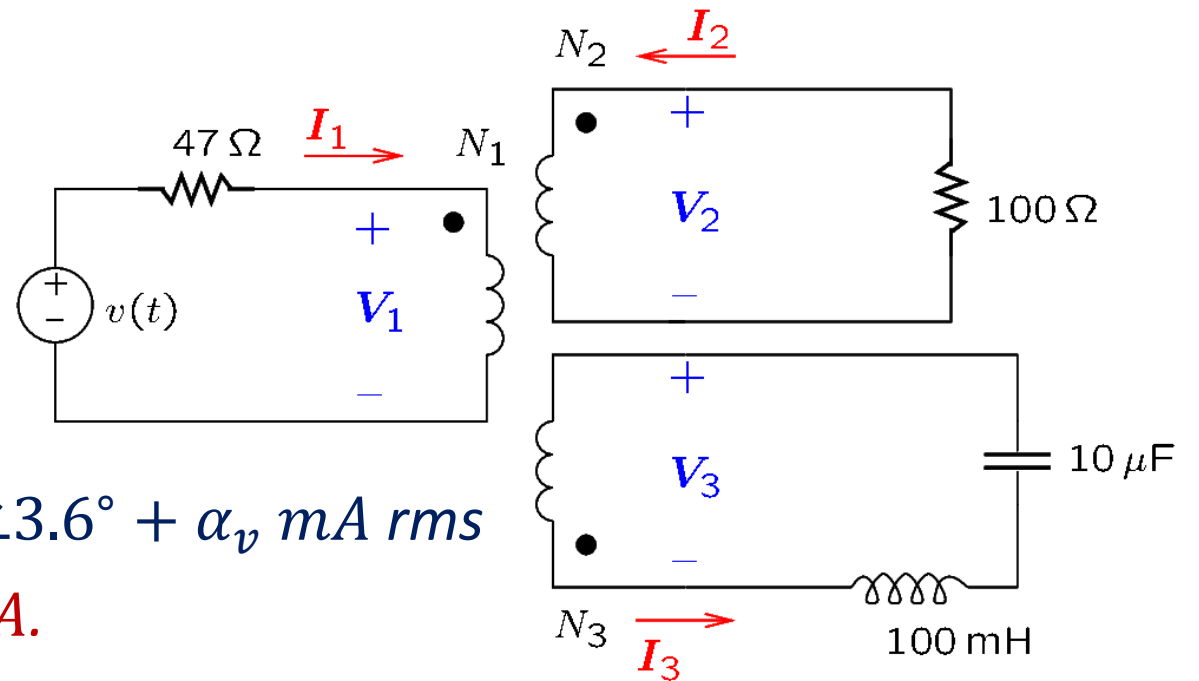
$$\Rightarrow i_1(t) = 380.58 \cos(\omega t + 3.6^\circ + \alpha_v) \text{ mA.}$$



Example—Remarks

- Note that the current equation

$$N_1 I_1 + N_2 I_2 - N_3 I_3 = 0$$

can be brought to the form

$$I_1 = V_1 \left(\frac{1}{Z_2 N_1^2 / N_2^2} + \frac{1}{Z_3 N_1^2 / N_3^2} \right)$$

- In other words, the transformer circuit is equivalent to the circuit shown below.
- $Z_2 N_1^2 / N_2^2$ and $Z_3 N_1^2 / N_3^2$ are reflected impedances (from the secondary windings to the primary winding).

