

Transformers—Part 2


Examples

Transformers in Electric Power Distribution

- Having finished the topics of our class, we will focus the remaining lectures on examples.
- Note that transformers play an important role in electric power distribution, as they lower considerably losses.
- Power line losses are due to the resistance of the cables.
- Losses are proportional to the square of the rms current and the resistance.
- To operate power lines at lower currents, power is transmitted at very high voltage levels.
 - Transformers are used to step up voltage near the source of power.
 - Transformers are used to step down the voltage at the consumers.
- The following example will illustrate the role of transformers.

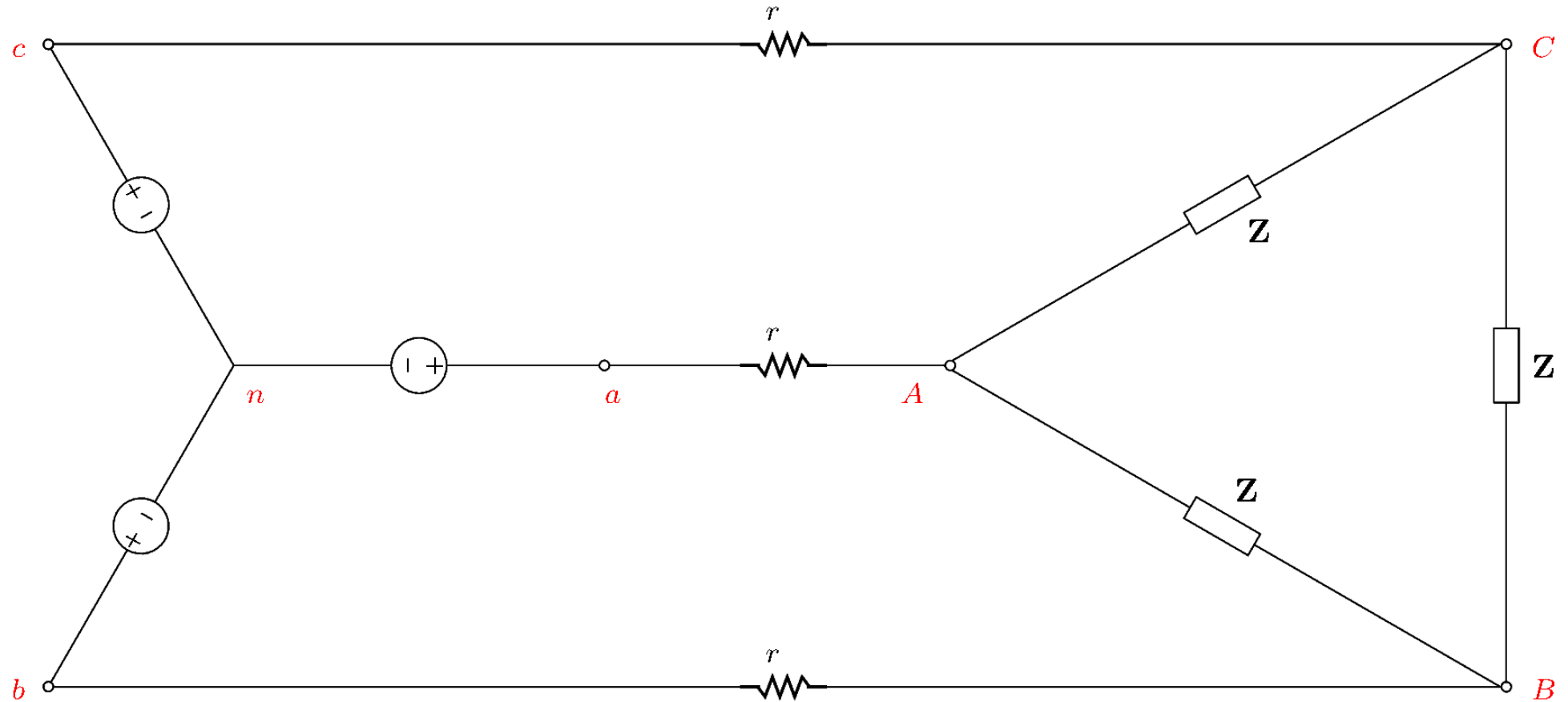
Example

Assume $v_{ab}(t) = 500 \cos(\omega t)$ V and $\mathbf{Z} = 4\angle 30^\circ \Omega$. Assume that the power lines have each a resistance $r = 2 \Omega$. Find the efficiency of the system.



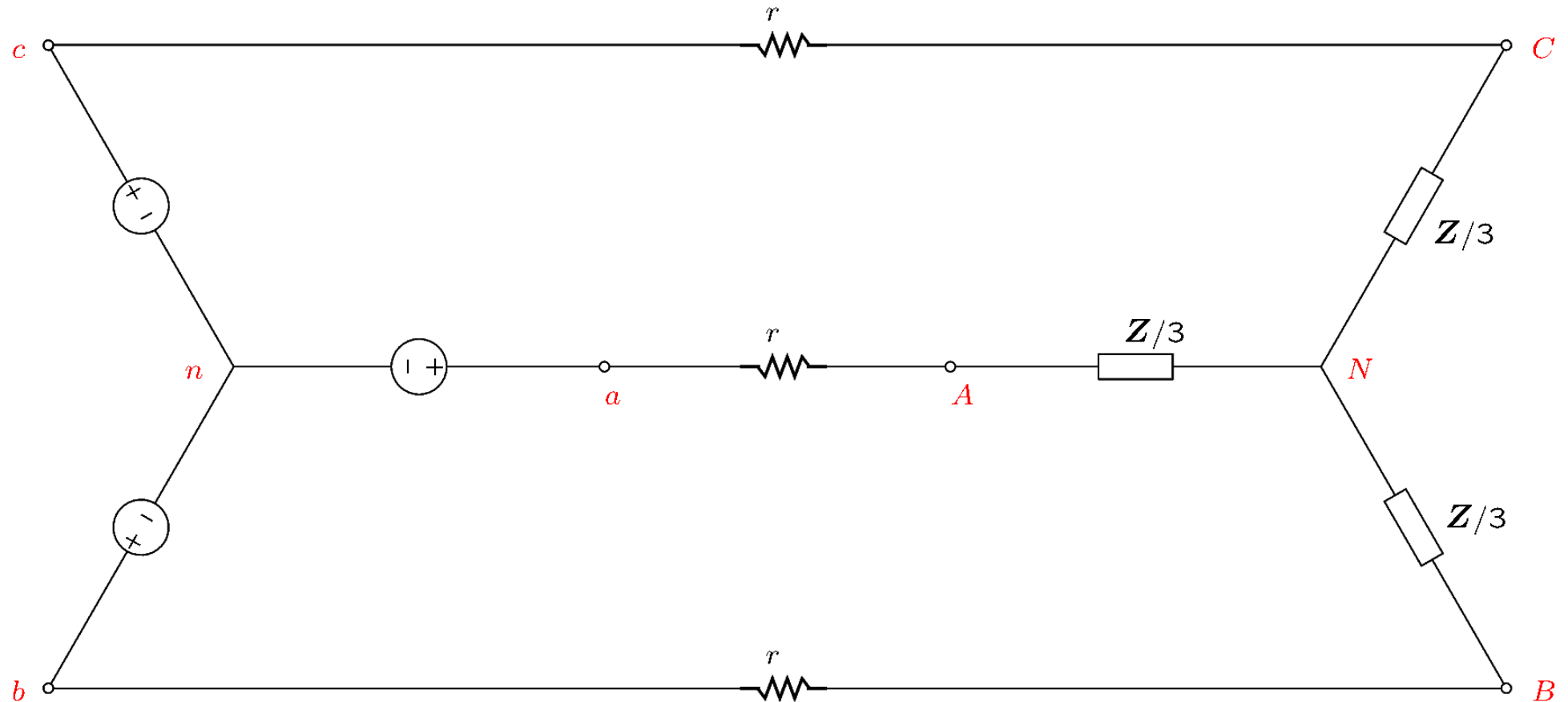
Example (Continued)

- *Let us first convert the Δ -connected load to a Y -connected load.*
- *The circuit is balanced, so we can draw an equivalent circuit per phase.*



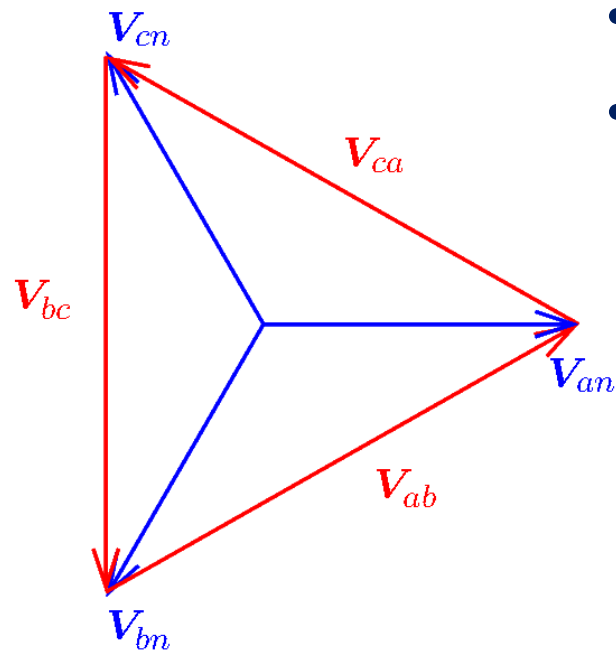Example (Continued)


- The equivalent circuit per phase could show any of the three phases; let's show the first phase (this is a random choice).
- The problem does not give $v_{an}(t)$ but $v_{ab}(t)$.
- A phasor diagram showing the phase and line voltages can help establish the relationship between the two voltages.



- Note that $v_{ab}(t)$ leads $v_{an}(t)$ by 30° .
- The magnitudes also are different by a factor of $\sqrt{3}$, since $v_{ab}(t)$ is a line voltage.

• Therefore, $v_{ab}(t) = 500 \cos(\omega t) V \Rightarrow$
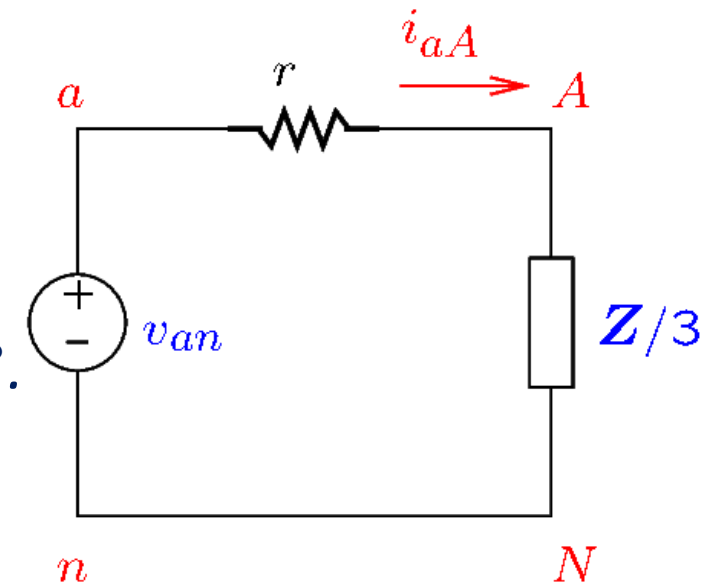
$$v_{an}(t) = \frac{500}{\sqrt{3}} \cos(\omega t - 30^\circ) V.$$



Example (Continued)

- Note that:

$$V_{an} = \frac{500}{\sqrt{3}} \angle -30^\circ \text{ V}$$


$$I_{aA} = \frac{V_{an}}{r + \mathbf{Z}/3} = 89.53 \angle -41.93^\circ \text{ A}$$

- The power generated by the source, per phase, is

$$\begin{aligned} P_{in} &= V_{an,rms} I_{aA,rms} \cos(\alpha_v - \alpha_i) \\ &= \frac{500}{\sqrt{3}\sqrt{2}} \cdot \frac{89.53}{\sqrt{2}} \cdot \cos(-30^\circ - (-41.93^\circ)) \end{aligned}$$

$$P_{in} = 12.643 \text{ kW}$$

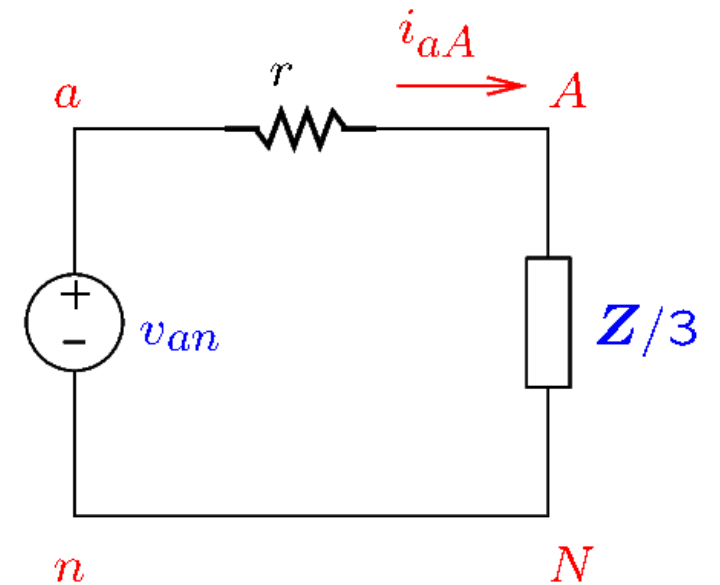- To find the power dissipated by the load, we need to find first V_{AN} .



Example (Continued)

- By voltage division:

$$V_{AN} = V_{an} \cdot \frac{Z/3}{r + Z/3}$$

$$V_{AN} = 119.37 \angle -11.93^\circ \text{ V}$$


- The power dissipated by the load, per phase, is:

$$\begin{aligned} P_{out} &= V_{AN,rms} I_{aA,rms} \cos(\alpha_v - \alpha_i) \\ &= \frac{119.37}{\sqrt{2}} \cdot \frac{89.53}{\sqrt{2}} \cdot \cos(30^\circ) \end{aligned}$$

$$P_{out} = 4.6277 \text{ kW}$$

- The efficiency is:
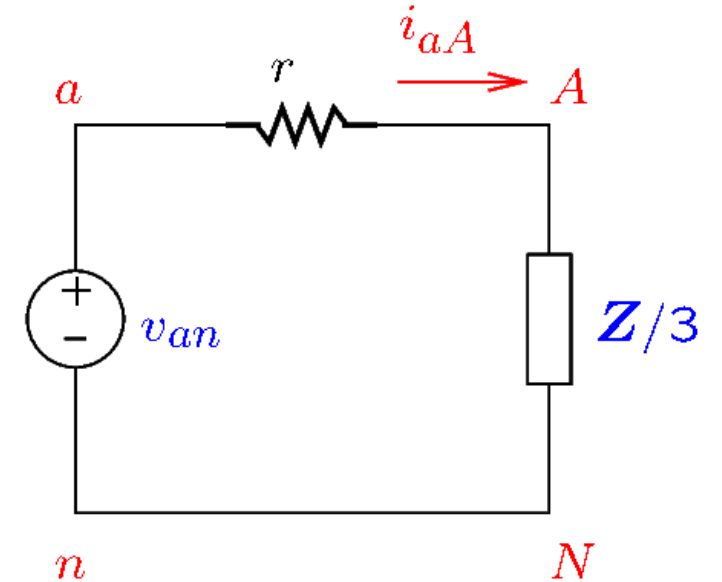
$$\eta = \frac{P_{out}}{P_{in}} = \frac{4.6277}{12.643} = 36.6\%$$




Remarks

- In our previous example, only 36.6% of the power generated by the source was dissipated by the load.
- 63.4% (almost twice as much!) was dissipated on the power lines.
- A possible way of improving efficiency is by correcting the power factor.
- This will reduce the line current, and in this way the losses on the power lines.
- However, this improvement will not eliminate power losses.
- Note that power factor correction must be done at the load, after the power lines, not at the generator, before the power lines.
- Otherwise, the current through the power lines will not be reduced.

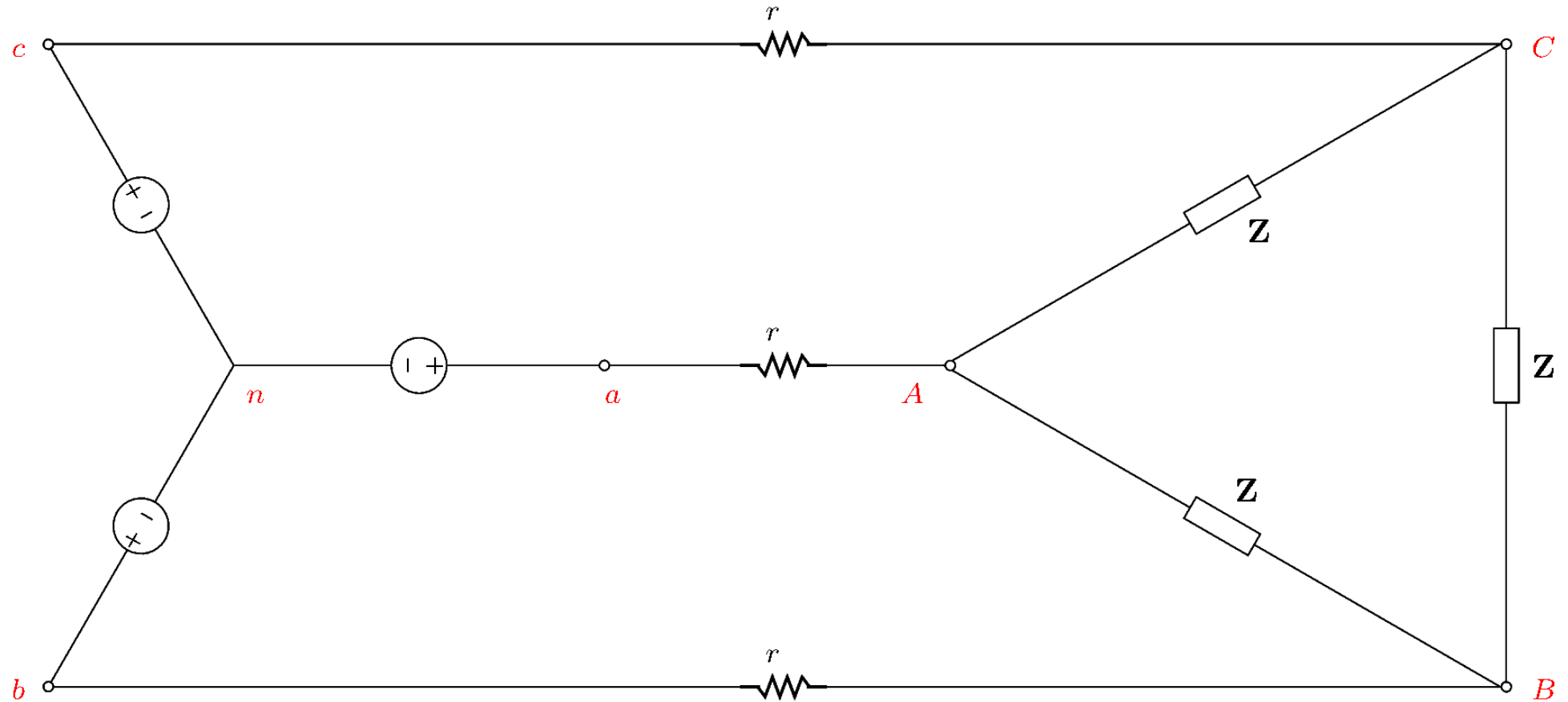Example 2

Assume $v_{ab}(t) = 500 \cos(\omega t)$ V, $\mathbf{Z} = 4\angle 30^\circ \Omega$, and $r = 2 \Omega$. Find the efficiency of the system after power factor correction.




Example (Continued)

- Power factor correction at the load is equivalent to an additional component Z_a added in parallel to each phase of the load.
- The role of Z_a is to cancel the susceptance of the load.
- Recall that the susceptance of $Z/3$ is the imaginary part of $1/(Z/3)$.
- The equivalent load impedance is

$$Z_L = \left(\frac{Z}{3}\right) \parallel Z_a$$
$$\frac{1}{Z_L} = \frac{3}{Z} + \frac{1}{Z_a} = 0.6495 - 0.375j + \frac{1}{Z_a}$$

- Power factor correction cancels the imaginary part, so
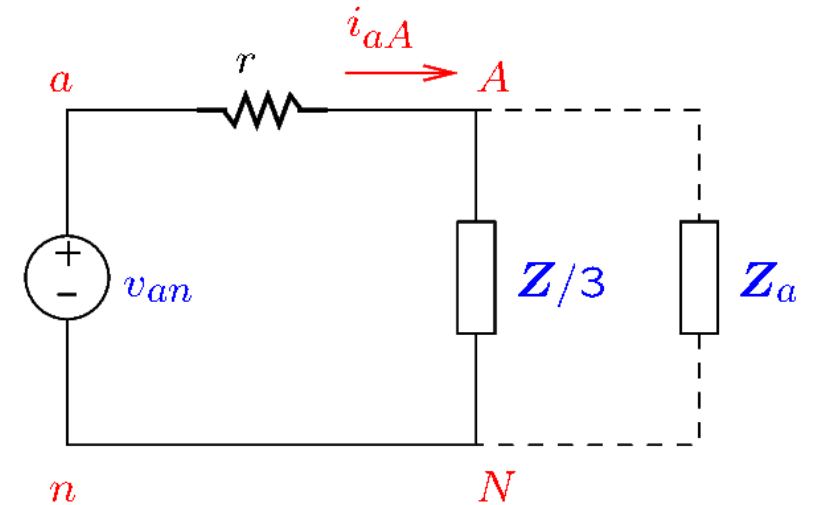
$$\frac{1}{Z_L} = 0.6945 \text{ S} \Rightarrow Z_L = 1.54 \angle 0^\circ \Omega$$



Example (Continued)


- *By voltage division:*

$$V_{AN} = V_{an} \cdot \frac{Z_L}{r + Z_L}$$

$$V_{AN} = 0.435 \cdot V_{an}$$

- *Since Z_L has an angle of 0° , the total impedance is real.*
- *Thus, all voltages and currents are in phase.*
- *This means that apparent power is identical to average power, since $\alpha_v = \alpha_i$.*
- *Therefore, the efficiency can be calculated as*
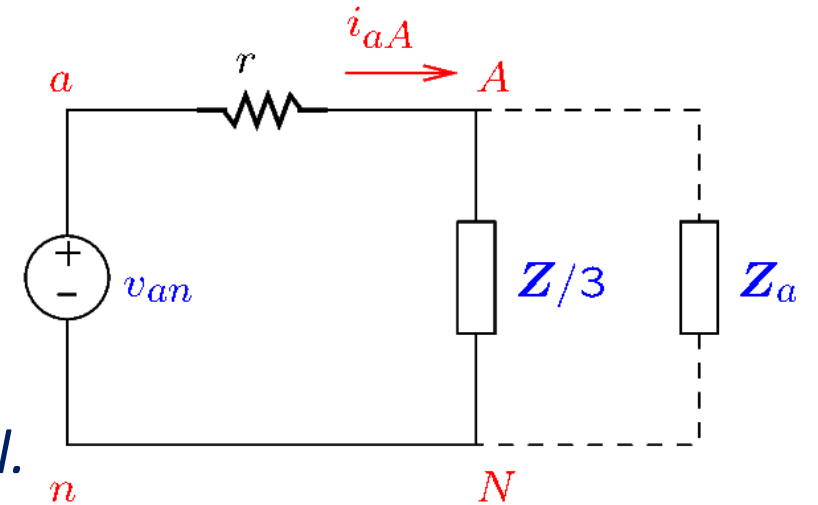
$$\eta = \frac{V_{AN,rms} I_{aA,rms}}{V_{an,rms} I_{aA,rms}} = \frac{V_{AN,rms}}{V_{an,rms}} = \frac{V_{AN}}{V_{an}} = 43.5\%$$




Remarks

- In our example, power factor correction has improved the efficiency of the system from 36.6% to 43.5%.
- This is a considerable improvement!
- However, even after power factor correction, more than half of the generated power is wasted!
- Losses can be further reduced with transformers.

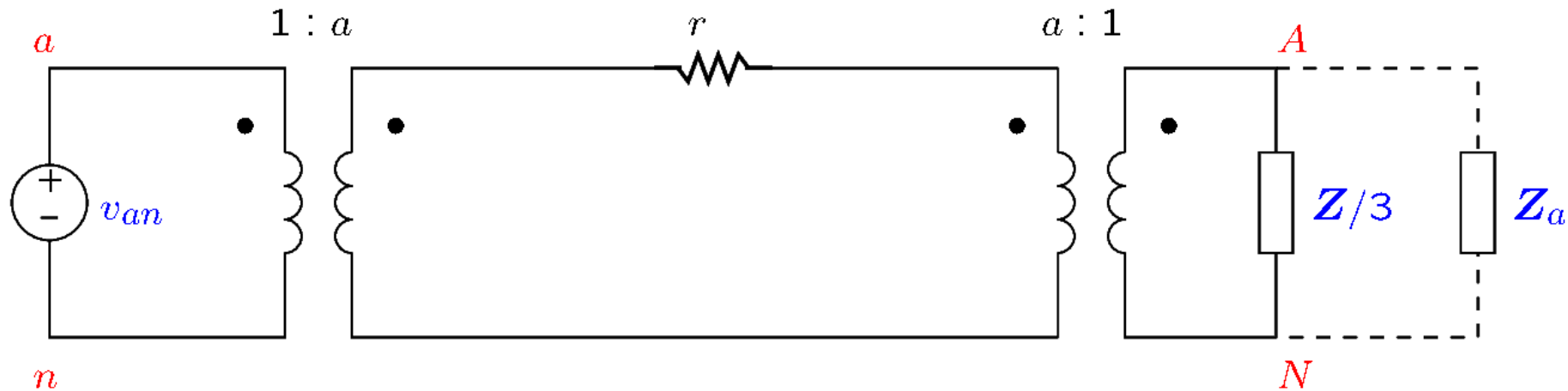Example 3

Consider the previous example. Assume that a three-phase transformer steps up the source voltage by a factor of $a = 100$. Assume that at the load, a three-phased transformer steps down the voltage by the same factor. Assume also that all transformers have the primary and secondary windings Y -connected. Find the efficiency of the system after power factor correction.

- The equivalent circuit per phase is shown in the figure.



Example 3 (Continued)

- As shown in the previous example, the load has an impedance $\mathbf{Z}_L = 1.54 \angle 0^\circ \Omega$.
- Thus, the load transformer with the \mathbf{Z}_L load is equivalent to the impedance $a^2 \mathbf{Z}_L$.
- Since r is in series with $a^2 \mathbf{Z}_L$, proceeding as in the previous example:

$$\eta = \frac{a^2 \mathbf{Z}_L}{r + a^2 \mathbf{Z}_L} = 99.99\%$$

- We have assumed ideal transformers; real transformers are very efficient but do have losses, so they will reduce a little this efficiency.

