


Review

Example 1

In the following example we will practice operational amplifiers, transformers, and the Thevenin equivalent.

Find the Thevenin equivalent at the terminals of the load resistor R_L . Assume $v_s(t) = 10 \cos(\omega t)$ mV.

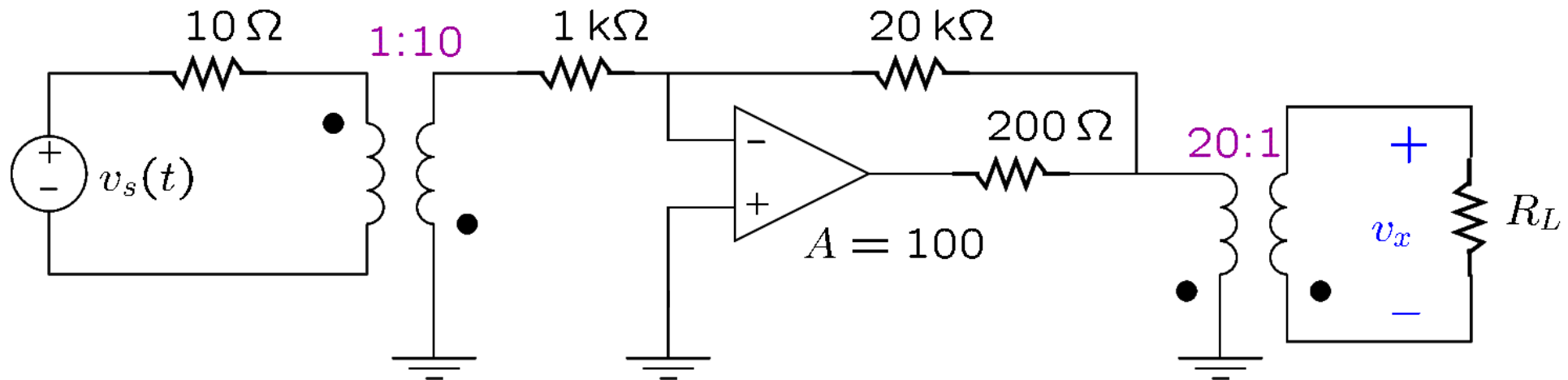
- When a part of the circuit is considered to be the load, to find the Thevenin equivalent, remove first the load from the circuit.*



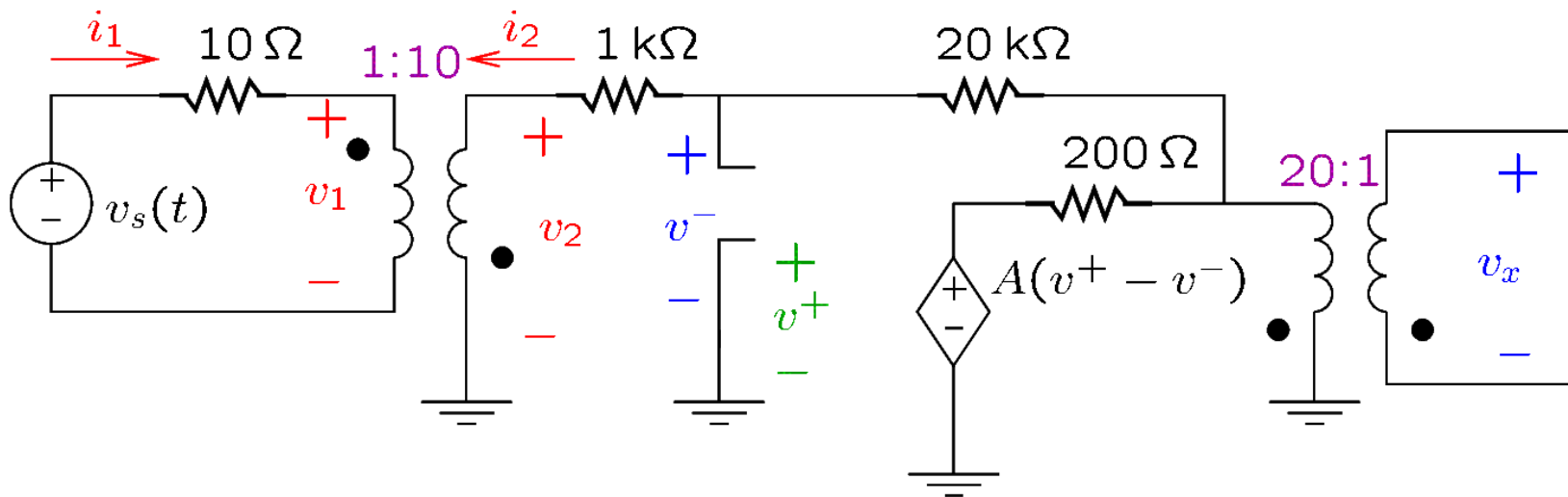
Example 1 (Continued)

- By replacing the operational amplifier with its equivalent circuit we obtain the circuit shown in the figure.
- We will further simplify the circuit before finding the Thevenin equivalent.
- Note the transformer equations:

$$\frac{-V_2}{V_1} = 10 \text{ and } 1 \cdot I_1 + 10 \cdot (-I_2) = 0$$




Example 1 (Continued)

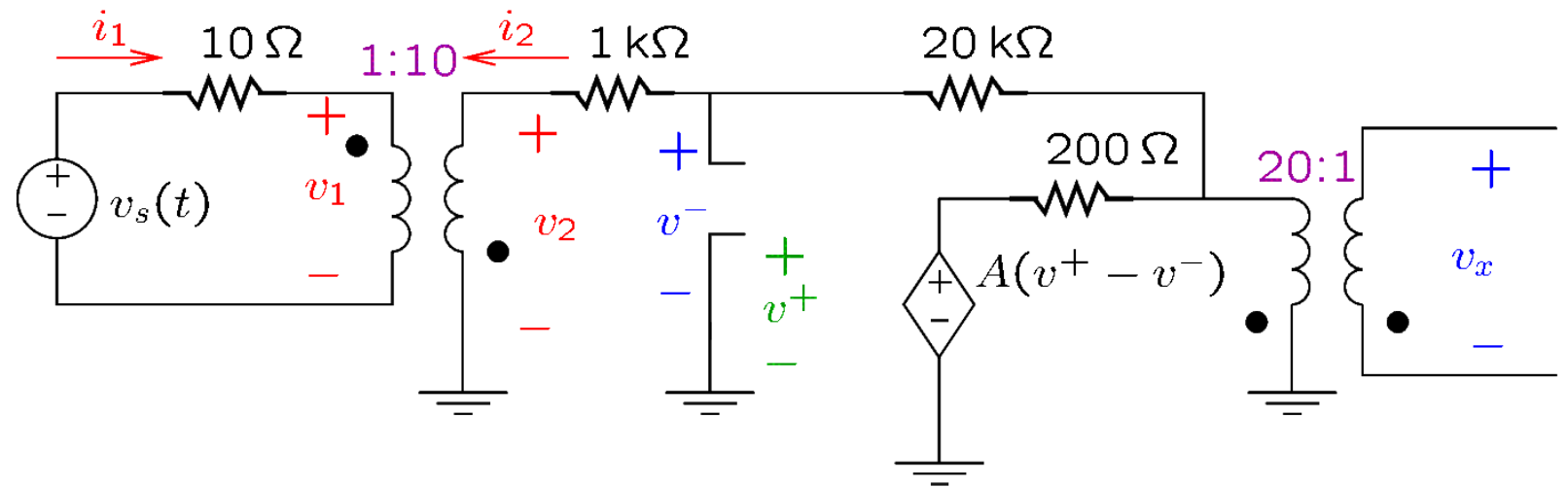

- Substituting $V_1 = -V_2/10$ and $I_1 = 10I_2$ in $V_1 = V_s - I_1 \cdot 10 \Omega$, we find that


$$V_2 = -10V_s + I_2 \cdot 10^2 \cdot 10 \Omega$$

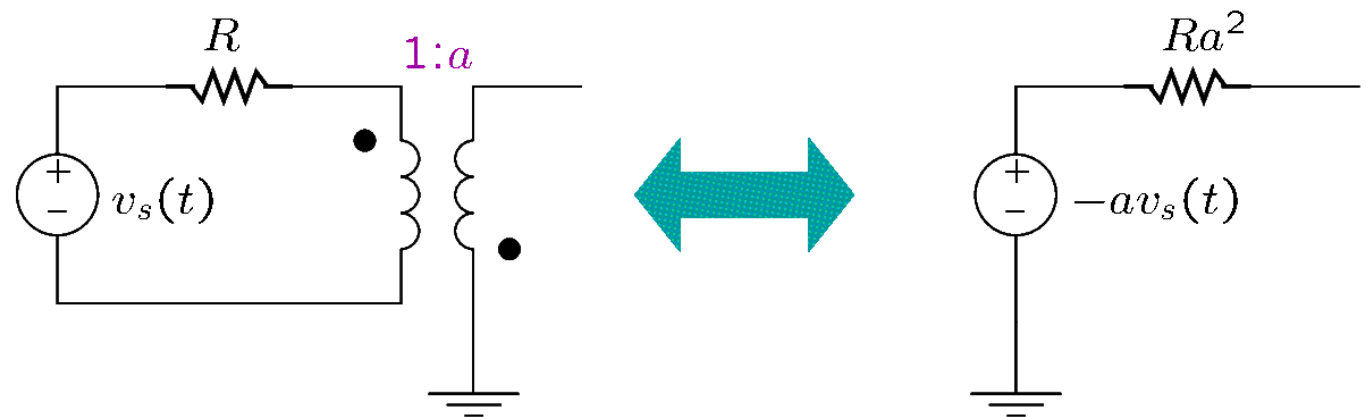- Thus, we have proved the following equivalence:



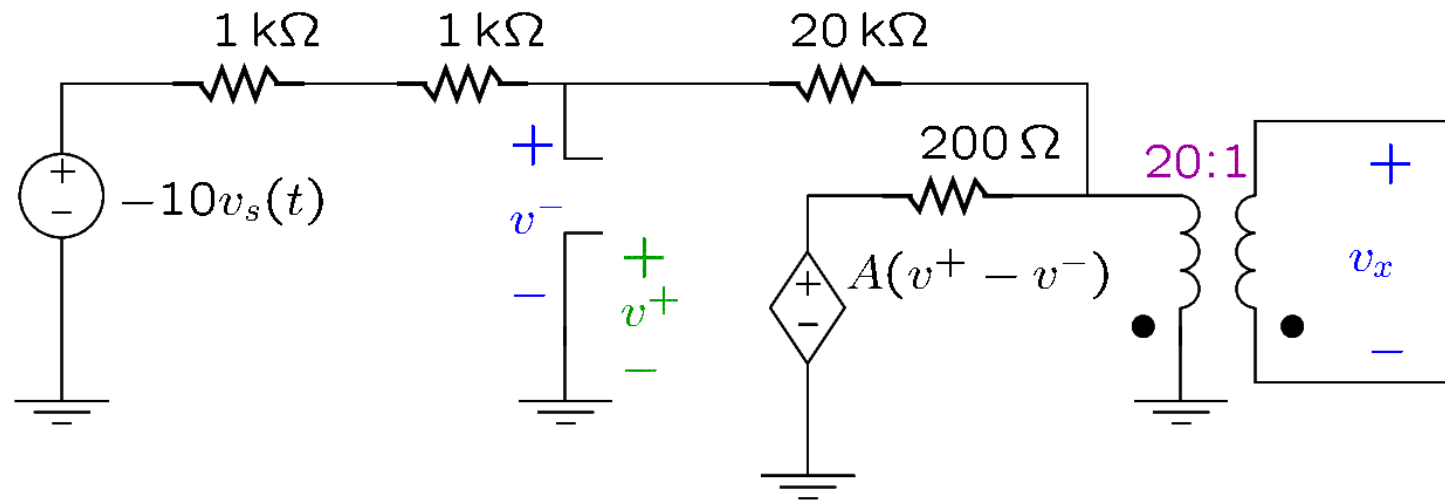
Example 1 (Continued)

- We have simplified the circuit to the form shown below.
- We can further simplify it by combining the $1\text{ k}\Omega$ resistors.
- Let us also notice that $v^+ = 0$.




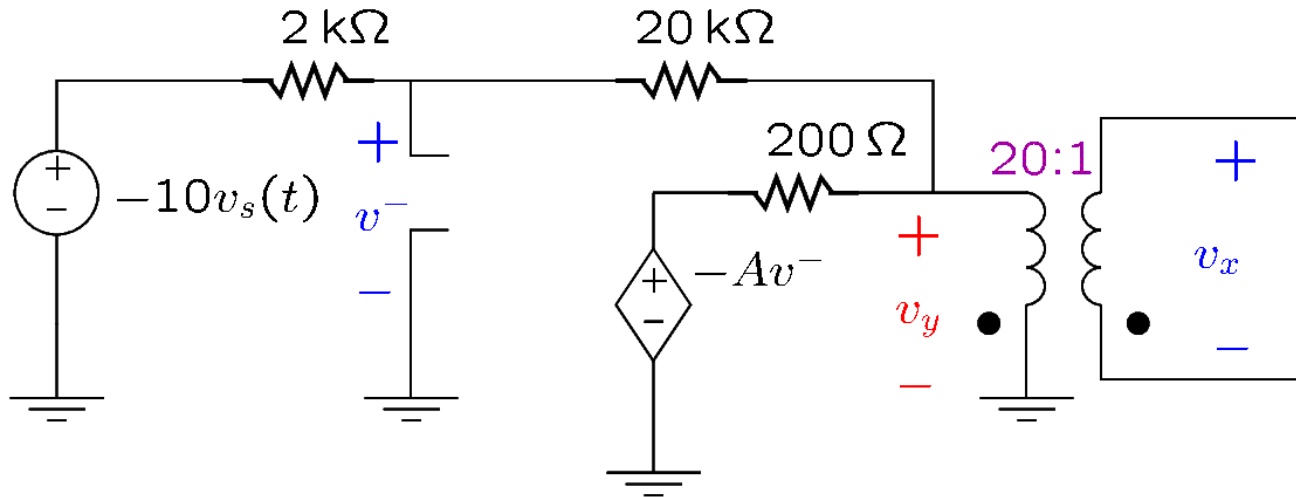Example 1 (Continued)

- We have simplified the circuit to the form below.




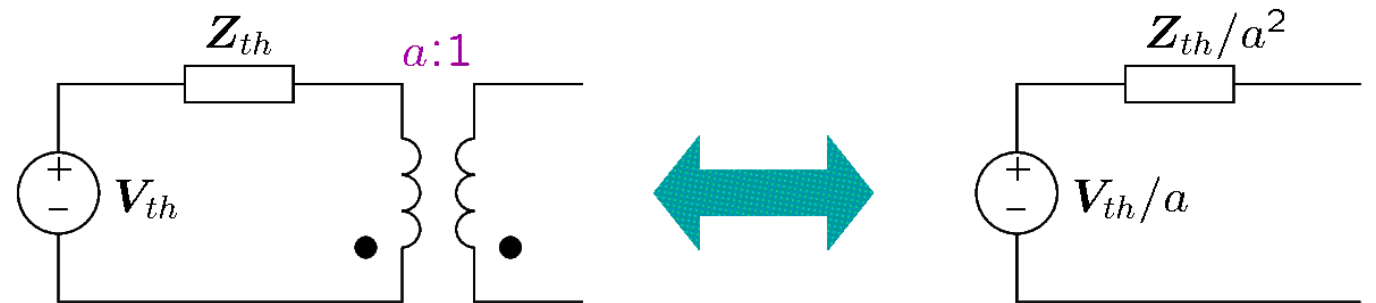- Now if we find the Thevenin equivalent between the nodes of v_y , we can obtain immediately the Thevenin equivalent between the nodes of v_x !



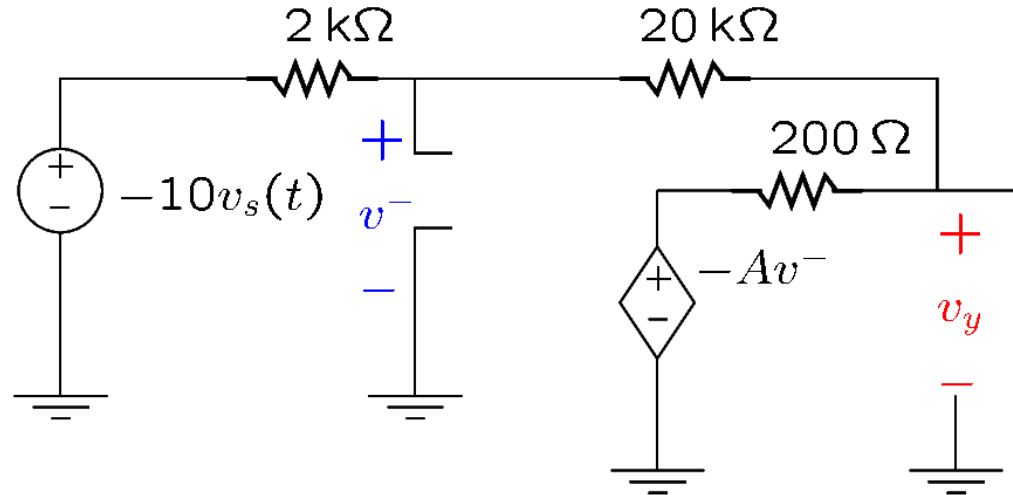Example 1 (Continued)

- Therefore, we will find first the Thevenin equivalent of this simpler circuit:



- The nodal equations are:

$$\frac{V_y - (-AV^-)}{200} + \frac{V_y - V^-}{20\text{ k}\Omega} = 0 \Rightarrow V_y = -V^- \frac{100A - 1}{101}$$


$$\frac{V^- - (-10V_s)}{2\text{ k}\Omega} + \frac{V^- - (-AV^-)}{20.2\text{ k}\Omega} = 0 \Rightarrow V^- = -V_s \frac{101}{A + 11.1}$$

Example 1 (Continued)

- We conclude that

$$V_{th} = V_y = V_s \frac{100A - 1}{A + 11.1} = 900 \angle 0^\circ \text{ mV}$$

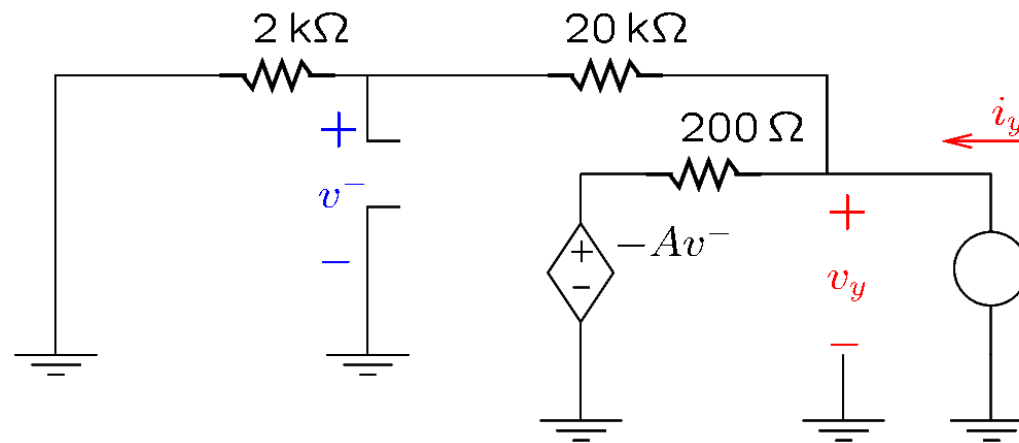- To find Z_{th} , we could find the short-circuit current or apply an external source.
- The external source method will be illustrated here.
- We will set to zero the independent sources and connect an external source between the nodes of v_y .



Example 1 (Continued)

- Note that

$$I_y = \frac{V_y}{2 \text{ k}\Omega + 20 \text{ k}\Omega} + \frac{V_y - (-AV^-)}{200 \Omega}$$


- By voltage division:

$$V^- = V_y \frac{2 \text{ k}\Omega}{2 \text{ k}\Omega + 20 \text{ k}\Omega}$$

- Substituting V^- :


$$I_y = \frac{V_y(111 + 10A)}{22 \text{ k}\Omega}$$
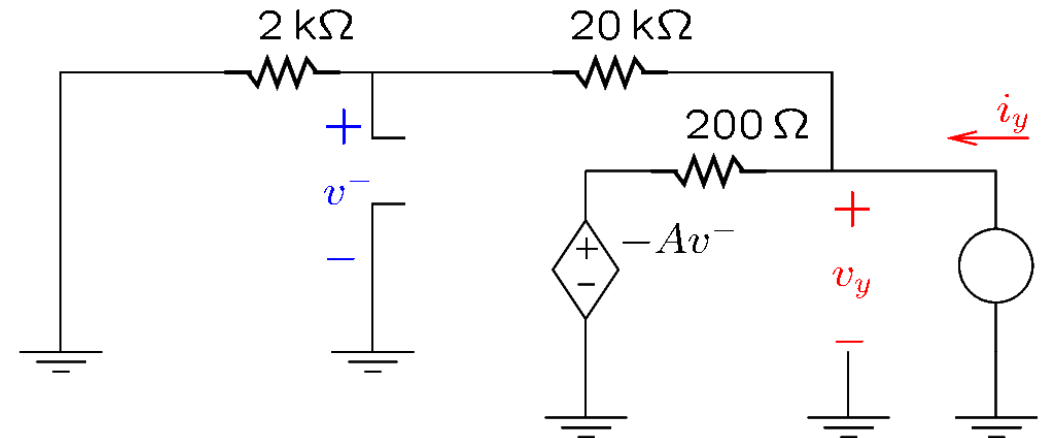
$$\Rightarrow \mathbf{Z_{th}} = \frac{V_y}{I_y} = \frac{22 \text{ k}\Omega}{111 + 10A} = \mathbf{19.8 \Omega}$$



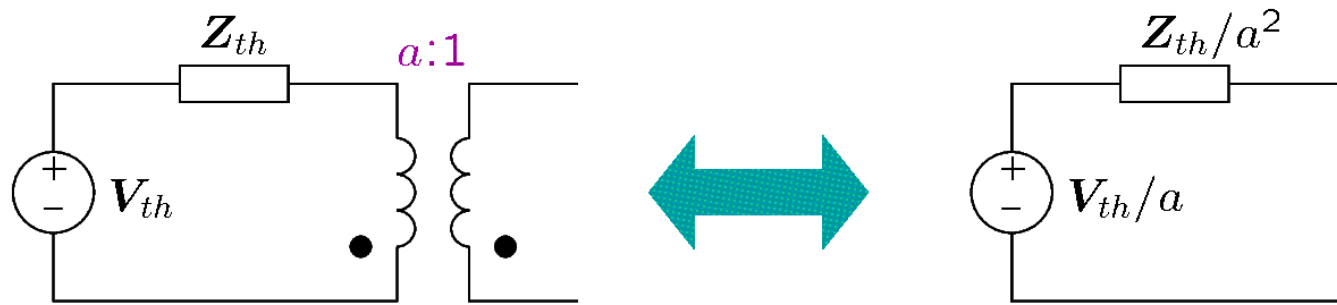Example 1 (Continued)

- At this point we need to take in account the last transformer in order to obtain the final result.
- As mentioned earlier, the effect of the transformer is:



- Since $a = 20$, the Thevenin equivalent between the nodes of V_x has

$$V_{x,th} = \frac{900}{20} = 45 \angle 0^\circ \text{ mV}$$

$$Z_{x,th} = \frac{19.8}{20^2} \Omega = 49.5 \angle 0^\circ \text{ m}\Omega$$

Example 2

Repeat the previous example for $A \rightarrow \infty$.


- Since the calculations were done in terms of A , we can simply take the limit:

$$V_{th} = \lim_{A \rightarrow \infty} V_s \frac{100A - 1}{A + 11.1} = 100V_s \Rightarrow V_{x,th} = \frac{V_{th}}{20} = 50 \angle 0^\circ \text{ mV}$$

$$Z_{th} = \lim_{A \rightarrow \infty} \frac{22 \text{ k}\Omega}{111 + 10A} \Rightarrow Z_{x,th} = 0$$

- However, the approximation $A \rightarrow \infty$ is used because it simplifies very much all calculations; it is unnecessary to solve for the unknowns in terms of A and then take the limit.

Example 2 (Continued)

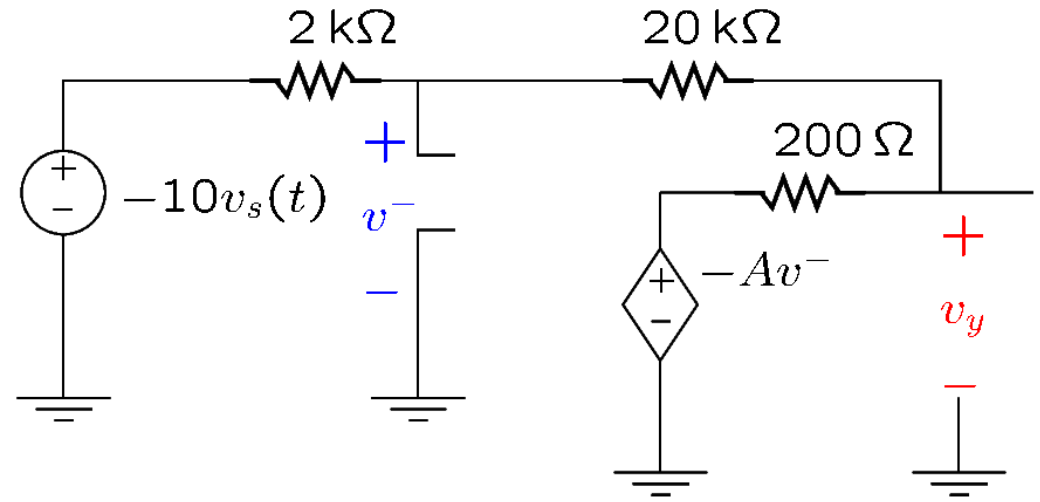

- Note that $A \rightarrow \infty$ implies $v^- \rightarrow 0$.
- Accounting for $V^- = 0$, the nodal equation of V^- is:

$$\frac{V_y - 0}{20\text{ k}\Omega} + \frac{-10V_s - 0}{2\text{ k}\Omega} = 0 \Rightarrow V_{th} = V_y = 100V_s$$

- Therefore,

$$V_{x,th} = \frac{V_{th}}{20} = 50\angle 0^\circ\text{ mV}$$

Example 2 (Continued)

- Moreover, when finding the Thevenin impedance with an external source, we can note that by voltage division:

$$V^- = V_y \frac{2 \text{ k}\Omega}{2 \text{ k}\Omega + 20 \text{ k}\Omega}$$

- Therefore, $V^- = 0 \Rightarrow V_y = 0 \Rightarrow Z_{th} = \frac{V_y}{I_y} = 0$

$$\Rightarrow Z_{x,th} = \frac{Z_{th}}{20^2} = 0$$

