

Review—Part 2

Example 1

A three-phase transformer steps down voltage to a Δ -connected load. The load operates at 30 kW and a power factor of 0.8 leading. The primary of the transformer is Δ -connected and the secondary is Y -connected. The turns ratio is $a = 0.1$. The line voltage of the primary is 2 kV rms. Find the impedance of the load, per phase, and the line current drawn by the primary of the transformer.

- *Since the primary is Δ -connected, the phase voltage of the primary equals the line voltage of the primary: $V_{p,phase} = V_{p,line} = 2 \text{ kV rms}$.*
- *The phase voltage of the secondary is: $V_{s,phase} = V_{p,phase} \cdot a = 200 \text{ V rms}$.*
- *Since the secondary is Y -connected, the line voltage of the secondary is: $V_{s,line} = \sqrt{3}V_{s,phase} = 200\sqrt{3} \text{ V rms}$.*
- *The load is connected to the secondary, so the secondary and the load have the same line voltage.*
- *The load is Δ -connected, so the phase voltage of the load equals the line voltage of the load: $V_{l,phase} = V_{s,line} = 200\sqrt{3} \text{ V rms}$.*

Example 1 (Continued)

- The total power of the load being 30 kW, the power per phase is 10 kW.
- The kW unit implies average power.
- The power factor is 0.8. Therefore, $\alpha_v - \alpha_i = \pm \cos^{-1} 0.8 = \pm 36.87^\circ$.
- Since the power factor is 0.8 **leading**, current leads voltage ($\alpha_v < \alpha_i$).
- Therefore, $\alpha_v - \alpha_i = -36.87^\circ$.

• The apparent power is $S = \frac{P}{\cos(\alpha_v - \alpha_i)} = 12.5 \text{ kVA}$.


• Assuming rms values, $S = V_{l,phase} I_{l,phase}$.

• Therefore, the phase current of the load is

$$I_{l,phase} = \frac{S}{V_{l,phase}} = \frac{12.5 \text{ kVA}}{200\sqrt{3} \text{ V rms}} = \frac{62.5}{\sqrt{3}} \text{ A rms.}$$

• The load impedance of each phase is:
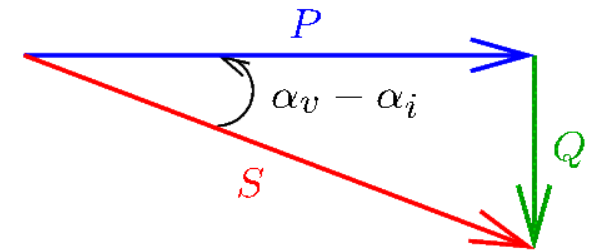
$$\mathbf{Z} = \frac{V_{l,phase}}{I_{l,phase}} = \frac{V_{l,phase}}{I_{l,phase}} \angle \alpha_v - \alpha_i = 9.6 \angle -36.87^\circ \Omega$$



Example 1 (Continued)


- The phase current of the load was shown to be $I_{l,phase} = \frac{62.5}{\sqrt{3}} \text{ A rms}$.
- Since the load is Δ -connected, the line current of the load is $I_{l,line} = \sqrt{3}I_{l,phase} = 62.5 \text{ A rms}$.
- Since the secondary of the transformer is Y -connected, it has the same line current: $I_{s,line} = 62.5 \text{ A rms}$.
- Since the secondary is Y -connected, the line and the phase currents are identical: $I_{s,phase} = I_{s,line} = 62.5 \text{ A rms}$.
- The phase current of the primary will be: $I_{p,phase} = a \cdot I_{s,phase} = 6.25 \text{ A rms}$.
- Since the primary is Δ -connected, the line current of the primary is

$$I_{p,line} = \sqrt{3}I_{p,phase} = 10.825 \text{ A rms}.$$

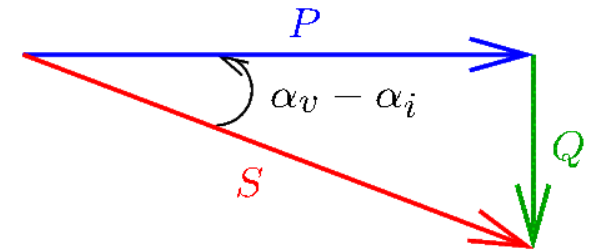Example 2

Indicate how the power factor can be corrected in the previous example.

- *The reactive power of the load, per phase, is $Q = S \sin(\alpha_v - \alpha_i) = -7.5 \text{ kVAR}$.*
- *To correct the power factor, we need to cancel the reactive power of the load.*
- *Only reactive elements have reactive power:*
 - *Capacitors generate reactive power.*
 - *Inductors absorb reactive power.*
- *Therefore, we need an additional inductive load of reactive power $Q_i = -Q = +7.5 \text{ kVAR}$, per phase.*
- *Let L be the inductance of each phase and $V_{i,phase}$ the rms phase voltage.*
- *Let $X = L\omega$ be the reactance of L .*



$$Q_i = \frac{V_{i,phase}^2}{X} \Rightarrow L = \frac{V_{i,phase}^2}{Q_i \omega}$$

Example 2 (Continued)

- Note that if the inductors are Y -connected, their value will be three times smaller than if they are Δ -connected.
- Assuming Y -connected inductors and a 60 Hz frequency:


$$L = \frac{V_{i,phase}^2}{Q_i \omega} = \frac{(200\sqrt{3} \text{ V} / \sqrt{3})^2}{7.5 \text{ kVAR} \cdot 2\pi \cdot 60 \text{ Hz}} = 14.147 \text{ mH}$$

Remarks

- Note that the admittance $\mathbf{Y} = \frac{1}{\mathbf{Z}} = G + jB$.
 - $G = \text{Real}(\mathbf{Y})$, the conductance, is the real part of \mathbf{Y} .
 - $B = \text{Imag}(\mathbf{Y})$, the susceptance, is the imaginary part of \mathbf{Y} .
- Any impedance \mathbf{Z} can be represented as $\mathbf{Z} = R_p || (jX_p)$, where $R_p = \frac{1}{G}$ and $X_p = -\frac{1}{B}$.
- Any impedance \mathbf{Z} can be represented also as $\mathbf{Z} = R + jX$, where
 - $R = \text{Real}(\mathbf{Z})$, the resistance, is the real part of \mathbf{Z} .
 - $X = \text{Imag}(\mathbf{Z})$, the reactance, is the imaginary part of \mathbf{Z} .


Remarks

- Let V_{rms} and I_{rms} be the rms voltage and current on an impedance \mathbf{Z} .
- If $\mathbf{Z} = R + jX$, note that:
 - The average power dissipated on \mathbf{Z} is $P = RI_{rms}^2$.
 - The reactive power absorbed by \mathbf{Z} is $Q = XI_{rms}^2$.
 - Let us note that X may be positive or negative.
- If we represent \mathbf{Z} instead as $\mathbf{Z} = R_p || (jX_p)$, then:
 - The average power dissipated on \mathbf{Z} is $P = V_{rms}^2/R_p$.
 - The reactive power absorbed by \mathbf{Z} is $Q = V_{rms}^2/X_p$.
- These equations can be derived immediately from $\mathbf{S} = P + jQ$, $\mathbf{S} = V_{rms}I_{rms}^*$, and $V_{rms} = \mathbf{Z}I_{rms}$.

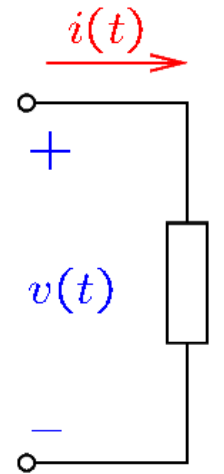


Remarks

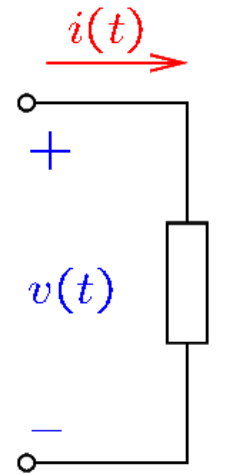- Thus, for a resistor: $\mathbf{Z} = R$, $P = RI_{rms}^2 = V_{rms}^2/R$ and $Q = 0$.
- For a capacitor: $\mathbf{Z} = jX$, $X = -1/\omega C$, $P = 0$ and $Q = XI_{rms}^2 = V_{rms}^2/X$.
- For an inductor: $\mathbf{Z} = jX$, $X = \omega L$, $P = 0$ and $Q = XI_{rms}^2 = V_{rms}^2/X$.




Example

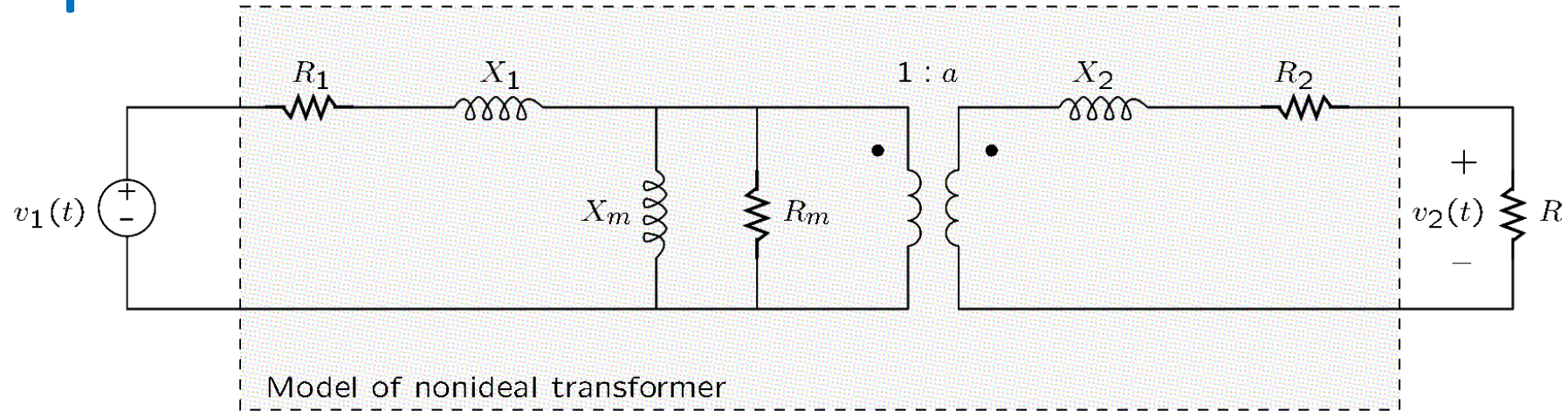

- One of the homework problems involves the circuit above.
- The average power of the resistor R is $P = V_2^2 / R$, where V_2 is the rms value of $v_2(t)$.
- A possible way to find the average power of the source is by finding the total power dissipated by the circuit.
- Let \mathbf{Z} be the total impedance seen by the source:

$$\mathbf{Z} = R_1 + jX_1 + (jX_m) \parallel R_m \parallel \left(\frac{jX_2}{a^2} + \frac{R_2}{a^2} + \frac{R}{a^2} \right)$$

Example (Continued)

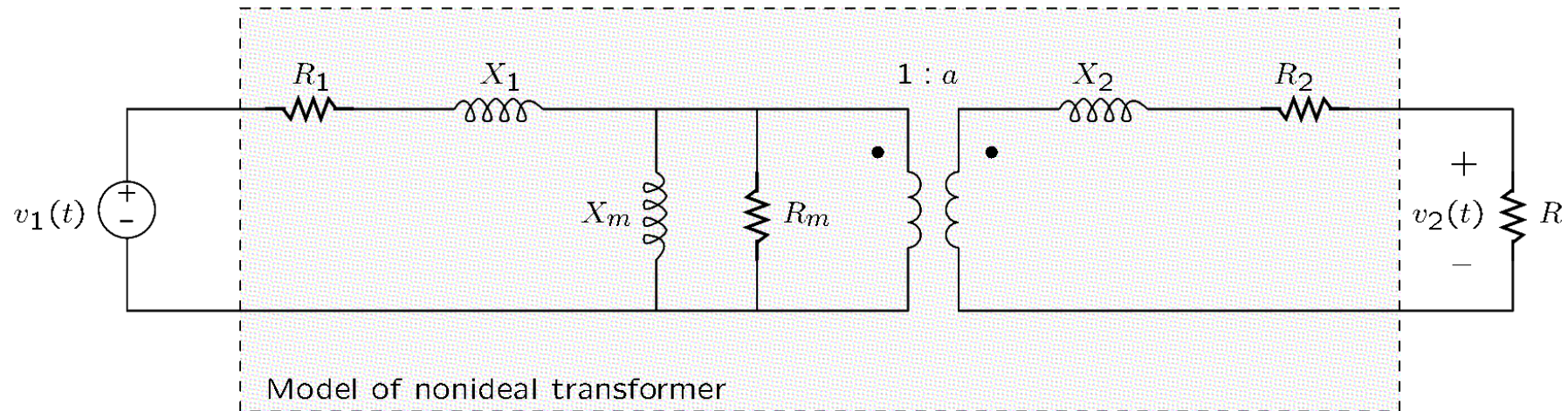

- Let $G = \text{Imag} \left(\frac{1}{Z} \right)$ be the imaginary part of the admittance.
- Let $R_p = \frac{1}{G}$.
- The average power dissipated by the circuit will be V_1^2 / R_p , where V_1 is the rms value of $v_1(t)$.