

# Controller Implementation— Operational Amplifiers

Discrete Time Approximations. Operational Amplifiers.


# Controller Implementation

- Control algorithms are commonly implemented on computers and microcontrollers.
  - This is a discrete-time implementation.
- Analog implementations can be done with analog electronic components such as *operational amplifiers*.
  - This is a continuous-time implementation of the control algorithms.
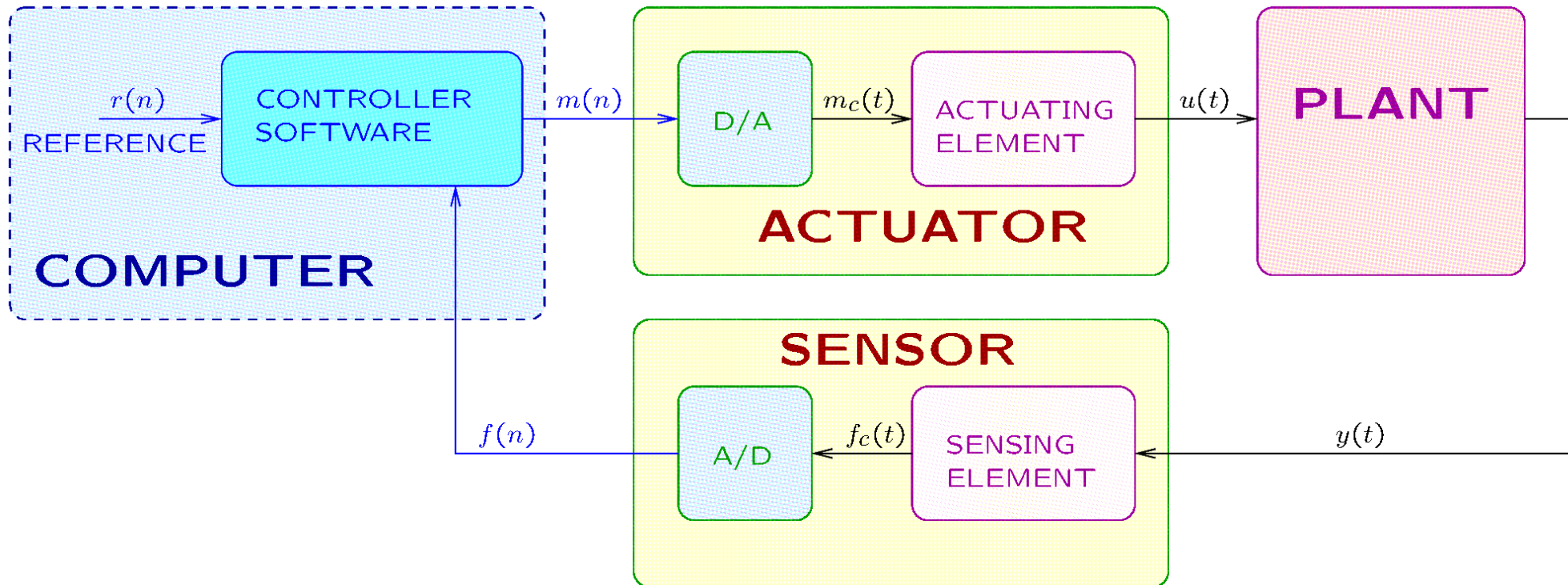
# Discrete-Time Implementation

The control system will include:


- Digital to analog converters (D/A).
- Analog to digital controllers (A/D).
- Software implementing the control algorithm.



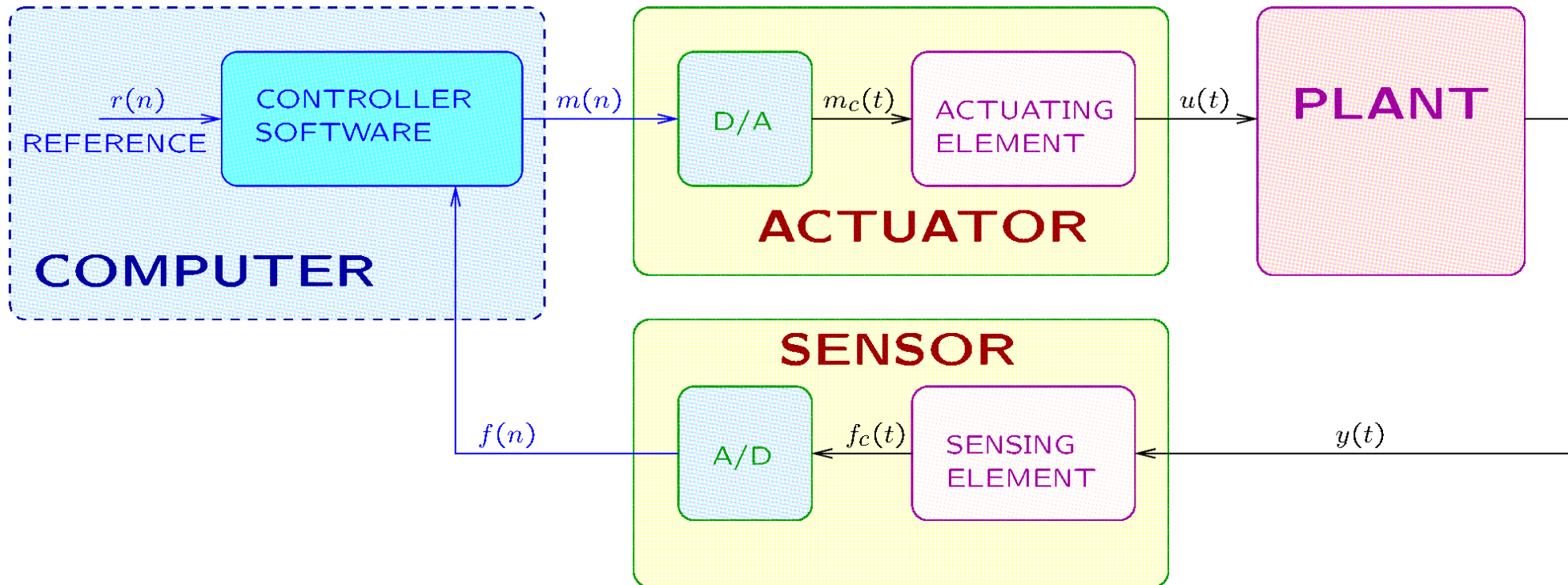
# Discrete-Time Implementation

The control system involves:

- Continuous-time signals:  $m_c(t)$ ,  $u(t)$ ,  $y(t)$ ,  $f_c(t)$ , where  $t$  is the time.
- Discrete-time signals:  $r(n)$ ,  $m(n)$ ,  $f(n)$ , where  $n = 0, 1, 2, \dots$  is an integer.



# Discrete-Time Implementation

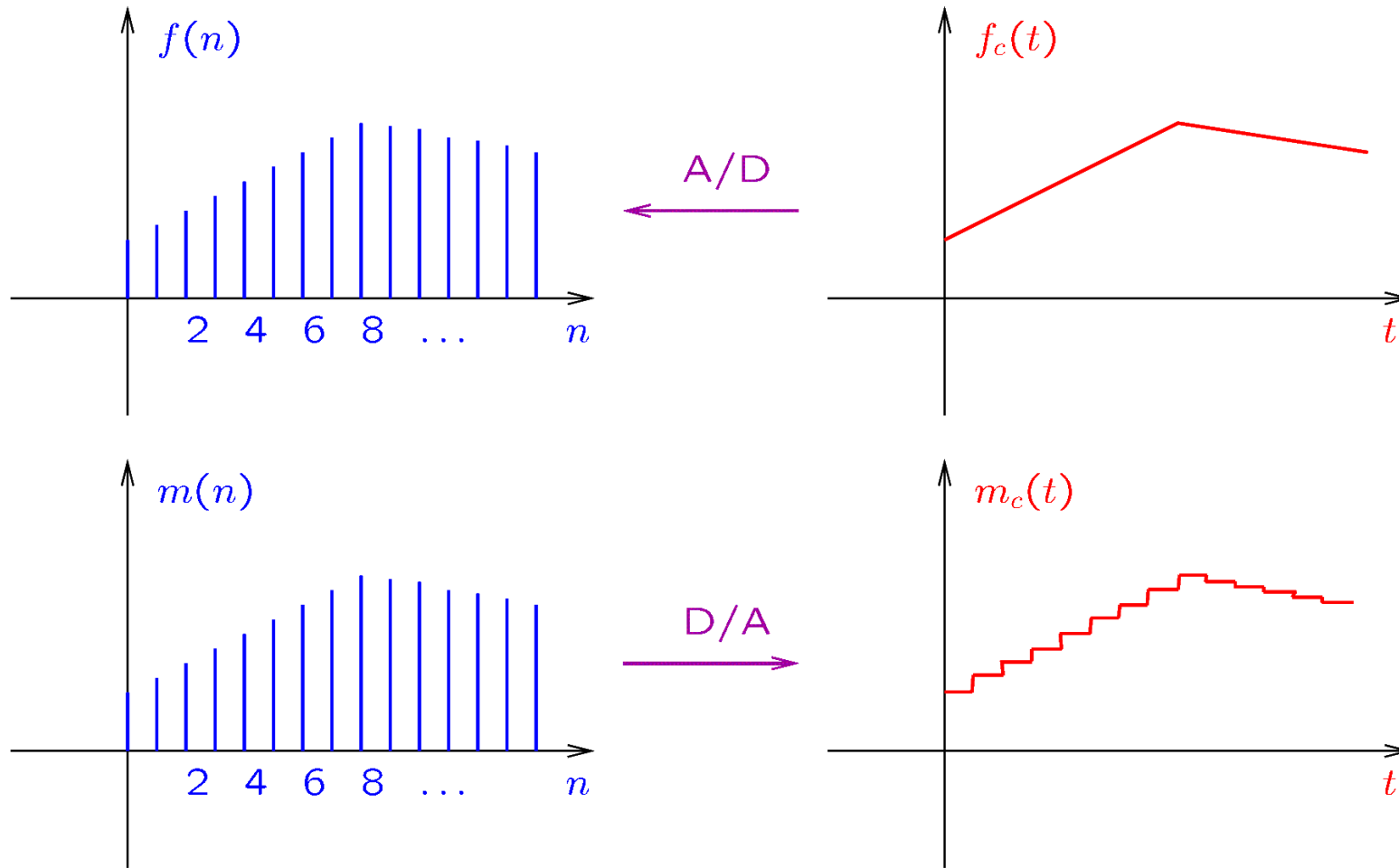

- The A/D samples periodically the input.
- Let  $T$  be the sampling interval.

$$f(n) = f_c(nT)$$

- The D/A outputs the latest discrete-time value:

$$m_c(t) = m(n) \text{ when } nT \leq t < (n+1)T$$

- The D/A output will change in steps.

# Discrete-Time Implementation

- Suppose that the following PID control law should be implemented in discrete time.

$$u_c(t) = k_p \cdot e_c(t) + k_i \int_0^t e_c(x) dx + k_d \cdot \dot{e}_c(t)$$

- The discrete-time controller should output  $u(n)$  so that

$$u_c(t) = u(n) \text{ when } nT \leq t < (n+1)T$$

- Moreover, the input of the controller should equal the samples of  $e_c(t)$ :

$$e(n) = e_c(nT)$$

- A possible way to implement the controller is by approximating the derivative and the integral.

$$\dot{e}_c(nT) \simeq \frac{e(n) - e(n-1)}{T}$$
$$\int_0^{nT} e_c(x) dx \simeq \int_0^{(n-1)T} e_c(x) dx + T \cdot e(n-1)$$

# Discrete-Time Implementation

- It follows that the discrete-time controller will be described by the equations:

$$u(n) = k_p e(n) + k_i v(n) + k_d \frac{e(n) - e(n-1)}{T}$$
$$v(n) = v(n-1) + T \cdot e(n-1)$$

where  $v(n)$  approximates the integral.

- *Note that the discrete-time control law depends on the sampling interval  $T$ .*

*Example: Find a discrete-time controller implementation of the continuous-time PID controller  $C(s) = 300 + \frac{0.4}{s} + 0.2s$ . Assume  $T = 10$  ms.*

- *Note that  $k_p = 300$ ,  $k_i = 0.4$ , and  $k_d = 0.2$ .*


$$u(n) = 300e(n) + 0.4v(n) + 0.2 \frac{e(n) - e(n-1)}{0.01}$$
$$= 320e(n) + 20e(n-1) + 0.4v(n)$$
$$v(n) = v(n-1) + 0.01 \cdot e(n-1)$$

# Continuous-Time Implementation

- A possible way to obtain a continuous-time implementation is using operational amplifiers.
- Operational amplifiers are widely used in electronic circuits.
- They allow precise implementations of gains and transfer functions.
  - In particular, they could be used to implement a PID control law.
  - They have been used in analog computers, which are devices simulating precisely solutions of differential equations.


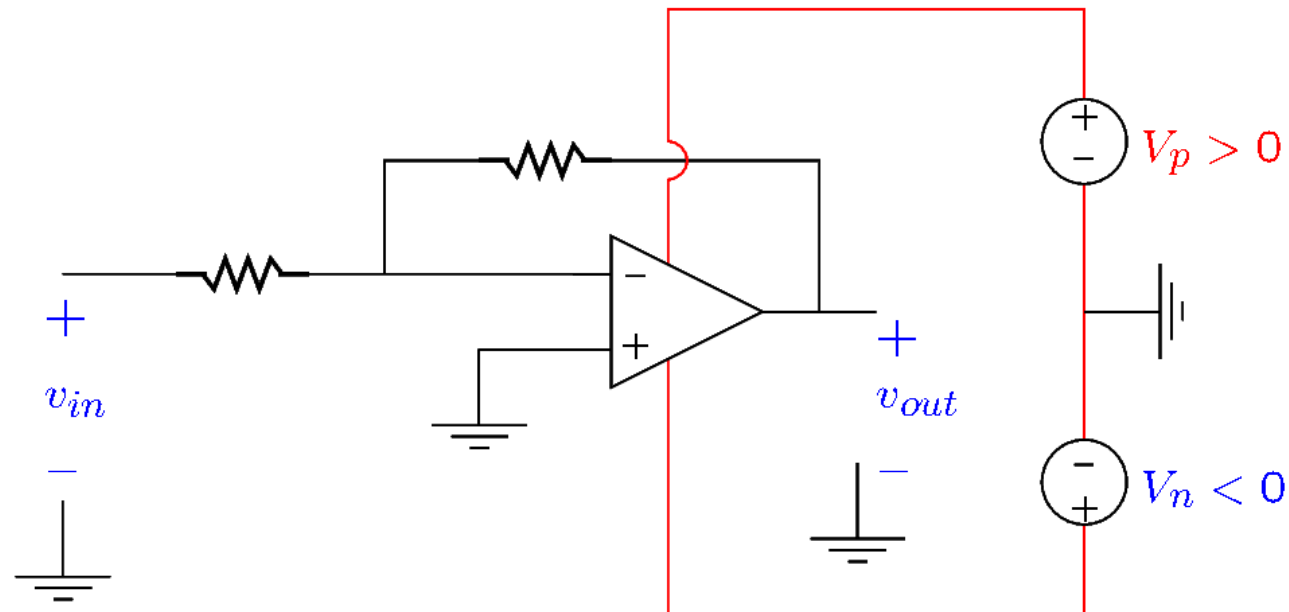
# Operational Amplifiers

- The figure shows an amplifier circuit that uses an operational amplifier.
- Operational amplifiers are commonly used to amplify signals.
- They have pins for the input and output signals (shown in black) and supply pins (shown in red) used to power the operational amplifier.


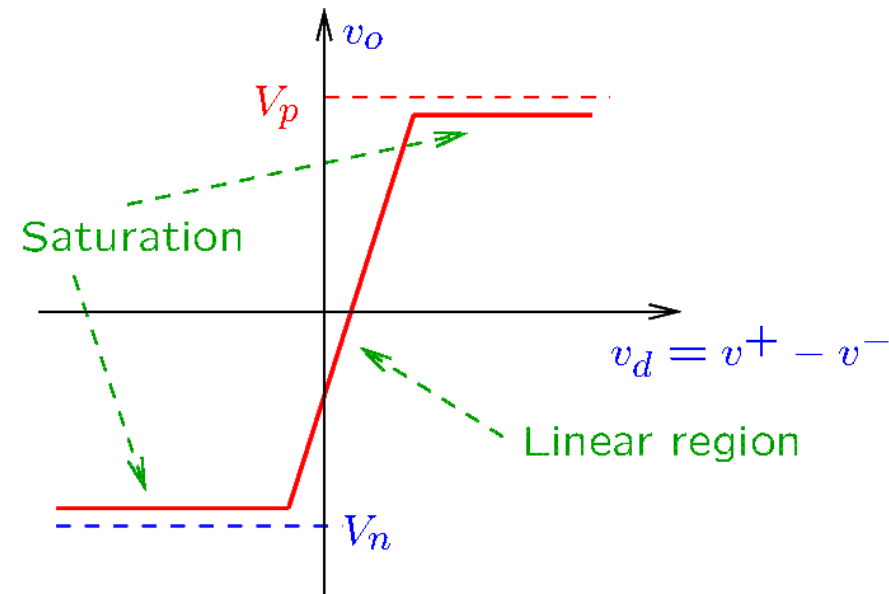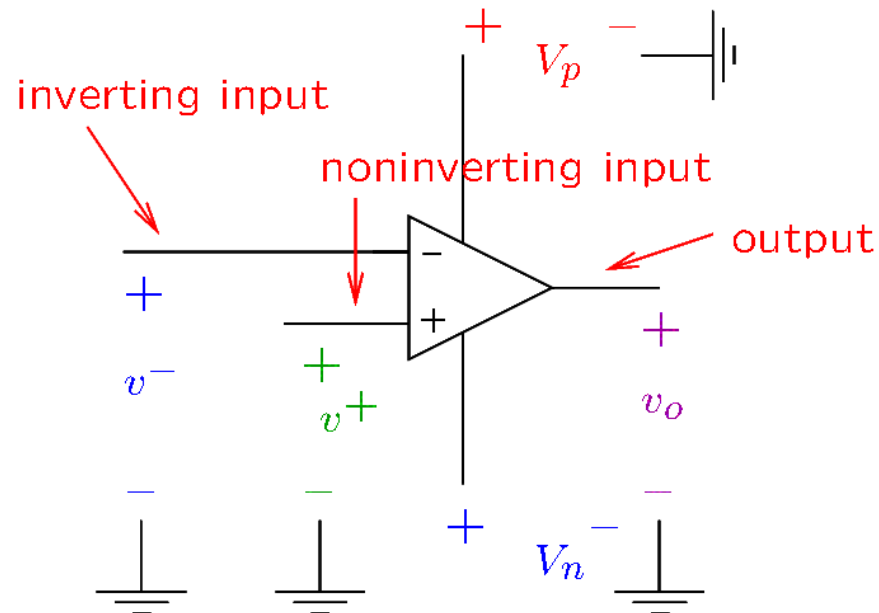
# Operational Amplifiers

- Let  $v^+$  be the *noninverting input* voltage and  $v^-$  the *inverting input* voltage.
- Let  $V_p$  be the voltage on the positive supply pin and  $V_n$  the voltage on the negative supply pin.
- In *saturation*, the output voltage is  $v_o \simeq V_p$  or  $v_o \simeq V_n$ .
- In the *linear region*,  $v_o \simeq A(v^+ - v^-)$ , where  $A$  is the operational amplifier **gain**.



# Operational Amplifiers


- Because the gain is typically very large:

$$v^+ \simeq v^- \text{ in the linear region.}$$


- The input currents are normally negligible:

$$i^+ \simeq i^- \simeq 0.$$

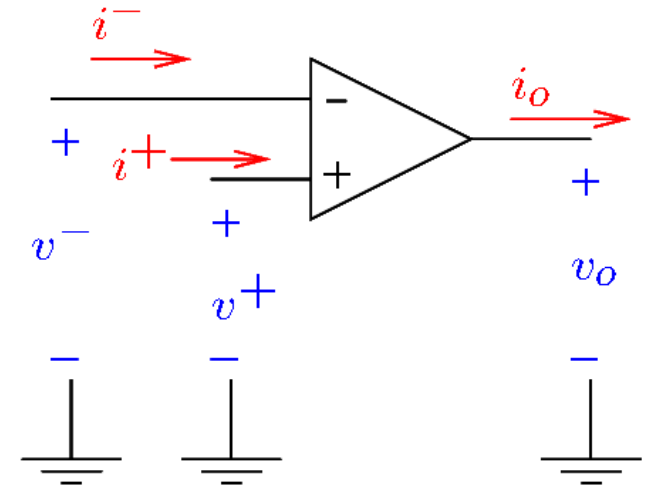- The equations  $v^+ = v^-$  and  $i^+ = i^- = 0$  can be used to solve operational amplifier circuits.




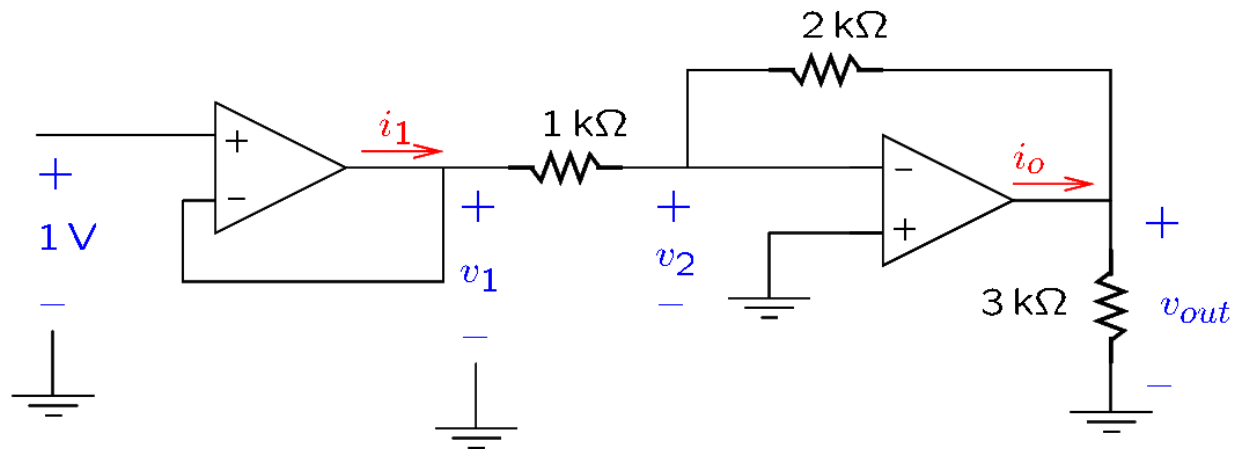*Example: Find the unknown voltages and currents. Assume linear region operation.*



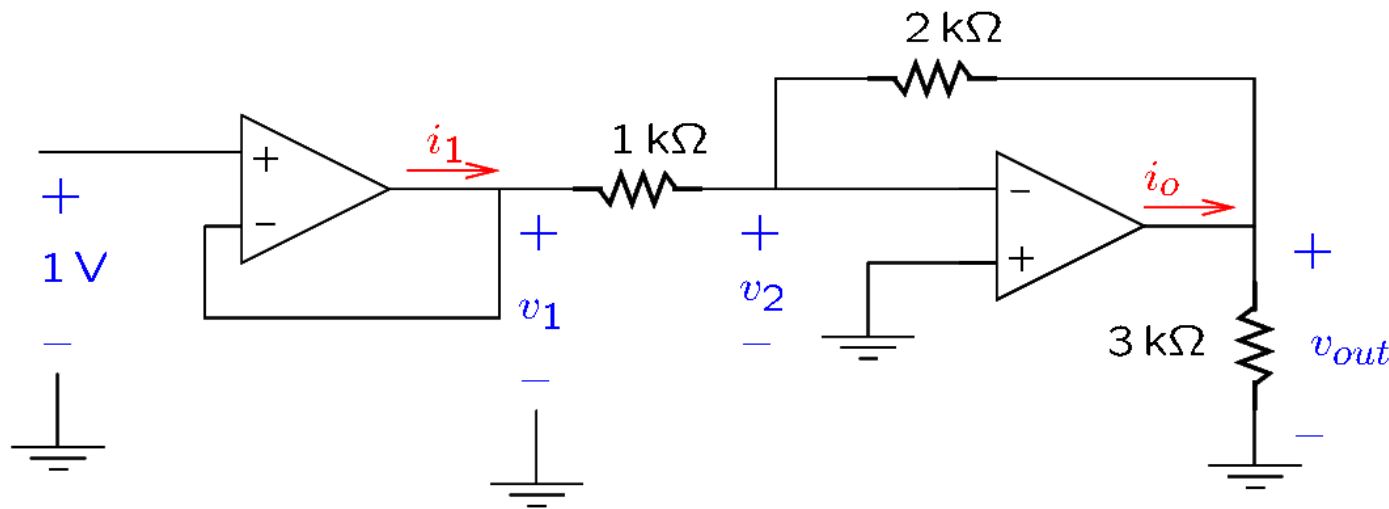
# Operational Amplifiers—Example

- For the first amplifier,  $v^+ = v^- \Rightarrow v_1 = 1 V$ .
- For the second amplifier,  $v^+ = v^- \Rightarrow v_2 = 0 V$ .
- Writing KCL at the node of  $v_1$ :  $i_1 = i^- + \frac{v_1 - v_2}{1 k\Omega} = 0 + \frac{1 - 0}{1 k\Omega} = 1 mA$ .
- Writing KCL at the node of  $v_2$ :  $\frac{v_1 - v_2}{1 k\Omega} + \frac{v_{out} - v_2}{2 k\Omega} = i^- = 0$ . Therefore,  $v_{out} = -2 V$ .
- Writing KCL at the node of  $v_{out}$ :  $i_o = \frac{v_{out}}{3 k\Omega} + \frac{v_{out} - v_2}{2 k\Omega} = -1.67 mA$ .


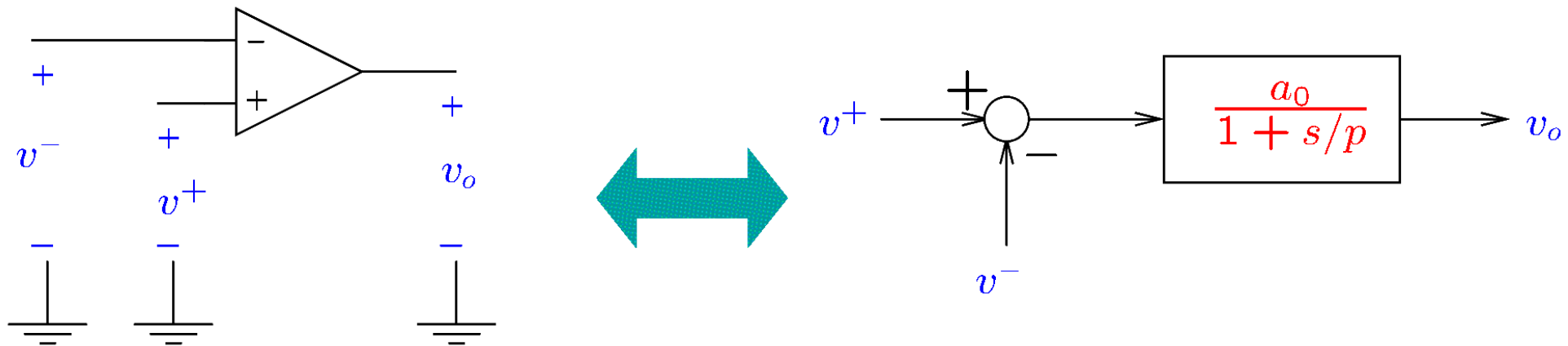
# Operational Amplifiers—Stability

- Circuits with operational amplifiers, if improperly designed, *can be unstable*.
- To understand instability, a first order approximation could be used for the transfer function.
  - The pole of the transfer function is often in the range  $-10$  to  $-100 \text{ rad/s}$ .
- The approximation refers to the linear region;  $a_0$  is the DC gain of the amplifier in the linear region.



# Operational Amplifiers—Stability Example


Example: The circuit and the block diagram below are equivalent.

$$V_f(s) = \beta V_o(s)$$

$$V_o(s) = \frac{a_0}{1 + \frac{s}{p}} (V_i(s) - V_f(s))$$

The closed-loop transfer function is:
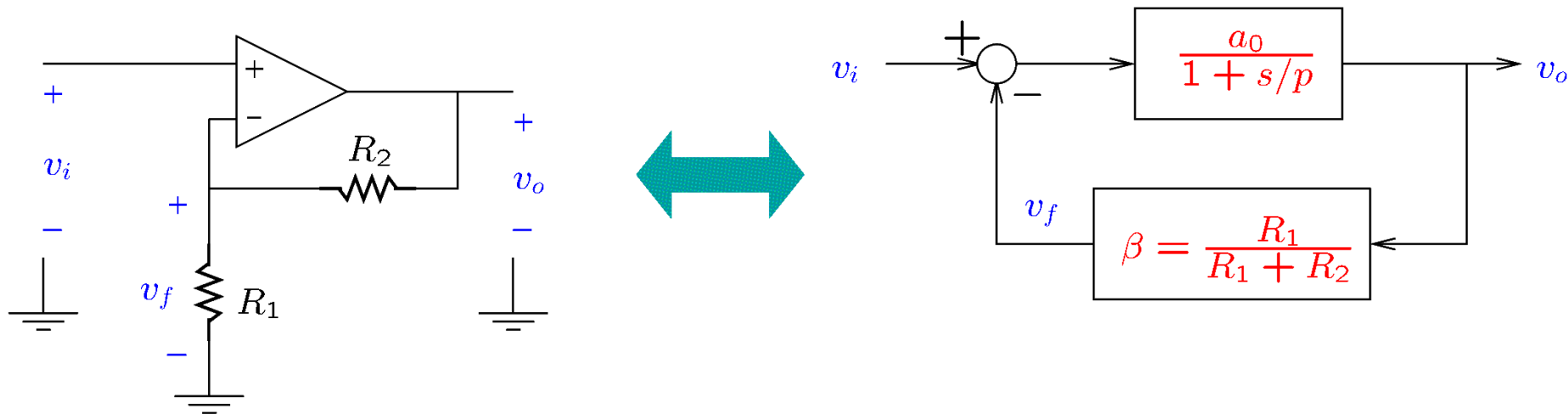
$$CL(s) = \frac{a_0}{1 + a_0\beta + s/p}$$





# Operational Amplifiers—Stability Example

The closed-loop transfer function is:

$$CL(s) = \frac{a_0}{1 + a_0\beta + s/p}$$

Since  $p > 0$ , the pole of the closed-loop transfer function is in the LHP.

Therefore, *the system is stable!*

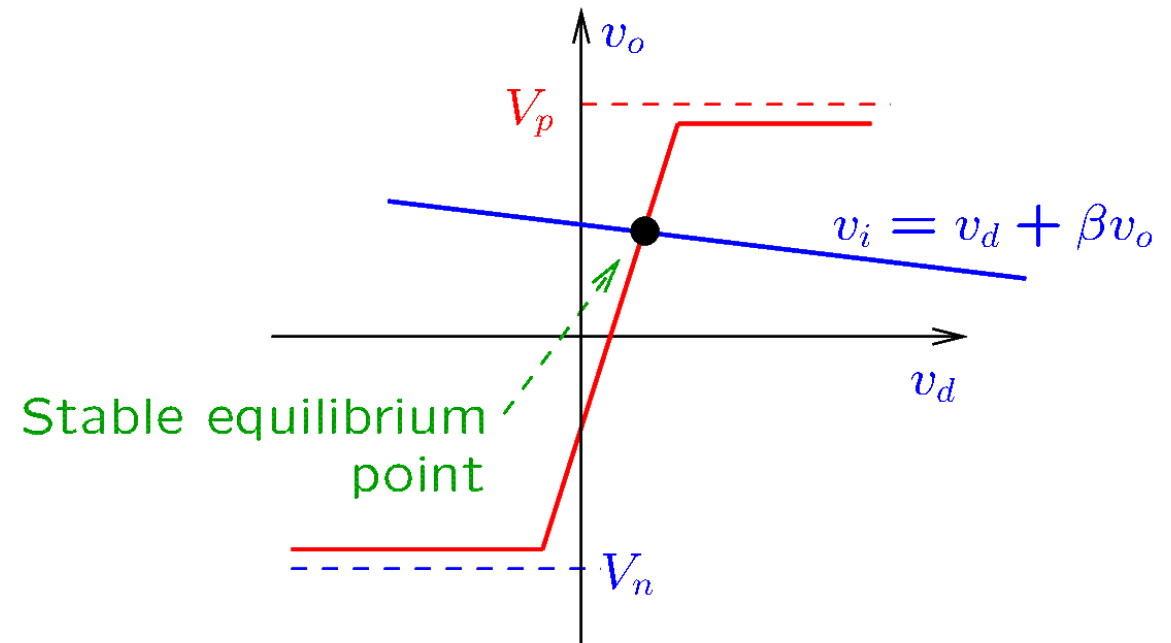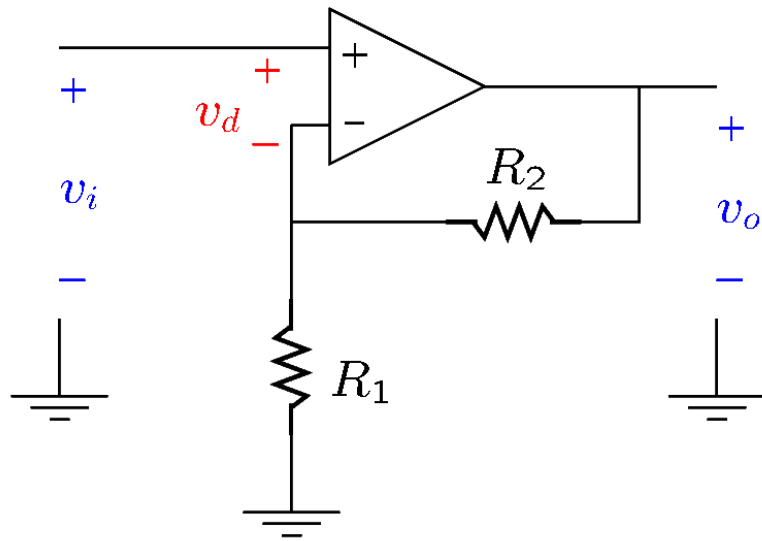


# Operational Amplifiers—Stability Example 2

*Example: Consider the previous circuit after interchanging the connections of the inputs of the operational amplifier.*

*The closed-loop transfer function is now:*

$$CL(s) = \frac{-a_0}{1 - a_0\beta + s/p}$$

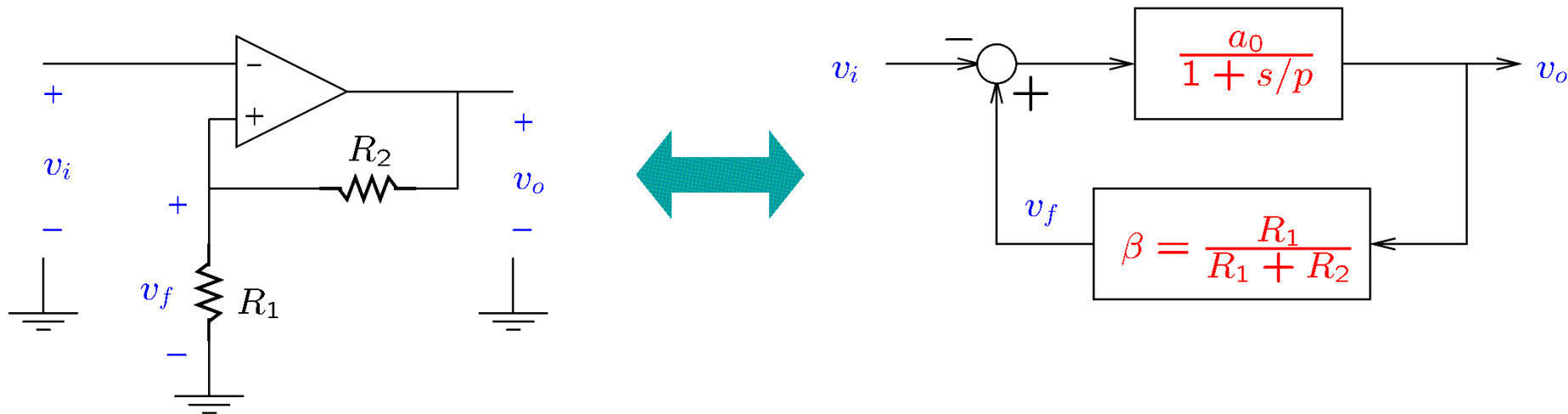*The pole is at  $p(a_0\beta - 1)$ . Unless  $a_0\beta < 1$ , which would be quite unusual, the pole is in the RHP and **the circuit is unstable** in the linear region.*





# Operational Amplifiers—Stability Example 2

*The circuit has three equilibrium points.*

*The equilibrium point in the linear region is unstable, as we have proved.*

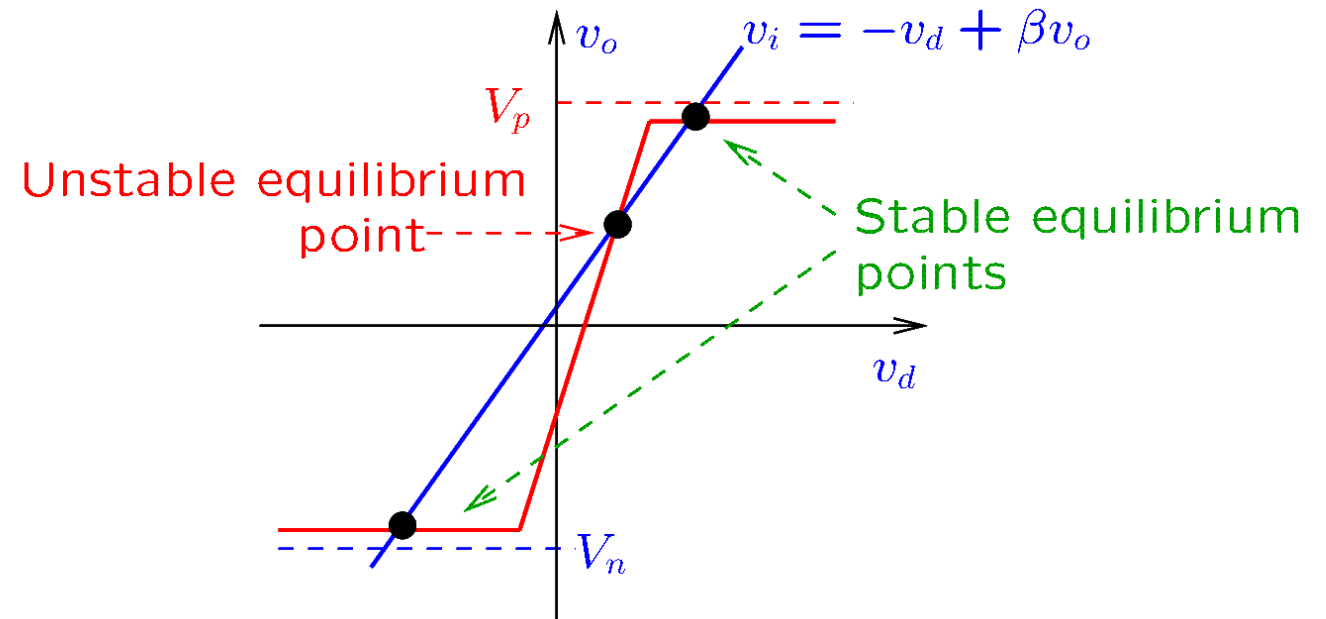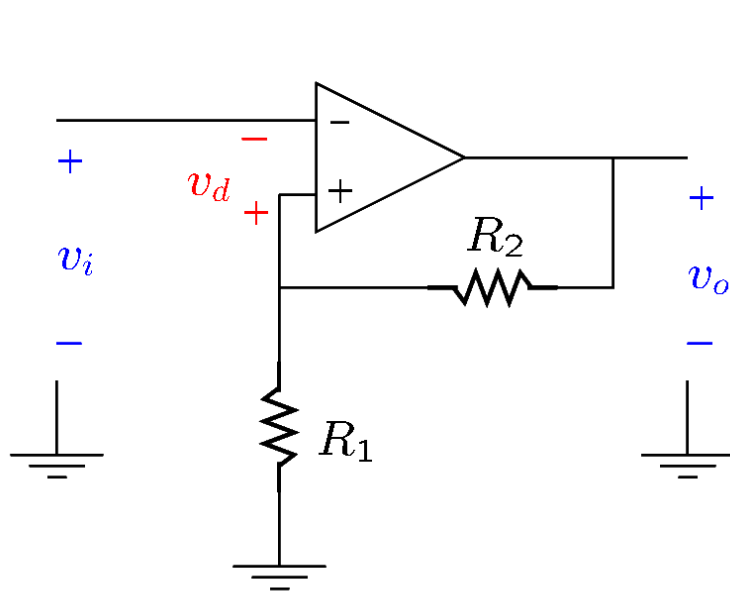*Therefore, the circuit will operate in one of the other two equilibrium points, outside of the linear region.*




# Block Diagrams and Operational Amplifiers

- Consider a block diagram representing a control algorithm.
- Suppose that the algorithm should be implemented in hardware.
- Various blocks can be implemented with operational amplifiers, including
  - Summing junctions
  - Transfer function blocks
- See the *operational amplifier handout*.
- For a more efficient implementation, several blocks could be combined and implemented with a single operational amplifier.
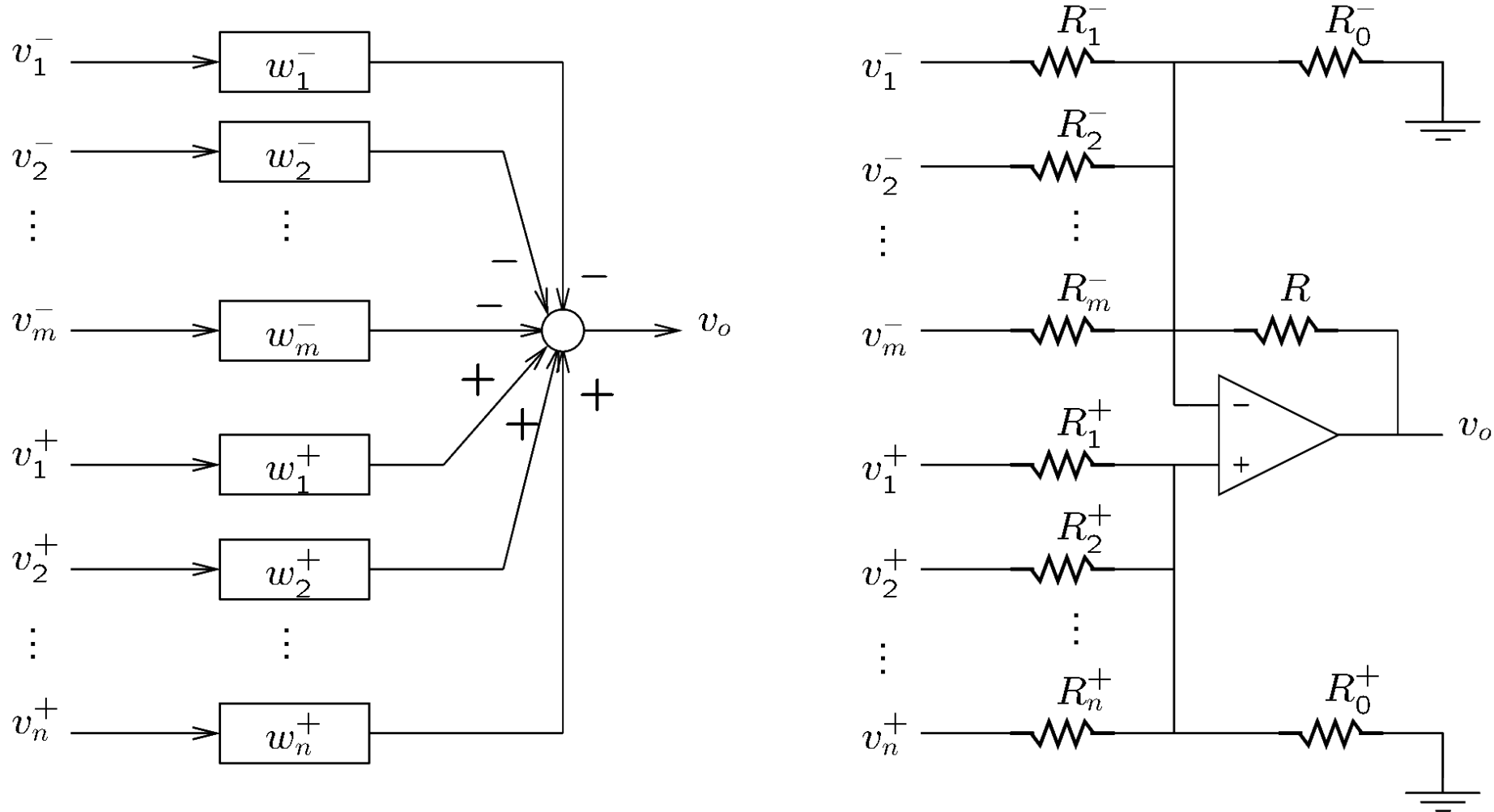
# Summing Junctions

An operational amplifier can implement the weighted sum  $v_o = \sum_i^n w_i^+ v_i^+ - \sum_i^m w_i^- v_i^-$ .



# Summing Junctions



- The weights  $w_1^+ \dots w_n^+$  and  $w_1^- \dots w_m^-$  are given.
- Select  $R_1^+ \dots R_n^+$  and  $R_1^- \dots R_m^-$  so that

$$w_i^+ = \frac{R}{R_i^+} \text{ and } w_i^- = \frac{R}{R_i^-}.$$

- Select  $R_0^+$  and  $R_0^-$  so that

$$1 + \sum_{i=0}^m \frac{R}{R_i^-} = \sum_{i=0}^n \frac{R}{R_i^+}.$$

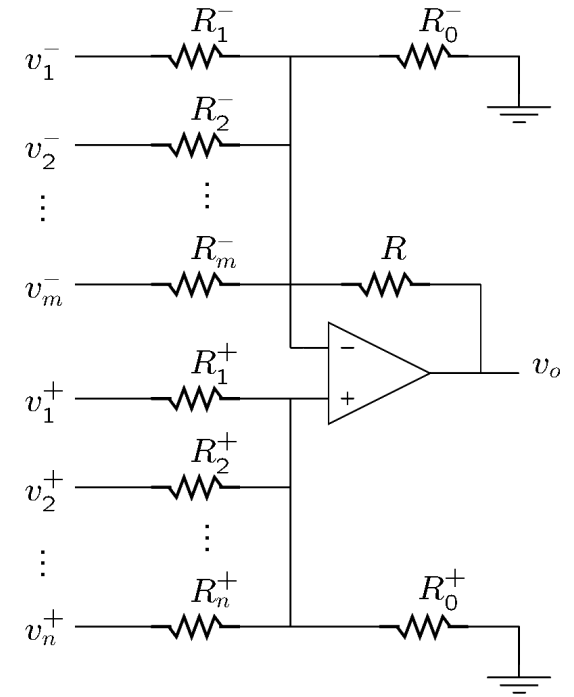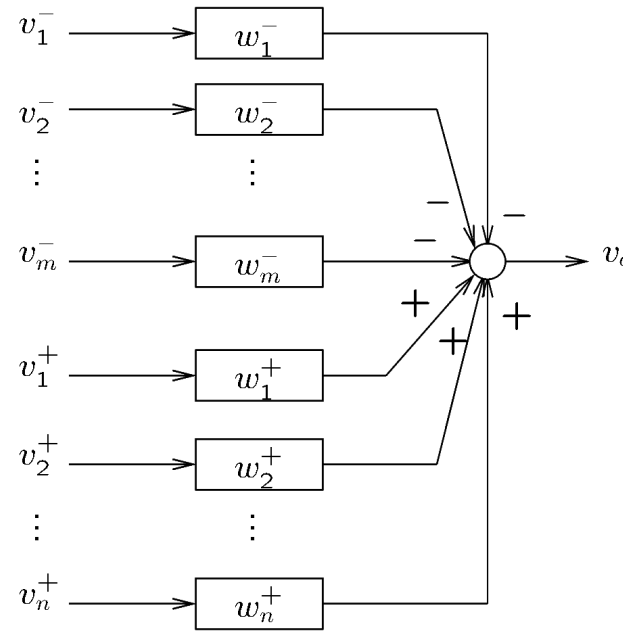- *Note that choosing  $R_0 = \infty$  is fine (this means open circuit—no resistor).*
- *The proof follows immediately via nodal analysis.*



# Summing Junctions—Example

Find a circuit implementing  $v_0 = 3v_1 - 2v_2 - 5v_3$ .

- There is one “+” input, so  $n = 1$ .
- There are two “-” inputs, so  $m = 2$ .
- The constraints for  $R_1^+$ ,  $R_1^-$ ,  $R_2^-$  are:

$$\frac{R}{R_1^+} = 3 \Rightarrow R_1^+ = \frac{R}{3}; \frac{R}{R_1^-} = 2 \Rightarrow R_1^- = \frac{R}{2}; \frac{R}{R_2^-} = 5 \Rightarrow R_2^- = \frac{R}{5}.$$

- The constraints for  $R_0^+$  and  $R_0^-$  are:


$$1 + \frac{R}{R_0^-} + \frac{R}{R_1^-} + \frac{R}{R_2^-} = \frac{R}{R_0^+} + \frac{R}{R_1^+} \Rightarrow 1 + \frac{R}{R_0^-} + 2 + 5 = \frac{R}{R_0^+} + 3.$$

- The equation has many possible solutions; the simplest is

$$R_0^+ = \frac{R}{5} \text{ and } R_0^- = \infty \text{ (no resistor)}$$
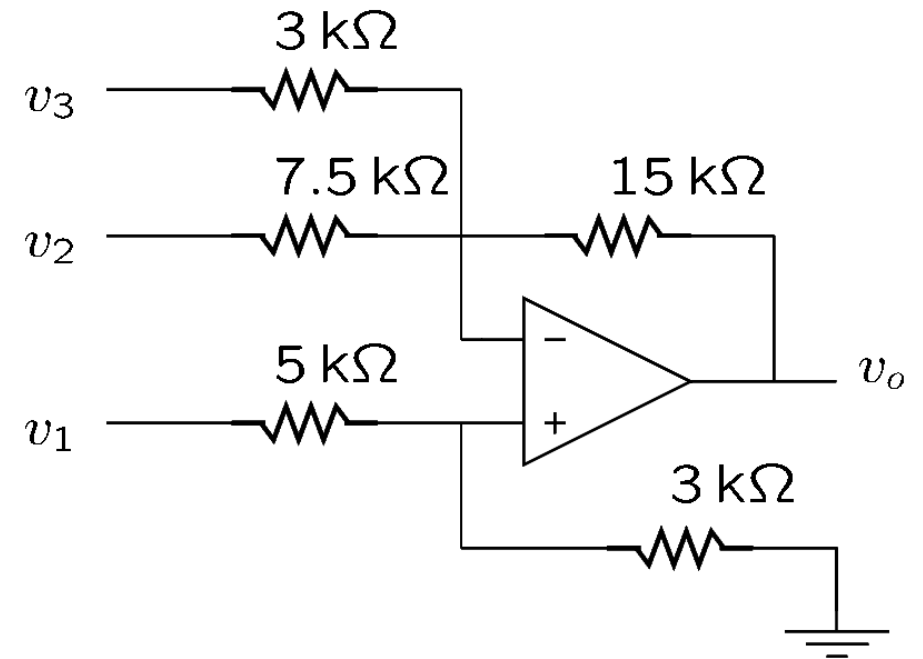
# Summing Junctions—Example


- Let  $R = 15 \text{ k}\Omega$  (this is an arbitrary choice).
- Then  $R_2^- = R_0^+ = 3 \text{ k}\Omega$ ,  $R_1^- = 7.5 \text{ k}\Omega$ , and  $R_1^+ = 5 \text{ k}\Omega$ .
- Potentiometers (variable resistors) may be needed to adjust precisely the weights of each input.


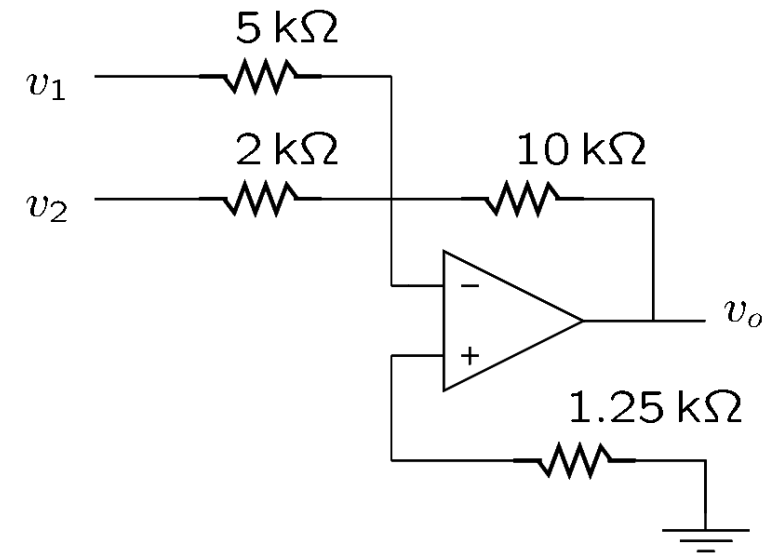
# Summing Junctions—Example 2


Find a circuit implementing  $v_0 = -2v_1 - 5v_2$ .

- There are no “+” inputs, therefore  $n = 0$ .
- There are 2 “-” inputs, therefore  $m = 2$ .
- $R_1^- = \frac{R}{2}$  and  $R_2^- = \frac{R}{5}$ .
- The constraint  $1 + \frac{R}{R_0^-} + \frac{R}{R_1^-} + \frac{R}{R_2^-} = \frac{R}{R_0^+}$  implies  $1 + \frac{R}{R_0^-} + 2 + 5 = \frac{R}{R_0^+}$ , for which we could choose  $R_0^- = \infty$  and  $R_0^+ = \frac{R}{8}$ .
- The figure shows an implementation with  $R = 10 \text{ k}\Omega$ .


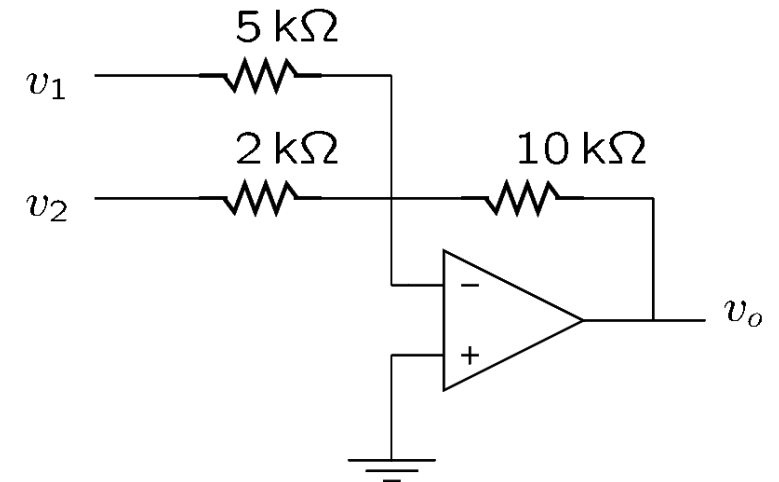
# Summing Junctions—Remarks


- *The method presented here does not lead to unique solutions.*
- *For example, the circuit shown here is also a solution of the previous example.*
- *However, the solution we have obtained earlier is better, as it can reduce the effect of the bias currents  $i^-$  and  $i^+$ , which we normally neglect.*


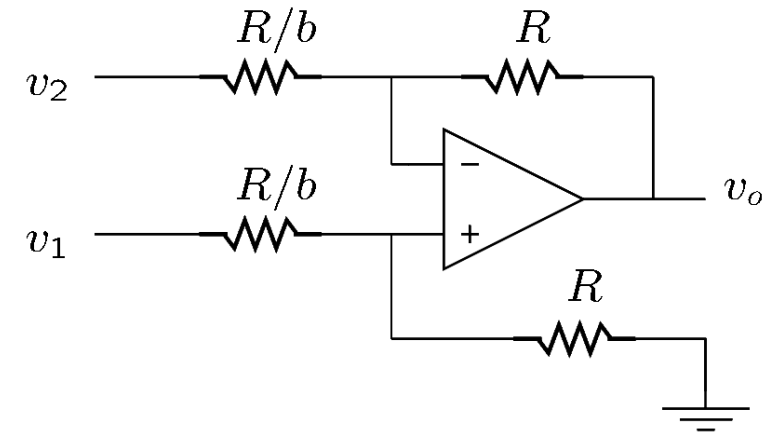
# Summing Junctions—Example 3


Find a circuit implementing  $v_o = bv_1 - bv_2$ , where  $b$  is a constant.

- There is one “+” input, so  $n = 1$ .
- There is one “-” input, so  $m = 1$ .
- $R_1^- = \frac{R}{b}$  and  $R_1^+ = \frac{R}{b}$ .
- The constraint  $1 + \frac{R}{R_0^-} + \frac{R}{R_1^-} = \frac{R}{R_0^+} + \frac{R}{R_1^+}$  implies  $1 + \frac{R}{R_0^-} + b = \frac{R}{R_0^+} + b$ , for which we could choose  $R_0^- = \infty$  and  $R_0^+ = R$ .
- The figure shows the circuit.


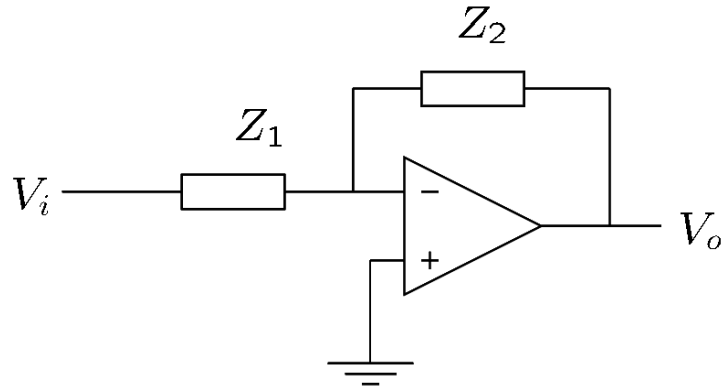
# Transfer Functions

- Transfer functions can be implemented with resistors, capacitors, and *the inverting amplifier*:











- The circuit implements the transfer function

$$\frac{V_o(s)}{V_i(s)} = -\frac{Z_2}{Z_1}$$

- Each of  $Z_i$  and  $Z_f$  can be a capacitor, resistor, or a combination of the two.
- This solution is not unique; there are other ways to implement a transfer function.

TIME  
DOMAIN

FREQUENCY  
DOMAIN

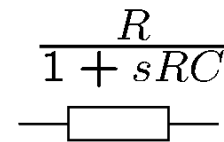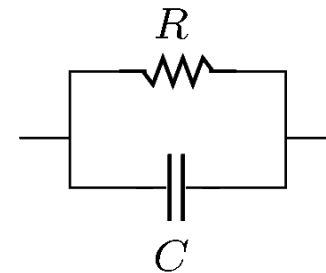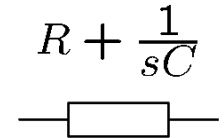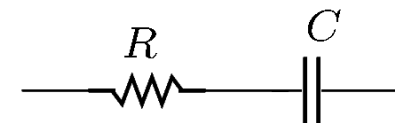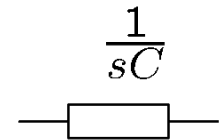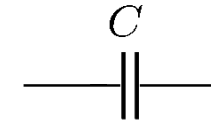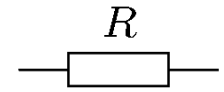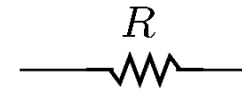

# Transfer Functions—Example

Implement the transfer function  $-\frac{100}{s+10}$ .

- Let  $Z_1 = R_1$  and  $Z_2 = \frac{R_2}{1+sR_2C_2}$ .

- The transfer function is

$$\frac{V_o(s)}{V_i(s)} = -\frac{Z_2}{Z_1} = -\frac{R_2/R_1}{1+sR_2C_2}$$

- Let us rewrite the given transfer function in a more convenient form:









$$-\frac{100}{s+10} = -\frac{10}{1+0.1s}$$

- We have the constraints

$$\frac{R_2}{R_1} = 10 \text{ and } R_2C_2 = 0.1.$$

TIME  
DOMAIN

FREQUENCY  
DOMAIN

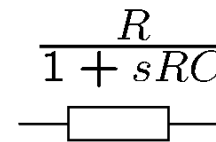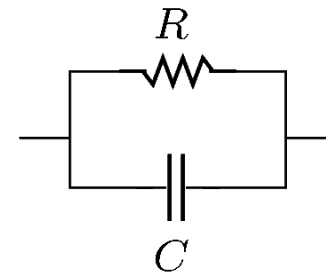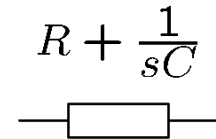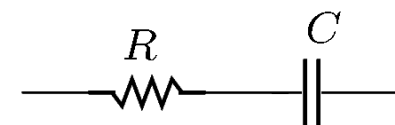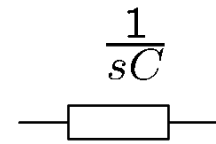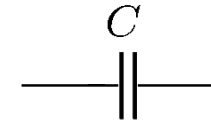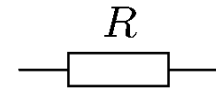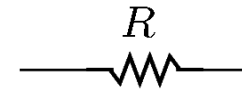

# Transfer Functions—Example


- We have the constraints

$$\frac{R_2}{R_1} = 10 \text{ and } R_2 C_2 = 0.1.$$

- We can choose (arbitrarily) the value of one variable and then solve for the other two.

- Let  $R_2 = 1 \text{ M}\Omega$ .
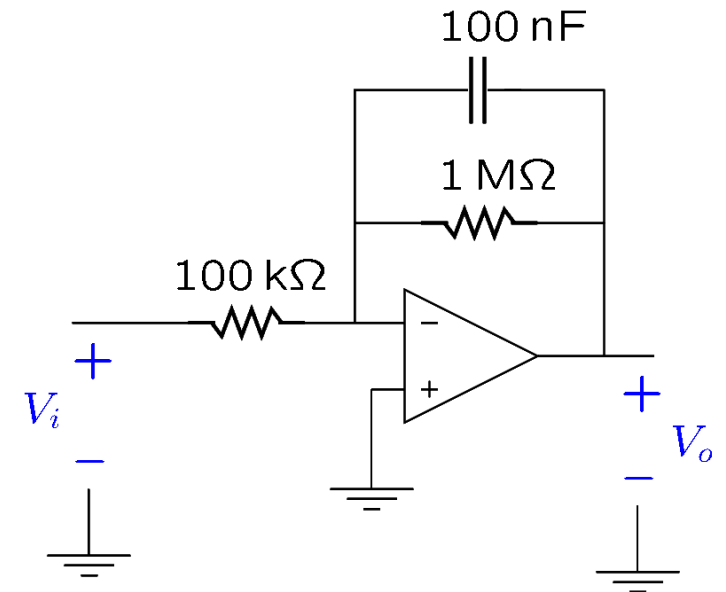
$$\Rightarrow R_1 = 100 \text{ k}\Omega \text{ and } C_2 = 100 \text{ nF}.$$



# Transfer Functions—Example 2

Implement the transfer function  $-100 \cdot \frac{s+10}{s+100}$ .

- Let  $Z_1 = \frac{R_1}{1+sR_1C_1}$  and  $Z_2 = \frac{R_2}{1+sR_2C_2}$ .

- The transfer function is

$$\frac{V_o(s)}{V_i(s)} = -\frac{Z_2}{Z_1} = -\frac{R_2}{R_1} \cdot \frac{1+sR_1C_1}{1+sR_2C_2}$$

- Let us rewrite the given transfer function in a more convenient form:









$$-100 \cdot \frac{s+10}{s+100} = -10 \frac{1+0.1s}{1+0.01s}$$

- We have the constraints

$$\frac{R_2}{R_1} = 10 \text{ and } R_2C_2 = 0.01 \text{ and } R_1C_1 = 0.1.$$

TIME  
DOMAIN

FREQUENCY  
DOMAIN

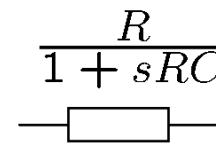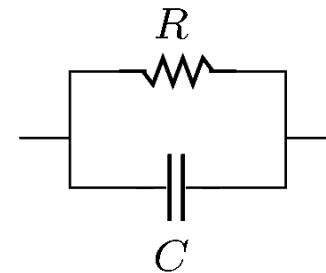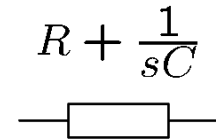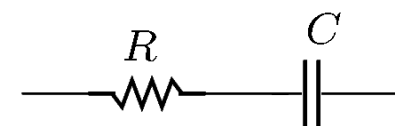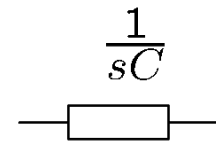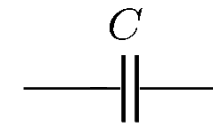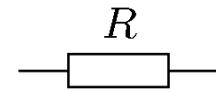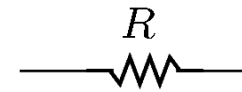

# Transfer Functions—Example 2

- We have the constraints


$$\frac{R_2}{R_1} = 10 \text{ and } R_2 C_2 = 0.01 \text{ and } R_1 C_1 = 0.1.$$

- We can choose (arbitrarily) the value of one variable and then solve for the other two.

- Let  $R_2 = 1 \text{ M}\Omega$ .



$$\Rightarrow C_2 = 10 \text{ nF and } R_1 = 100 \text{ k}\Omega$$

$$\Rightarrow C_1 = 1 \mu\text{F}$$

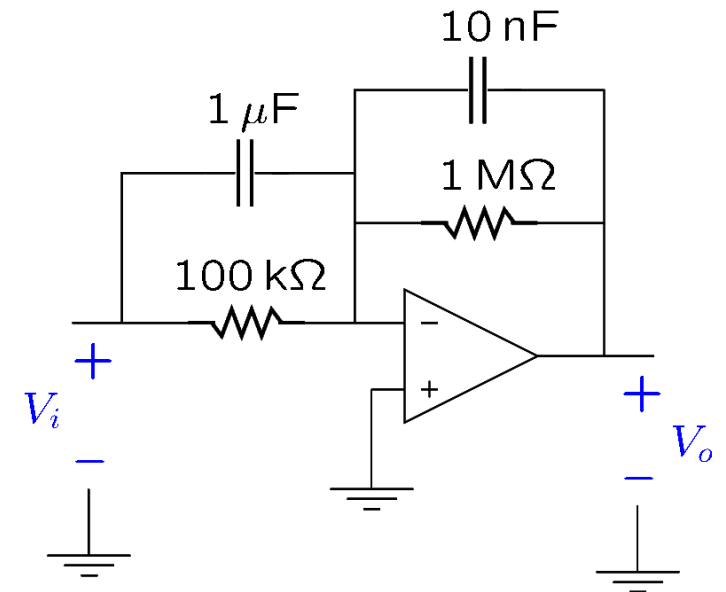
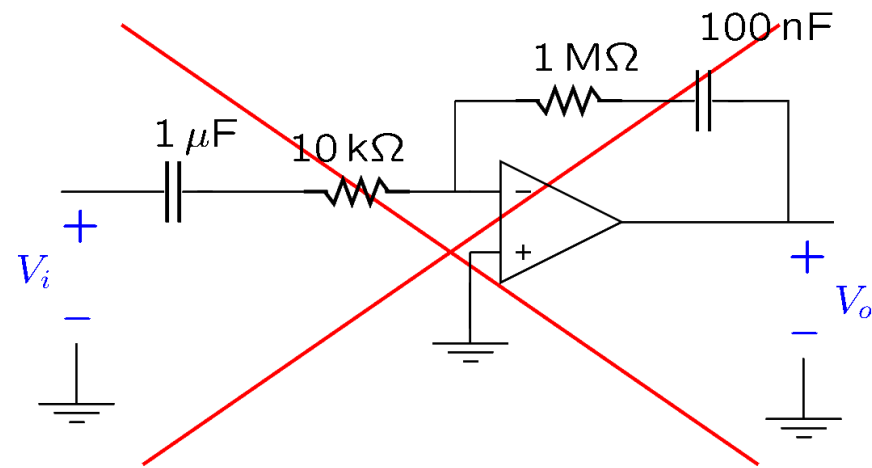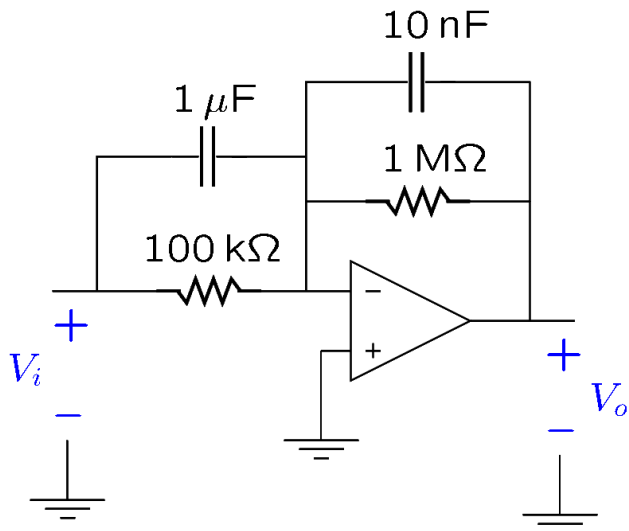
# Transfer Functions—DC Paths


- Though the bias DC currents  $i^-$  and  $i^+$  are normally negligible, they are present and should not be ignored.
- A valid solution should ensure that the DC currents  $i^-$  and  $i^+$  can flow.
  - Otherwise, the operational amplifier will malfunction.
- Note that capacitors block DC current; they should not block  $i^-$  and  $i^+$ .
- For example, the two circuits below would be expected to have the same transfer function. The right circuit, however, is incorrect because it blocks  $i^-$ .



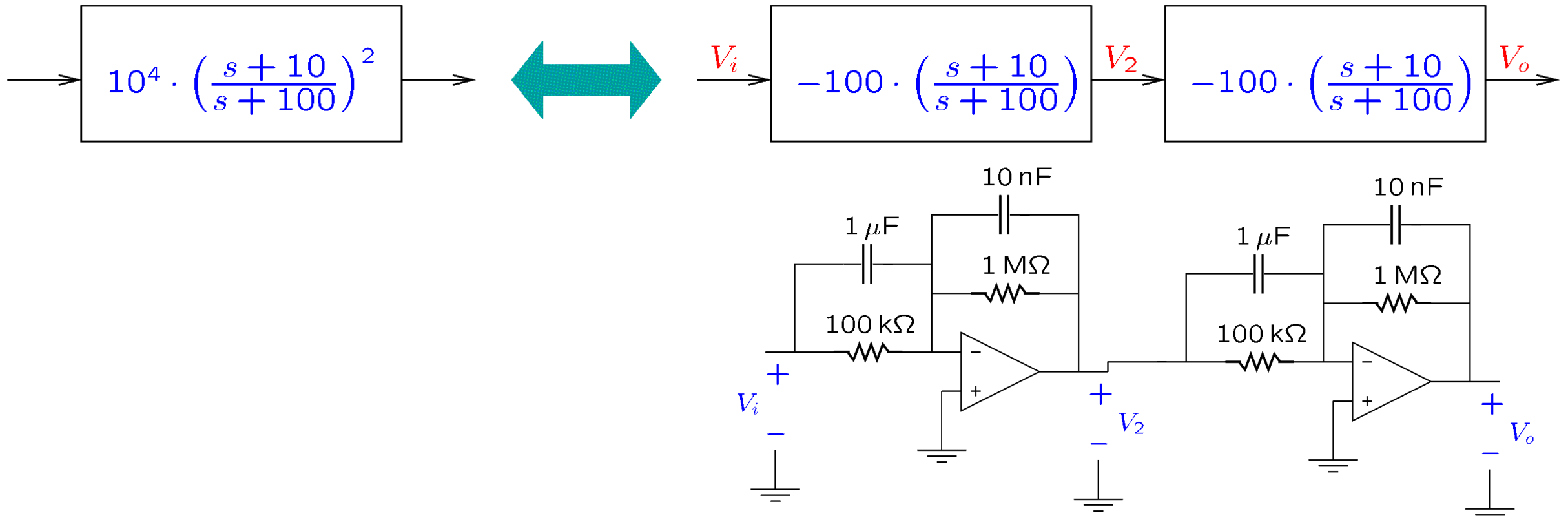
# Transfer Functions—Example 3

Implement the transfer function  $10^4 \cdot \left(\frac{s+10}{s+100}\right)^2$ .

- The desired transfer function is the square of the transfer function of Example 2.
- Therefore, it can be implemented by two identical cascaded amplifier stages.




# Transfer Functions—Example 4

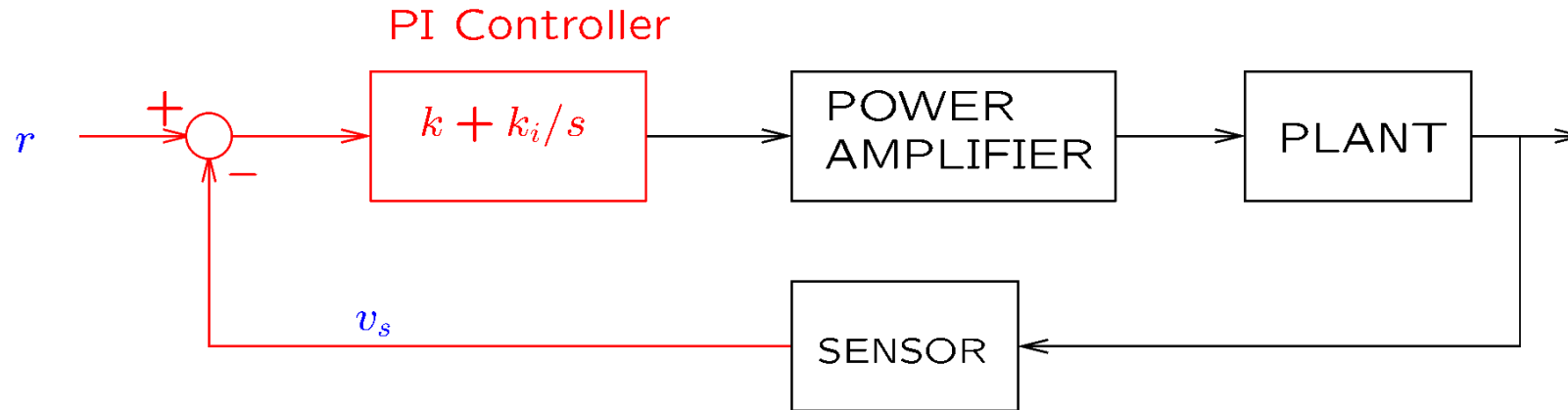



*Implement in hardware the highlighted part of the control system.*

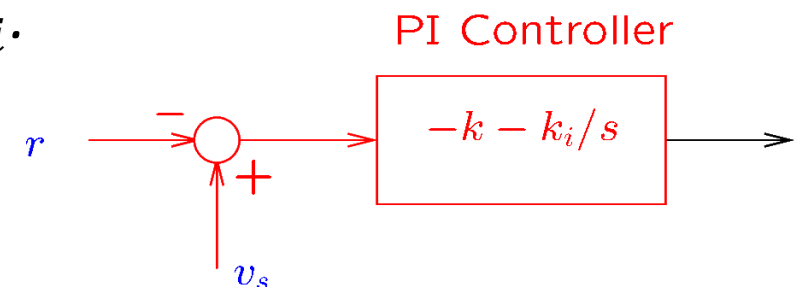- *Note that transfer functions implemented with the inverting amplifier have negative coefficients.*
- *Therefore, the controller coefficients will be  $-k$  and  $-k_i$ .*
- *To compensate for the minus signs, the signs of the summing junction will be reversed.*


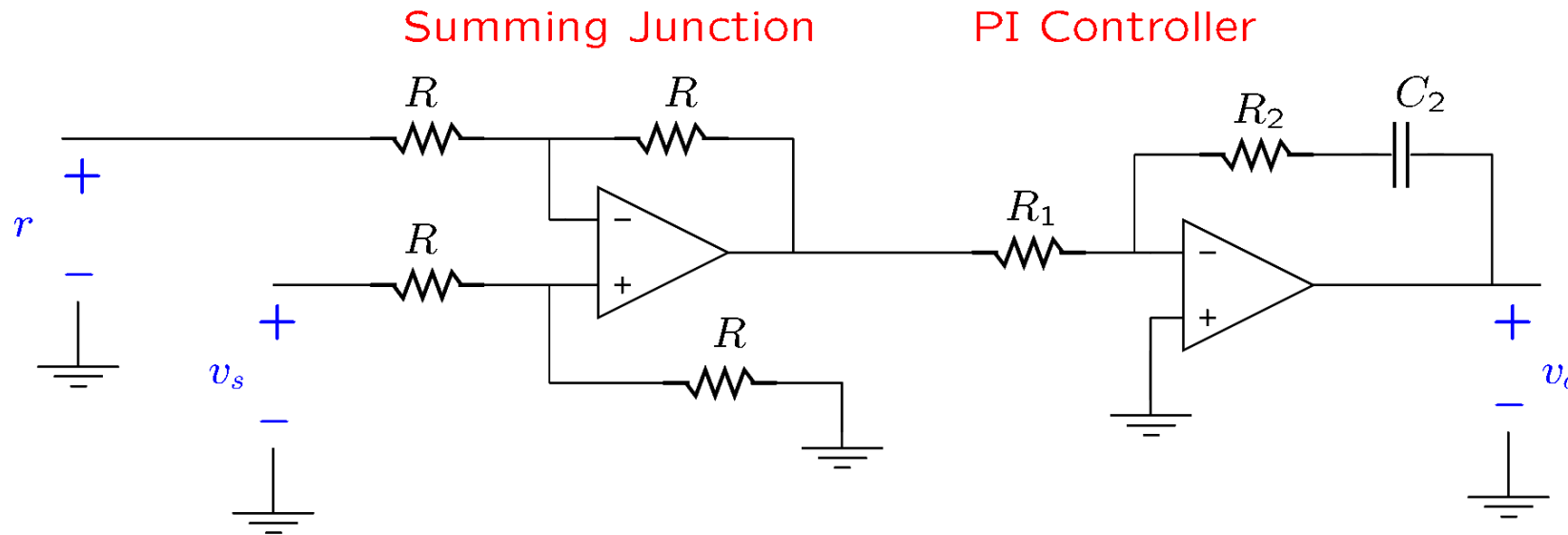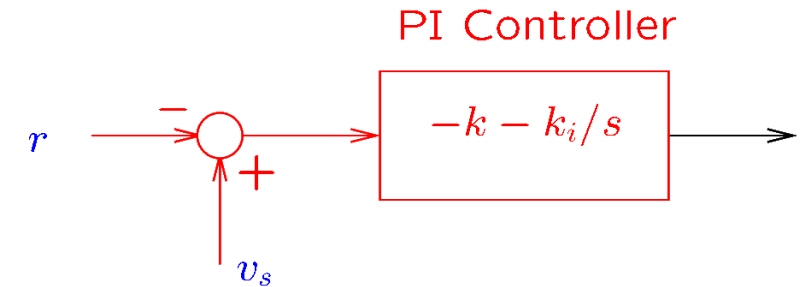
# Transfer Functions—Example 4



- A possible solution would utilize two cascaded stages:
  - The first stage implements the summing junction.
  - The second stage implements the PI controller.



- However, if the sign of the sensor signal  $v_s$  can be changed without an additional stage, there is a simpler solution that uses a single operational amplifier.
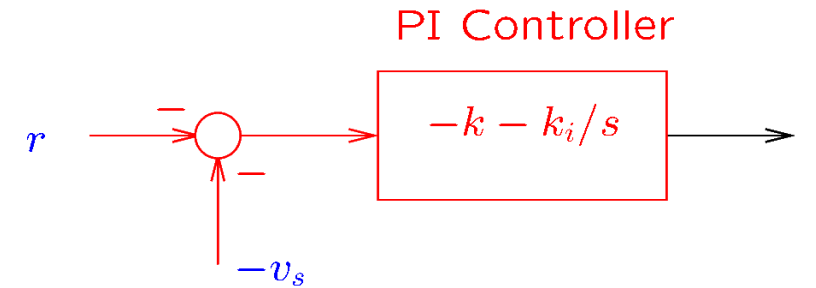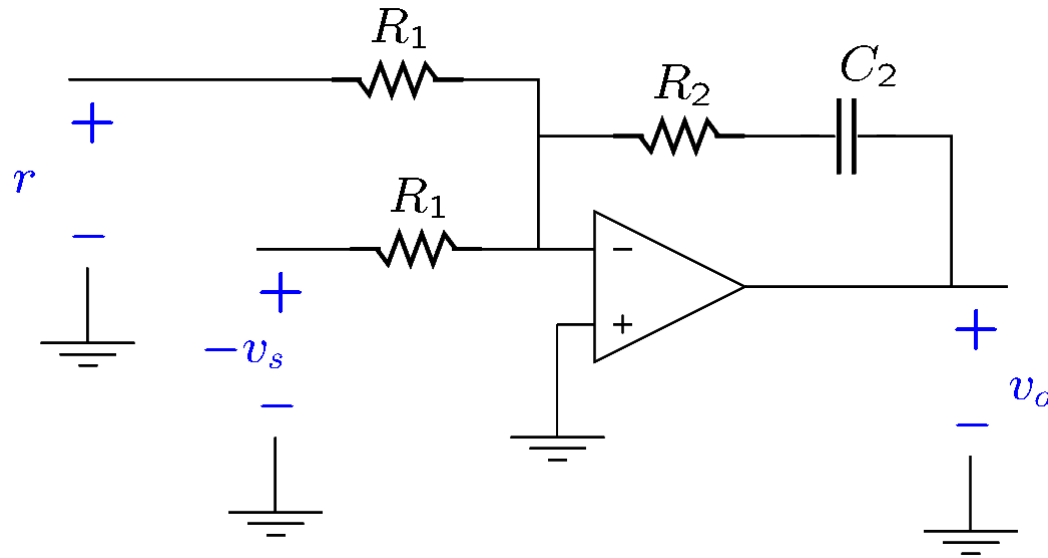
# Transfer Functions—Example 4

- A simpler solution is to combine the summing junction and the controller into a single stage.*



$$k = \frac{R_2}{R_1} \text{ and } k_i = \frac{1}{R_1 C_2}$$