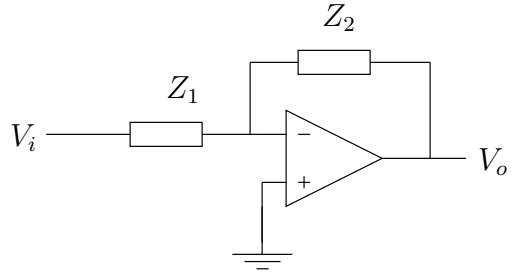
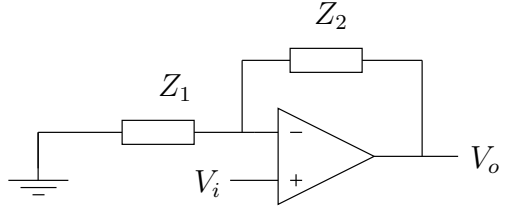
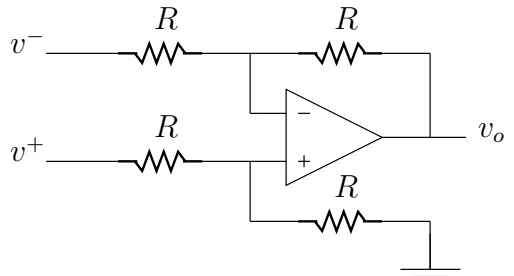
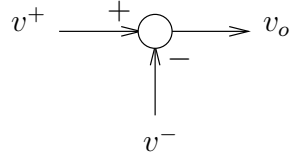
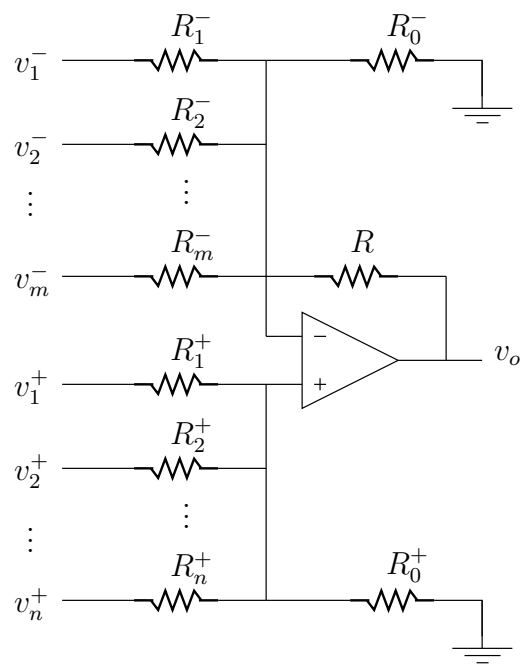
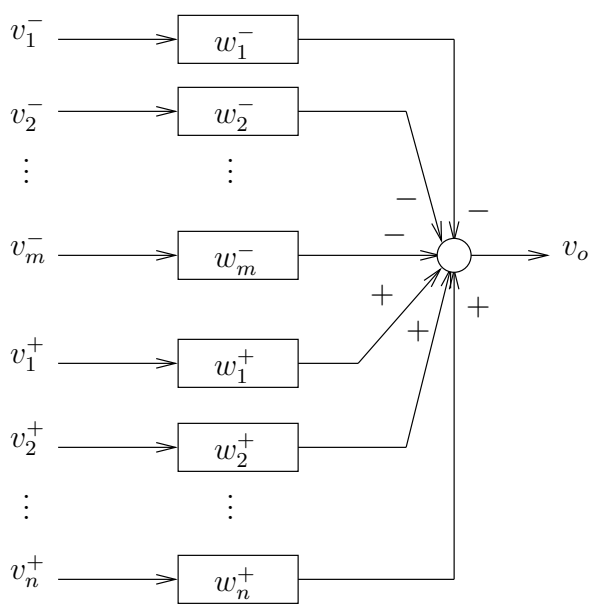


Note:  $Z_i$  denotes the equivalent impedance of the input w.r.t. ground (the input impedance).

CIRCUIT	MODEL
	$V_i \longrightarrow \boxed{-\frac{Z_2(s)}{Z_1(s)}} \longrightarrow V_o$ $Z_i(s) = Z_1(s)$
	$V_i \longrightarrow \boxed{1 + \frac{Z_2(s)}{Z_1(s)}} \longrightarrow V_o$ $Z_i(s) \rightarrow \infty \text{ (ideally)}$
	 $Z_i^- = R \quad Z_i^+ = 2R$
	 <p>If (but not only if) <math>1 + \sum_{i=0}^m \frac{R}{R_i^-} = \sum_{i=0}^n \frac{R}{R_i^+}</math>  then <math>w_i^- = \frac{R}{R_i^-}</math> and <math>w_i^+ = \frac{R}{R_i^+}</math></p>